

HOW TO DESIGN DIGITAL CIRCUITS FROM SCRATCH

\$1.25 ■ DEC. 1978

Radio IND Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

COVER STORY

SOLAR ENERGY CONTROL

A guide to interfacing and controlling solar energy panels. Story starts on page 35.

HI-FI SPEAKER SYSTEM

State-of-the-art time-compensated design you can build yourself for true hi-fi sound. Construction starts on page 38.

REMOTE TELEPHONE EAR

Easy to build telephone accessory lets you monitor the sounds in your home from a remote location. Turn to page 67.

NUMBER CRUNCHER

Math board for 1802-based microcomputers speeds execution time and saves memory. Construction details start on page 45.

PROM'S TO THE RESCUE

New applications for the PROM make digital circuits simpler. Story starts on page 43.

PLUS:

- ★ Design your Own Computer Power Supply
- ★ Do Hi-Fi Speaker Cables Make a Difference?
- ★ Build Arcade Quality Tank Game
- ★ Understanding Dynamic Headroom
- ★ R-E Tests
 - Sansui G-9000 Receiver
 - Lectrotech Peak Power Indicator
- ★ Hobby Corner
- ★ Computer Corner
- ★ Jack Darr's Service Clinic




A
GERNSBACK
PUBLICATION

vero

small enclosures

VEROBOX
PLASTIC

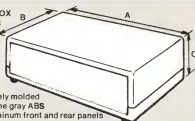

Attractively molded in two-tone gray ABS with aluminum front and rear panels. Accepts circuit boards horizontally or vertically.

ORDER CODE	A	B	C	PRICE
75-1238D	154	85	60	\$6.82
75-3008J	180	120	65	\$8.90
75-1411D	205	140	75	\$9.02




VEROCASE
PLASTIC

Vacuum formed from textured black ABS. Designed for instruments incorporating a keyboard and display. Anodized aluminum panel supplied for component mounting.


ORDER CODE	WIDTH	DEPTH	HEIGHT	PRICE
75-1800J	220	278	100	\$25.70
75-3960E	550	340	120	\$50.31

FLIP TOP BOX

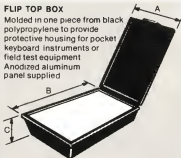Molded in one piece from black polypropylene to provide protective housing for pocket keyboard instruments or field test equipment. Anodized aluminum panel supplied.




ORDER CODE	A	B	C	PRICE
75-3018C	75	130	22	\$5.76
75-3019J	127	196	32	\$7.50

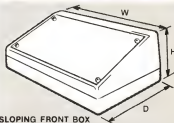

SLOPING FRONT BOX

Sloping front boxes. Two-tone gray with aluminum front panel. Provisions in base for circuit board or plate mounting.

ORDER CODE	WIDTH	DEPTH	HEIGHT	PRICE
75-1798K	171	121	75	\$10.94
65-2523E	220	156	100	\$11.74

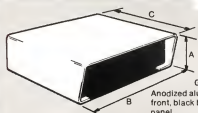


G SERIES CASES

Anodized aluminum cover with visor front, black base, front and rear panel.


ORDER CODE	A	B	C	PRICE
91-2672A	44.0	134.0	123.0	\$12.07
91-2673G	64.0	224.0	176.5	\$18.32

TILT LEG ASSEMBLY FOR PLASTIC VEROBOX

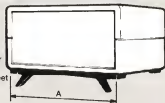A kit containing a tilt leg and four molded feet with rubber inserts which replace the existing box feet and raise the front panel to a convenient viewing angle.




ORDER CODE	A	COMPATIBLE VEROBOX	PRICE
75-1493A	144	75-1238D	\$2.39
85-1494G	170	75-3008J	2.45
75-1492F	193	75-1411D	2.48

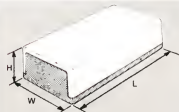


Two-tone gray boxes molded in high impact polystyrene. Lower section provided with threaded inserts for mounting components or circuit boards.

ORDER CODE	WIDTH	LENGTH	HEIGHT	PRICE
65-2514F	50	100	25	\$3.25
65-2518H	65	120	40	4.09
65-2520J	80	150	50	4.68

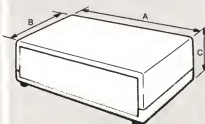

New additions to the series of two-tone gray ABS boxes with aluminum front and rear panels.

ORDER CODE	A	B	C	PRICE
75-2682L	125	65	30	\$5.24
75-2683F	125	65	40	6.08
75-2684A	125	65	50	6.79

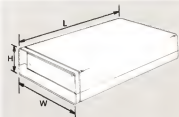

Attractive light gray boxes of high impact polystyrene come complete with anodized aluminum front panel and molded-in compartment for standard 9V battery.

ORDER CODE	WIDTH	LENGTH	HEIGHT	PRICE
65-2036H	68	110	33	\$5.78
65-2068B	92	155	45	8.90
65-2073K	138	190	68	12.09



Vero Electronics, Inc.

171 Bridge Road, Hauppauge, N.Y. 11787
Tel: 516-234-0400 TWX 510-227-8890

No C.O.D.'s. Include \$1.50 for Shipping, with Check or Money Order.

The Age of Affordable Personal Computing Has Finally Arrived.

Ohio Scientific has made a major breakthrough in small computer technology which dramatically reduces the cost of personal computers. By use of custom LSI micro circuits, we have managed to put a complete ultra high performance computer and all necessary interfaces, including the keyboard and power supply, on a single printed circuit board. This new computer actually has more features and higher performance than some home or personal computers that are selling today for up to \$2000. It is more powerful than computer systems which cost over \$20,000 in the early 1970's.

This new machine can entertain your whole family with spectacular video games and cartoons, made possible by its ultra high resolution graphics and super fast BASIC. It can help you with your personal finances and budget planning, made possible by its decimal arithmetic ability and cassette data storage capabilities. It can assist you in school or industry as an ultra powerful scientific calculator, made possible by its advanced scientific

math functions and built-in "immediate" mode which allows complex problem solving without programming! This computer can actually entertain your children while it educates them in topics ranging from naming the Presidents of the United States to tutoring trigonometry all possible by its fast extended BASIC, graphics and data storage ability.

The machine can be economically expanded to assist in your business, remotely control your home, communicate with other computers and perform many other tasks via the broadest line of expansion accessories in the microcomputer industry.

This machine is super easy to use because it communicates naturally in BASIC, an English-like programming language. So you can easily instruct it or program it to do whatever you want, but you don't have to. You don't because it comes with a complete software library on cassette including programs for each application stated above. Ohio Scientific also offers you hundreds of inexpensive programs on ready-to-run cassettes. Program it yourself or just enjoy it; the choice is yours.

Ohio Scientific offers you this remarkable new computer two ways.



Challenger 1P \$349

Fully packaged with power supply. Just plug in a video monitor or TV through an RF converter to be up and running.

Superboard II \$279

For electronic buffs. Fully assembled and tested. Requires +5V at 3 Amps and a video monitor or TV with RF converter to be up and running.



Standard Features

- Uses the ultra powerful 6502 microprocessor
- 8K Microsoft BASIC-in-ROM
- Full feature BASIC runs faster than currently available personal computers and all 8080-based business computers.
- 4K static RAM on board expandable to 8K
- Full 53-key keyboard with upper/lower case and user programmability
- Kansas City standard audio cassette interface for high reliability
- Full machine code monitor and I/O utilities in ROM
- Direct access video display has 1K of dedicated memory (besides 4K user memory), features upper case, lower case, graphics and gaming characters for an effective screen resolution of up to 256 by 256 points. Normal TV's with overscan display about 24 rows of 24 characters; without overscan up to 30 X 30 characters.

Extras

- Available expander board features 24K static RAM (additional), dual mini-floppy interface, port adapter for printer and modem and an OSI 48 line expansion interface.
- Assembler/editor and extended machine code monitor available.

ORDER FORM

Order direct or from your local Ohio Scientific dealer.

- ☐ I'm interested. Send me information on your:
- ☐ Personal Computers ☐ Business Systems
- ☐ Send me a Superboard II \$279 enclosed
- ☐ Send me a Challenger 1P \$349 enclosed
- ☐ Include 4 more K of RAM (8K Total) \$69 more enclosed

Name

Address

City State Zip

Payment by: BAC(VISA) ☐ Master Charge ☐ Money Order ☐

Credit Card Account #

Expires Interbank # (Master Charge)

Ohio Residents add 4% Sales Tax

TOTAL CHARGED OR ENCLOSED

All orders shipped insured UPS unless otherwise requested FOB Aurora, OH

Interested in a bigger system? Ohio Scientific offers 15 other models of microcomputer systems ranging from single board units to 74 million byte hard disk systems.

OHIO SCIENTIFIC
America's Largest Full Line Microcomputer Company
1333 S. Chillicothe Road • Aurora, Ohio 44202 (216) 562-3101

CIRCLE 36 ON FREE INFORMATION CARD

PIÈCE DE RÉSISTANCE



Sylvania, of course. And there are 594 more just as good. It's the most complete line of flameproof resistors in the industry.

Our flameproof resistors come in $\frac{1}{4}$, $\frac{1}{2}$, 1 and 2-watt sizes for use in home entertainment, communications, industrial equipment or any job requiring a fuse resistor. They can replace carbon composition, carbon film, metal film, wirewound and fuse resistors with tolerances of 2, 5, 10 or 20 percent. And noncombustible ceramic construction provides stable resistance plus indefinite shelf life.

All Sylvania flameproof resistors come in color-coded blister packs for easy identification. For a good look see your nearest distributor. You can find his location by contacting GTE Sylvania, Distributor and Special Markets Div., 1025 Westminister Drive, Williamsport, Pa. 17701.

**SYLVANIA**

CIRCLE 34 ON FREE INFORMATION CARD

Electronic
Components

GTE

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Electronics publishers since 1908

DECEMBER 1978 Vol. 49 No. 12

BUILD ONE OF THESE

- 35 **Solar Energy Controller**
A guide to interfacing and controlling solar energy panels.
- 38 **Time-Compensated Speaker System**
State-of-the-art design you can build yourself for true hi-fi sound.
- 45 **NOM Card For The 1802**
Number crunching math board for 1802-based microcomputers speeds execution time and saves memory.
- 67 **Remote Telephone Ear**
Lets you monitor the sounds in your home from a remote location.
- 74 **Tank**
Part II: Final details of this dedicated TV battle game.

DIGITAL ELECTRONICS

- 43 **Making PROM's Work For You**
New applications make digital circuits simpler.
- 56 **Designing Hobby Computer Power Supplies**
How to design and add a power supply for your S-100 mainframe.
- 63 **Digital Circuit Design**
Everything from combinational switching circuits and the Karnaugh map to the Quine-McCluskey method and sequential circuits.
- 78 **Computer Corner**
Software required to control an 8-channel analog signal monitor.

STEREO HI-FI PRO SOUND

- 49 **R-E Lab Tests Sansui G-9000 Receiver**
This 160-watt FM receiver rates excellent.
- 52 **R-E Lab Tests Lectrotech Peak Power Indicator**
A new add-on for your hi-fi.
- 53 **Dynamic Headroom**
A new amplifier measurement from the IHF—it tells why amplifiers with the same rated power may perform differently under varying signal levels.
- 60 **Hi-Fi Speaker Cables**
Ordinary speaker cables can adversely affect sound quality. An in-depth look at newly developed uniquely constructed cables and how well they solve this problem.

TELEVISION

- 80 **Jack Darr's Service Clinic**
Trouble with the color and how to localize the problem.
- 81 **Service Questions**
R-E's Service Editor solves reader problems.

GENERAL ELECTRONICS

- 4 **Looking Ahead**
Preview of tomorrow's news—today.
- 14 **Radar Speed Traps, Detectors, etc.**
Editorial
- 76 **Hobby Corner**
A look at clever reader solutions to radar problems including a rocket launching circuit, a super simple oscillator and a low voltage detector.

EQUIPMENT REPORTS


- 27 **Super Slueth Descrambler**
- 32 **Continental Specialties LP-2 & DP-2 Logic Probes**

DEPARTMENTS

- | | |
|------------------------------|--------------------|
| 130 Advertising Index | 103 Market Center |
| 14 Advertising Sales Offices | 6 New & Timely |
| 96 Computer Products | 94 New Products |
| 131 Free Information Card | 101 Next Month |
| 16 Letters | 98 Stereo Products |
| 100 New Books | |

SEASON'S GREETINGS

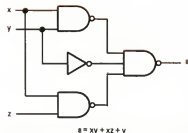*The editors and staff
of Radio-Electronics
join in sending
holiday greetings and
our best wishes for
a happy new year*



DESIGNING DIGITAL CIRCUITS from scratch. The step-by-step approach starts on page 63.

Radio-Electronics, Published monthly by Gamsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, \$9.98, Canada, \$12.98, Other countries, \$14.98. Single copies \$1.25. © 1978 by Gamsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3578) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

TV and hi-fi: Important developments are in the wind in the field of TV sound—a chain of events set in motion by the very limited use of satellites for domestic networking and followed by the telephone company's conversion of its intercity relay systems to diplexed sound (*Radio-Electronics*, July, 1978). Both relay systems now accommodate sound channels capable of a frequency response up to 15 kHz, compared with 5 kHz under AT&T's old system of transmitting TV sound by separate telephone line. Since last January, most network broadcasting (except for an occasional 16-mm movie) has been accompanied by noticeably better sound. But that's not all—AT&T's network lines now are capable of handling two discrete multiplexed sound channels, each with a frequency response out to 15 kHz.

This two-channel sound will be available with the TV signal as soon as a rate schedule is worked out by AT&T and approved by the FCC. There are no stereo TV sets, of course, and TV stations aren't allowed to transmit stereo sound signals—even if they were equipped to do so—so the first use of two-channel sound is likely to be for the simulcast FM-station sound accompanying TV music broadcasts. The diplexed signal along with the TV picture eliminates the complicated synchronizing and phasing processes that are needed when the stereo sound is networked separately from the picture, as traditional in network stereo simulcasts.

So now we have an interesting situation: Most TV broadcasting is accompanied by true hi-fi sound, but virtually no TV receivers are capable of passing it on to viewers. Network television is capable of transmitting stereo or other types of dual-sound signals, but stations aren't permitted to broadcast with dual sound. However, there are signs that this impasse will be broken. Most TV set manufacturers are now working on improved sound systems to take advantage of the better vibes coming from the stations. Don't expect hi-fi perfection, but starting with next spring's lines of sets, some models will offer wider frequency response, higher-powered amplifiers, bigger speakers and better baffling.

For those who can't wait for better TV sets to provide higher-quality sound, there will be a growing number of hi-fi video tuners and receivers, such as those now being developed by Pioneer and Wintec, both in direct response to the better sound offered by stations.

Will the next step be stereo sound? The whole subject is highly controversial, and many broadcasters, as well as some TV set manufacturers, will tell you at the drop of a decibel that stereo isn't suitable for TV—there's not enough music being broadcast, the picture is too small, and so forth. But there are exceptions in both ranks. Projection TV manufacturers are gung ho for stereo sound; as is the Public Broadcasting Service, whose associated stations originate many musical programs. Sylvania also hopes to take leadership among set manufacturers in pushing for stereo.

Even if broadcasters and manufacturers collectively don't want stereo, this doesn't mean they're against two-channel sound. Many approve of a system that was used in

Japan in 1970 (and about to be revived there). This system provides two completely discrete channels, and can be used for language translations, stereo or any other application in which two sound tracks can be used. The broadcasters—led by ABC-TV—see the dual-sound track concept as a winner in bilingual areas such as New York, southern California and Miami, where viewership is low among those whose primary language isn't English. Manufacturers certainly wouldn't mind producing TV sets with special circuitry for selecting sound Channel A, Channel B or stereo.

The next step is expected to be the formation of an industry committee to develop and test various two-track proposals before any proceeding by the FCC. It could take from three to five years before definitive standards are set for stereo and other dual-sound TV broadcasts but they do finally seem to be on the way. And the pressure for stereo won't be lessened in any way when videodiscs come on the market. Many of these discs will have stereo sound, and all videodisc recorders will have jacks for stereo inputs.

New VCR's: Home videocassette recorders are proliferating, with new, more versatile step-up units reaching the market this fall. Perhaps the most fascinating is a programmable unit made by Matsushita Electric and being marketed in two slightly different versions under the Magnavox and RCA brandnames, with other similar units to come. The new VCR takes maximum advantage of the four-hour-per-cassette recording mode of the VHS format. Using a built-in microprocessor, a fluorescent digital display and a 14-pushbutton varactor tuner, the new VCR may be programmed up to one week in advance to record four different shows, automatically turning on and off and switching channels. An optional mode of programming permits the recording of the same show every day of the week.

An interesting feature of the programmable VCR is "electronic indexing." A special electronic cue is placed on the tape at the start of each recording, whether the machine is in the manual or the programmed mode. The beginning of any program then may be located automatically by pushing the fast-forward button.


New VCR's in the Beta and VHS formats have been introduced for outdoor recording. The Sony and JVC units each weighs about 20 pounds. A rechargeable battery will operate the VCR and its associated color camera for one hour on a charge. Accessory tuners and timers are available for recording TV programs off the air.

A new VHS-format recorder by JVC lets you double your television viewing without increasing the amount of time you watch—that is, if you don't mind speeded-up action. A special remote-control switch plays tapes at double speed. Digital encoding keeps the sound at the proper pitch and comprehensible. The same unit provides a freeze-frame picture when the pause button is pressed. A new Hitachi VHS recorder also has the freeze-frame feature. With a new recording head, Hitachi claims a picture signal-to-noise ratio of 46 dB, which it says is the best of any home VCR.

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

STATIC PROFITS? TUNE TO PTS

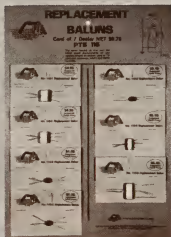Tune In a clearer profit with four new profit-makers from PTS, and you'll discover four ways to higher profits with PTS.



REPLACEMENT BALUNS

A new profit-maker from PTS that will more than pay for itself after you sell the first two baluns. Selection of seven replacements (five models) will replace most baluns found in TV sets, antenna systems, MATV or CATV systems.

Dealer Net. \$9.75.



PTS 8001 COMPONENT ANALYZER

This component test instrument works in or out of circuit. Simple hook-up to any standard oscilloscope. High, medium and low range switch for matching impedance.

Dealer Net \$54.95.



PTS DG-1 DIGITAL POWER SUPPLY

External power supply for substituting voltages in televisions, stereos, radios, computers, micro-processors, appliances, CBs and many other electronic units.

Dealer Net. \$114.95.



PTS DG-4 VOLTAGE CONTROL CENTER/DIGITAL POWER SUPPLY

Independently produces four variable DC supply voltages. Excellent for substituting critical control voltages for TV electronic/varactor tuners, and many other electronic products.

Dealer Net \$178.50.

TUNE ON TO MORE PROFIT, THE PTS WAY.

Now available from PTS stocking distributors or at any of the PTS' 42 company-owned Servicenters. Check the yellow pages for the one nearest you or contact:



PTS ELECTRONICS, INC.

5233 S. HWY. 37 • P.O. 272 • BLOOMINGTON, IN 47401 • 812-824-9331

new & timely

Quartz analog watches tells time with "electronic hands"

Texas Instruments' completely electronic *Time Indicator* watch is an antimagnetic, shock-resistant LCD quartz analog watch that tells time without any moving parts, using "electronic hands." TI believes this design may provide the answer for those who want a watch without gears or other moving parts to wear out, yet need to see a visual time relationship.



TEXAS INSTRUMENTS new *Time Indicator* watches combine the advantages of both mechanical and digital watches.

The liquid crystal display that sweeps the face of the watch (in similar fashion to mechanical hands) is driven by an IC. Several timekeeping modes are available: hours/minutes; minutes/seconds; hours/minutes in another time zone; plus day and date; and a stopwatch gives the elapsed time in hours/minutes, minutes/seconds and seconds/10ths of seconds.

The watch is powered by a lithium-manganese dioxide battery and comes in two styles: round, in either white-gold or yellow-gold tone metal or square in either stainless steel or gold-tone metal; the strap can either be of leather or matching metal clasp bracelet. The watches range in price from \$275 to \$325.

50 Radio Shack Computer Centers to open in 1978-1979

Lewis Kornfeld, president of Tandy Corporation's Radio Shack Division, has announced that 50 new computer sales and service stores will open in 1978-1979; the new ventures will be called Radio Shack Computer Centers.

Although some of the Computer Centers will be located in new or existing Radio Shack stores, most will be separate operations in major market areas. According to Mr. Kornfeld, "their purpose will be to assist area Radio Shack stores in answering computer questions, closing sales and developing quantity sales (particularly of

Radio Shack's TRS-80 system), and peripheral systems to businesses and institutions."

The Centers will provide classroom areas to teach computer use and programming to customers. In addition to servicing Radio Shack computer products, the Centers will sell a variety of components, software and some hardware of brands other than the TRS-80 system.

Video inventions use liquid-crystal switches

Two new inventions use liquid-crystal optical transmission switches that can help reduce the size, price and power requirements of video cameras, screens and projectors.

The "Flying Hole Video Camera" and "Flying Hole Display and Projector" use a two-dimensional array of liquid-crystal switches operated so that all but one are opaque. This "hole" is moved around in a scanning pattern.

In the camera, the light that is transmitted through the hole is converted to electrical signals by a photo detector or color-sensitive photo detectors. In the projector and display, the light is projected through the hole by a light source or a group of color-sensitive light sources. Since the video projector/display does not require a cathode-ray tube, it is small and flat enough to be either wall-mounted or worn on the wrist. The inventions were announced by an independent Canadian inventor, Donald L. Orr.

Wrist device prints messages, aids handicapped

Canon, U.S.A., a subsidiary of Canon, Inc., Tokyo, has developed a small battery-operated wrist device that prints messages



WRIST DEVICE, the *Communicator*, keyboard contains 26 letters, and shift, back and space keys to print messages at a 10 character-per-second speed. The device is a special fast communication aid for nonverbal, deaf and other handicapped persons.

on paper tape designed to provide fast communications for persons suffering from a variety of verbal or motor disabilities.

The device called the *Communicator* is

distributed by Telesensory Systems, Inc., 3408 Hillside Avenue, Palo Alto, CA 94304. It is as small as a pocket dictionary, weighs 11 ounces and can also be worn around the neck. Messages are printed on paper tape at a speed of 10 characters-per-second, with a tape storage capacity of 12,500 characters. The keyboard contains 26 alphabetical letters arranged according to frequency of use, plus it contains shift, back and space keys. Pressing the shift pushbutton allows numbers and symbols to be used, and vowels and consonants are differentiated by color. The *Communicator* sells for \$549.

Computerized information system is developed for Canadian TV viewers

Three Canadian firms, Bell Canada, Southam Press, Ltd., and Torstar Corporation have agreed to cosponsor a pilot demonstration of a data system that will provide information stored at a central computer and transmitted via telephone lines to TV viewers whose sets are connected to the computer center.

The data system (known generically as videotex) consists of a computer connected to a single TV set with an attached keyboard. Using the keyboard a viewer can retrieve preprogrammed data, which is then displayed on the screen either as words or graphically. A Bell Canada spokesman said that this pilot demonstration will be followed by a more extensive market study later in 1980, in which the computer will be connected to several home TV terminals. Suggested future applications for the system are in providing weather news, travel data, general news programs, entertainment and even some advertising.

NESDA/ISCET choose officers and distribute awards at 1978 NESD

Approximately 600 persons attended the August 1978 National Electronics Service Convention (NESC) in Portland, OR. Among the many scheduled events, including a trade show, seminars and many social functions, were both the NESDA and ISCET conventions.

The ISCET and NESDA agenda included the election of officers for 1978-1979, as follows:

For NESDA—president, Robert A. Vilont; vice president, Warren Baker; secretary, West Correll; treasurer, George Simpson; and regional officers Ted Stackhouse, Dorothy Cicchetti, Joe Gately, Billy Williams, Art Nelson, Bill Abernathy, Keith Knos, Jack Kelly, Bill Lawler, and Dick Scott.

For ISCET—president, Jesse Leach (also serving ex-officio on the NESDA executive committee and council); vice chairman,

continued on page 12

We've done the impossible again!

A versatile and superior frequency counter kit for only \$89.95



Now you can forget about price/performance trade-offs when you select a frequency counter. In Sabtronics' Model 8100 you get features you once expected to pay several hundreds of dollars for. But you pay only our low, low price of \$89.95!

Dare to Compare. This frequency counter, using LSI technology, has the performance and input characteristics you demand. Note the specifications: You will see that the frequency range is guaranteed all the way to 100 MHz; and a high or low input impedance allows you to select for high-frequency operation. And you'll see a sensitivity that holds well over the frequency range; convenient selectable gate-time for best resolution; and selectable attenuation; and even an optional pre-scaler. Note the highly accurate time base, and its excellent ageing and temperature characteristics. And a full 8-digit LED display with floating decimal point, leading zero suppression, and overflow indicator.

You would expect to find all these features together only on a much higher-priced instrument. But Sabtronics' advanced digital technology combines with your own skill — you assemble this kit from our easy-to-follow instructions — to make it possible for you to have this fine frequency counter at a fraction of what you would otherwise expect to pay.

Free 10-day trial

Examine the 8100 Frequency Counter Kit for 10 days. If not completely satisfied, return unassembled for full refund of \$89.95 purchase price.

sabtronics 
INTERNATIONAL INC.

13426 Floyd Circle • Dallas, Texas 75243
Telephone 214/783-0994

Brief Specifications

- Frequency Range: 20 Hz to 100 MHz guaranteed (10 Hz to 120 MHz typical)
- Sensitivity: 25 mV RMS, 20 Hz to 70 MHz (20 mV typical); 45 mV RMS, 70 MHz to 120 MHz (30 mV typical)
- Selectable Impedance: 1 M Ω at 25 pF, or 50 Ω
- Selectable Attenuation: X1, X10, or X100
- Accuracy: ± 1 Hz plus time-base accuracy
- Ageing rate: ± 5 ppm/yr
- Temperature stability: ± 10 ppm, 0 $^{\circ}$ to 50 $^{\circ}$ C
- Selectable Gate-time: 0.1 sec, 1 sec., or 10 sec.
- 8-digit LED display with floating D.P., overflow indication
- Input: 9-15 VDC, 350 mA (550 mA with optional prescaler)
- Input protection: 150 V RMS, 20 Hz to 10 kHz; 30 V RMS to 2 MHz; and 3 V RMS to 100 MHz
- Optional prescaler extends frequency range to 650 MHz. (Available soon)

To: Sabtronics International, Inc.
13426 Floyd Circle, Dallas, TX 75243

RE-12

Please send me _____ Sabtronics Model 8100
Frequency Counter Kit(s) at \$89.95 each \$ _____
Texas Residents add Sales Tax \$ _____
Shipping and handling, \$5.00 per unit \$ _____
(USA only) * \$ _____

Payment enclosed ☐
Charge my Master Charge ☐
Visa ☐

Account No. _____ Exp. Date _____

Name _____

Street _____

City _____

State _____ Zip _____

*Canada \$6.50. All other countries \$19.00 Airmail.

**NRI training in TV
and Audio Servicing
keeps up with the
state of the art.
Now you can learn to
service video cassette
and disc systems.**





You build color TV, hi-fi, professional instruments.

Now, in addition to learning color TV and audio systems servicing, you get state-of-the-art lessons in maintaining and repairing video cassette recorders, playbacks and the amazing new video disc players, both mechanical and laser-beam types.

Learn at Home in Your Spare Time

And you learn right at home, at your own convenience, without quitting your job or going to night school. NRI "bite-size" lessons make learning easier...NRI "hands-on" training gives you practical bench experience as you progress. You not only get theory, you actually build and test electronic circuits, a complete audio system, even a color TV.

Build Color TV, 4-Channel Audio

As part of your training in NRI's Master Course in TV and Audio Servicing, you actually assemble and keep NRI's exclusive,

designed-for-learning 25" diagonal color TV. As you build it, you introduce and correct electronic faults, study circuits to gain a better understanding of what they're for and how they interface with others.

Likewise, as part of your audio training, you construct a 4-channel stereo amplifier and tuner, complete with cabinet and speakers. You even assemble professional-grade test instruments, so you know what makes them tick, too. Then you use them in your course, keep them for actual TV and audio servicing work.

NRI Includes the Instruments You Need

You start by building a transistorized volt-ohm meter which you use for basic training in electronic theory. Then you assemble a digital CMOS frequency counter for use with lessons in analog and digital circuitry, FM principles. You also get an integrated circuit TV pattern generator, and an advanced design solid-state 5" triggered-sweep oscilloscope. Use them for learning, then use them for earning.

NRI Training Works... Choice of the Pros

More than 60 years and a million students later, NRI is still first choice in home study schools. A national survey of successful TV repairmen shows that more than half have had home study training, and among them, it's NRI 3 to 1 over any other school. (Summary of survey on request.)

That's because you can't beat the training and you can't beat the value! For hundreds of dollars less than competing schools, NRI gives you both color TV and audio...and now includes training in video cassette and disc systems. Send for our free catalog and see for yourself why NRI works for you.



Other NRI training includes Computer Technology, Complete Communications Electronics.

Free Catalog... No Salesman Will Call

Our free 100-page catalog completely describes all the equipment and every lesson. You can choose from five different TV and audio courses. Or explore the opportunities in other NRI home study courses like Computer Technology, CB and Mobile Radio, Aircraft and Marine Radio, or Complete Communications. Send the postage-paid card today and get a head start on the state of the art.

If card has been removed, write to:



NRI-Schools
McGraw Hill Continuing
Education Center
3939 Wisconsin Ave.
Washington, D.C. 20016

Learn at home at your convenience.



new & timely

continued from page 6

Forest Belt; secretary, Leon Howland; and treasurer, George Sopocko.

Those present at the ISCTET convention voted unanimously to return ISCTET headquarters to NESDA facilities in Indianapolis. A Joint Internal Affairs Committee was appointed by ISCTET and NESDA presidents to study and consider the question of ISCTET/NESDA autonomy. A report, incorporating the results of an opinion survey taken among the respective bodies, will be presented at a joint ISCTET/NESDA membership meeting in 1979. The committee is composed of ISCTET members Herschel B. Lawhorn, Dorman L. McDonald and Larry Steckler (chairman), and NESDA members Warren Baker, Jack Kelly and Dick Scott.

Among other scheduled events was a NESDA awards banquet at which LeRoy Ragsdale, outgoing president, received both the "Man of the Year" award and the "NESDA Outstanding Officer" award. Other winners were Don Surrette, Leo Cloutier, Nolan Boone, Fred Schuneman, Warren Baker, Gene Dillingham, Ray McAllister, Keith Knos, and Morris Finneburgh, Sr.

Another NESD highlight was the induction into the Electronics Hall of Fame of two new members: Enos Rice (CES/CET) and (posthumously) the late Ralph Johonnot. Mr. Rice, who is 74 years old, was honored for his 44½ years in the service industry and for his long involvement in and support of NESD activities. The late Mr. Johonnot was cited for his long career in the service industry; for his many years as an officer with the California State Electronics Association; and for his part in the inception of the CET program and the Western States Conference.

The 1979 NESD will be held in Tucson, AZ, concurrently with the Arizona State Electronics Association Convention.

Integrated optical device has multiple applications

A small integrated optical device that can have multiple applications has been developed by Bell Labs. It can be used as a logic element in optical memories; a pulse shaper and limiter; an optical switch; a difference amplifier; and as an "optical triode."

Operating at extremely low power levels over a wide range of wavelengths, the device is an optical waveguide version of a nonlinear Fabry-Perot resonator whose nonlinear characteristics are produced by using a photodetector output to drive the resonator's electro-optical elements. Other features include acceptance of electrical or optical outputs; its nonlinearity can be modified using a nonlinear circuit; acceptance of multiple logic inputs; and multilevel operation.

The device is processed using standard IC techniques by diffusing titanium ions

onto an electro-optic lithium-niobate substrate. Incoming light rays are reflected back and forth between dielectric mirrors affixed to the cleaved ends of the substrate material. A beam splitter transmits a portion of this light to the detector whose output is used to create an electric field



BELL LABS integrated optical device is Fabry-Perot resonator formed by dielectric mirrors on the ends of the electro-optic lithium-niobate substrate material.

between the electrodes on the crystal that modulates the refractive index of the crystal and produces the nonlinear characteristics.

In multilevel operation or A/D conversion, a high gain is required in the feedback loop, providing as many as 15 transmission levels. With less feedback and the resonator tuned for transmission showing a hysteresis characteristic, the device functions as a memory element. When operated in a high-transmission state, its constant power output lets it operate as an optical limiter. In the "optical triode" mode, when the resonator is tuned to transmit an S-shaped waveform, power transmitted through the waveguide changes rapidly according to the output. A small degree of light at the detector produces a vast change in transmitted light; a weak light signal falling on the detector controls the transmission of a power light beam on the device.

Morizono, Leonard, Staes win SMPTE awards

The Society of Motion Picture and Television Engineers (SMPTE) awarded the 1978 David Sarnoff Gold Medal to Masahiko Morizono of Sony Corporation. Mr. Morizono, general manager of Sony's Video Products Division, was cited for his leadership and outstanding engineering accomplishments in developing TV electronic news gathering (ENG) equipment. Mr. Morizono's other achievements include the development of portable helical-scan VTR systems exhibiting high-calibre editing capabilities; plus the design and development of audio and instrumentation recorders, U-matic cassette recorders, time-base cor-

rectors, cameras and accessories.

SMPTE also presented its 1978 Journal award to Eugene Leonard, Da Vinci Systems Group, with honorable mention to K. Staes, Agfa-Gevaert N.V., for their paper published in the October and August 1977 SMPTE Journal, respectively.

The award was presented at the Society's annual Awards Presentation in October, 1978, at the Americana Hotel, New York City.

Zenith releases three-hour VCR, color cameras, tape

A three-hour video cassette recorder, two color cameras and a three-hour-format cassette tape are all part of Zenith Radio Corporation's new fall line.

The model KR9000W is a single-speed VCR that can record up to three hours of programming using Zenith's three-hour tape. The remote PAUSE switch lets you stop the tape in either playback or record modes, so that you can edit during recording or stop playback if you must leave the room. Other controls include a six-push-button keyboard, a clock/timer, UHF/VHF tuners, automatic fine tuning control, and a special tracking feature to handle variations in prerecorded tapes.



THREE-HOUR VIDEO CASSETTE RECORDER (model KR9000W) released by Zenith is a single-speed unit with built-in UHF/VHF tuners; timer; standard pushbutton controls; tracking switch; remote PAUSE control; and tape counter with memory.

The two color cameras for use with the VCR (models KC1000 and KC1250) offer a number of significant features: the model KC1000 has a pop-up viewfinder that matches the view angle of the 25-mm-long barrel lens designed to be used with a tri-electrode vidicon tube; a built-in mike; a remote PAUSE switch; plus adjustable temperature and brightness controls and an automatic light-level switch. The model KC1250 (which incorporates all the features of the model KC1000 color camera) also has a 6:1 Canon zoom lens incorporating a viewfinder with a 1½-inch black-and-white monitor screen. Suggested retail price range: \$2095—\$1395. R-E

Regulated Power Supply



- ★ Uses LM 309K
- ★ Heat sink provided
- ★ P.C. board construction
- ★ Provides a solid 1 amp @ 5V
- ★ Includes components, hardware and instructions
- ★ Size: 3-1/2" x 5" x 2" high

JE200 5v 1amp \$14.95

Function Generator Kit



- ★ Provides 3 basic waveforms: sine, triangle & square wave
- ★ Frequency range from 1 Hz to 100K Hz
- ★ Output amplitude from 0-volts to over 6 volts (peak to peak)
- ★ Uses a 12V supply or a $\pm 6V$ split supply
- ★ Includes chip, P.C. board, components and instructions.

JE2206B \$19.95

Digital Stopwatch Kit



- ★ Use Intersil 7205 Chip
- ★ Plated thru double-sided P.C. Board
- ★ LED display (red)
- ★ Times to 59 min. 59.59 sec. with auto reset
- ★ Quartz crystal controlled
- ★ Three stopwatches in one: single event, split (cumulative) and taylor (sequential timing)
- ★ Uses 3 penlite batteries
- ★ Size: 4.5" x 2.15" x .90"

JE900 \$39.95

4-Digit Clock Kit



- ★ Bright .357" ht. red display
- ★ Sequential flashing colon
- ★ 12 or 24 hour operation
- ★ Extruded aluminum case (black)
- ★ Pressure switches for hours, minutes and hold functions
- ★ Includes all components, case and wall transformer
- ★ Size: 3-1/4" x 1-3/4" x 1-1/4"

JE730 \$14.95

6-Digit Clock Kit



- ★ Bright .300 ht. common cathode display
- ★ Uses MM5314 clock chip
- ★ Switches for hours, minutes and hold functions
- ★ Hours easily viewable to 20 feet
- ★ Simulated walnut case
- ★ 115 VAC operation
- ★ 12 or 24 hour operation
- ★ Includes all components, case and wall transformer
- ★ Size: 6-3/4" x 3-1/8" x 1-3/4"

JE701 \$19.95

Jumbo 6-Digit Clock Kit



- ★ Four .630" ht. and two .300" ht. common anode displays
- ★ Uses MM5314 clock chip
- ★ Switches for hours, minutes and hold functions
- ★ Hours easily viewable to 30 feet
- ★ Simulated walnut case
- ★ 115 VAC operation
- ★ 12 or 24 hour operation
- ★ Includes all components, case and wall transformer
- ★ Size: 6-3/4" x 3-1/8" x 1-3/4"

JE747 \$29.95

AVAILABLE AT YOUR LOCAL Jim-pak[®] DEALER TODAY !!

For Dealer Information, write or phone JIM-PAK[®], 1021 Howard Avenue, San Carlos, California 94070 Ph. (415) 592-8097

Radar Speed Traps, Detectors and Countermeasures

Technology is a wonderful thing. It starts off by doing a job. We can use radar to identify speeders on the highways . . . those people who endanger the lives of others using American highways. It can also help increase the monies received by a municipality in traffic fines. And it's been with us for a long time now.

Recently, electronic countermeasures have become available to the public in the form of detectors that warn you when you near a radar trap. Government agencies have fought these devices in several ways—made them illegal in some states, used portable units, different frequencies. Here's the latest development . . . police departments are buying miniature low-power radar transmitters to sprinkle along the sides of the road to trigger those radar detectors. Maybe they hope that after you've run through three or four false alarms you'll ignore the real radar and contribute some dollars to the local budget. By the way, those transmitters are frequently made by the same people who make your radar detector.

Then comes the latest countermeasure, a nifty little radar transmitter for the motorist. According to the outfit offering it, you simply dial in the speed you want the radar trap to clock you at. Your transmitter then issues a signal that tells the police you're only going 30 MPH or whatever you select. We're deliberately not listing the name or address of the manufacturer since we don't think such a device is legal under FCC rules. Please don't write us for that information because we won't respond. But what we would like to know is what you think of such devices and can you dream up any that are even better.

Electronic countermeasures aren't new, but what a funny world it is when so many dollars are being spent in a battle with the traffic laws. Maybe some serious thought to raising the speed limits to a reasonable level would make more sense.

Larry Steckler
LARRY STECKLER
Editor

Radio-Electronics®

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback, editor-in-chief and publisher

Larry Steckler, KTX-3644, CET, editor

Arthur Kleiman, KTZ-3288, managing editor

Robert F. Scott, CET, W2PWG, KKK-8533, technical editor

Sonia Greenbaum, copy editor

Jack Darr, CET service editor

Leonard Feldman contributing high-fidelity editor

Karl Savon, semiconductor editor

David Lachenbruch, contributing editor

Earl "Doc" Savage, K4SDS, hobby editor

Vincent P. Cicienja, production manager

Harriet I. Matysko, circulation director

Arline R. Bailey, advertising coordinator

Cover design by Louis G. Rubsamen

Cover photo by Bob Homan

Radio Electronics is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003
(212) 777-6400

President: M. Harvey Gernsback
Vice President: Larry Steckler
Treasurer: Carol A. Gernsback
Secretary: Bertina Baer

ADVERTISING SALES

Paul McGinnis
Director of Marketing

EAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
The Ralph Bergen Co.
540 Frontage Road—Suite 361-A
Northfield, Illinois 60093
(312) 446-1444

PACIFIC COAST

Mountain States
Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810
Sales Mart Building
1485 Bayshore Blvd., Box 140
San Francisco, CA 94124
(415) 467-0125



ALL NEW

Real-State-of-the-Art

TWO NEW AC•DC•BATTERY PORTABLE COUNTERS

OPTO-8000.1A 10Hz to 600 MHz — FREQUENCY COUNTER

- Precision TCXO time base 0.1 PPM Stability 17-40°C
- Super Sensitivity with preamps in both HI-Z & 50 Ohm inputs <10mV to 50MHz, 25 mV @ 150 MHz <50mV to 600MHz
- Auto Decimal Point • Aluminum Case • Socketed IC's
- Three position attenuator: X1, X10, X100 (avoids false counting)

#OPTO-8000.1A	Factory Assembled	\$329.95
#OPTO-8000.1AK	Kit Form	\$279.95
#NI-CAD-80	NI-CAD Battery Pack	\$ 19.95

OPTO-7000 10 Hz to 600 MHz MINIATURE COUNTER

- XTAL (TCXO) Time Base ± 0.08 PPM/°C
 - Aluminum Case • HI-Z & 50 Ohm inputs
 - 1 Sec. & 1/10 Sec. Gate times • Auto Dec. Pt.
 - Built-in Prescaler and Preamps Standard
- | | | |
|-------------|--|----------|
| #OPTO-7000 | Factory Assembled - 1 Year-Guar. | \$139.95 |
| #OPTO-7000K | Kit Form | 99.95 |
| #AC-70 | AC Power Pack | 4.95 |
| #NI-CAD-70 | NI-CAD Battery Pack | 19.95 |
| #TCXO-70 | Precision TCXO Time Base
<0.1PPM, 17-40°C | 79.95 |

ACCESSORIES

PROBES:

#P-100	50 Ohm, 1X	\$13.95
#P-101	Lo-Pass	16.95
#P-102	H1-Z, 2X	16.95
#AP-8015	UHF Counter Preamp 20 MHz to 600 MHz 15-50 DB Gain (Not Shown)	\$49.95/Kit \$39.95

#D-450 Antenna
Rubber Duck RF Pick-up 450 MHz ... \$12.50

#D-146 Same as above
146.5MHz ... \$12.50

#RA-BNC Right-Angle BNC Adapter for
above Antenna ... 2.95



ORDER FACTORY DIRECT — PHONE OR MAIL

TERMS: Orders to U.S. and Canada, add 5% to maximum of \$10.00 per order for shipping, handling and insurance. To all other countries, add 10% of total order. Florida residents add 4% state tax. C.O.D. fee: \$1.00. Personal checks must clear before merchandise is shipped.



OPTOELECTRONICS, INC.

5821 NE 14 Avenue
Ft. Lauderdale, FL 33334
Phones: (305) 771-2050 771-2051

Phone orders accepted

letters

WHAT IS AN ELECTRONIC ENGINEER?

As an engineer and head of a growing organization, I often meet people who don't really know what an electronic engineer does. All too often these people visualize an engineer as "someone who sits in a cave and designs things." Nothing could be farther from the truth, and I'd like to dispel this myth.

As I see it, the electronic engineer has the job of creating new electronic equipment or devices using the latest technology and to be manufactured at the lowest cost. In short, his job is to make money for the company that employs him. Besides circuit design, you'll find the engineer assisting in all areas from design to final product. And he will often be there when the design is being upgraded!

To be more specific, a typical engineer can spend as little as 10% of his time on actual circuit design. (This depends on the project, of course!) The rest of his time is

spent assisting draftsmen in circuit-board layout, assisting in package design, writing specifications for the product, selecting components and materials for the production models—not to mention the building of the prototypes!

After the device is built on the production line, there are process-control problems to resolve, quality-control problems and more. Ever see 20,000 pieces of equipment roll off a production line—defective? This same engineer may step in and solve the problem—saving the company money. This is engineering in its finest hour, and an important distinction. You'll find most engineers in industry doing at least most of these things, and often much more. The engineer is rewarded with a sense of accomplishment, a modest salary and, if he's good, a chance at getting a management level job.

Now that you know what an engineer does, let's look at working with IC's. Actually, working with IC building blocks on

paper isn't too hard. The computer fans do this often, as can anyone with the IC handbook. I believe this sort of work should be called *designing*. It is different from *engineering* because the designer generally does not become involved with all the areas mentioned previously; at least this has been true of the "designers" I know. Also, an engineer designs a circuit by either selecting components known to best fit the job from past experience, or by using components of the latest design. This process requires an extensive knowledge of electronic circuitry, electronic components, plus manufacturing processes. All this expertise is necessary to build a project easily at the lowest cost. . . and cost is the name of the game in electronics today. None of the designers I know have the knowledge to optimize their circuitry. Also an extensive knowledge of electronics is important when the production line shuts down—an engineer would know how to start it up, a designer might not. And that's what sepa-

Double your capability.

The VIZ Supplysts™

Power supplies with built-in circuit testing capability.

Only the VIZ Supplysts let you power equipment and circuits *and* test dc voltage points, all with the same instrument.

The Supplysts speed your work, help cut down bench clutter, and free VOMs for other jobs. And even with their extra testing capability, they cost less than most quality fully-regulated power supplies.



VIZ
7105



Single 0-50Vdc, 0-2A supply
with two 0-99.9V DC voltmeters
WP-705 \$240.00



Single 0-25Vdc, 0-4A supply
with two 0-99.9V DC voltmeters
WP-706 \$240.00



Dual Supplyst
Two 0-25Vdc, 0-2A supplies
with two 0-99.9V DC voltmeters
WP-707 \$299.00



Triple Supplyst
Two 0-20Vdc, 0-2A supplies
One 5Vdc (to 4A) fixed-output supply
with two 0-99.9V DC voltmeters
WP-708 \$333.00



The Circuit Tester line
Accuracy and stability assured

VIZ

VIZ Test Instruments Group 335 E. Price St. Philadelphia, PA 19144

CIRCLE 75 ON FREE INFORMATION CARD

rates the designers from the engineers—*knowledge and experience!*

If there are any doubters among the designers, let's see them design an 8-bit A/D converter for under \$5. It's been done—but not by designers. Cost is the reason; an IC block approach costs too much.

To sum up, I propose that the people who string IC's together should be called "designers," and people who do the same but have extensive knowledge about their product should be called "engineers."

GARY MCCLELLAN

S-100 BUS COMPANIES

I recently received from you a list of companies dealing with the S-100 bus.

I was somewhat surprised to see that the list was only two pages long. And it didn't even include the manufacturers of the equipment I have running in my system. Therefore, I decided to do a bit of research on a small scale. I looked through just the February 1978 issue of *Interface Age* and the February 1978 issue of *Kilobaud*, and the only company I knew about that I couldn't find was PolyMorphic Systems, the manufacturer of my computer.

Therefore, I am including a list of the companies I found less than the ones on your list, plus phone numbers. I've listed them in the order I found them:

Seattle Computer Products
16611 111th St. S.E.
Renton, WA 98055
(206) 255-0750

Alpha Microsystems
17875 Skypark North
Irvine, CA 92714
(714) 957-1404

Space Byte Systems Group
1720 Pontius Ave., Suite 201
Los Angeles, CA 90025
(213) 468-8080

Paratronics, Inc.
800 Charcot Ave.
San Jose, CA 95131
(408) 263-2252

MECA
7026 O.W.S. Rd.
Yucca Valley, CA 92284
(714) 365-7686


Info 2000 Corporation
20630 South Leapwood Ave.
Carson, CA 90746
(213) 532-1702

Trace Electronics, Inc.
P.O. Box 3247
Hampton Station
Reading, PA 19604
(215) 779-3677

Forethought Products
P.O. Box 386-E
Coburg, OR 97401
(503) 485-8575

Wameco, Inc.
3107 Laneview Drive
San Jose, CA 95132
No telephone listing

continued on page 22

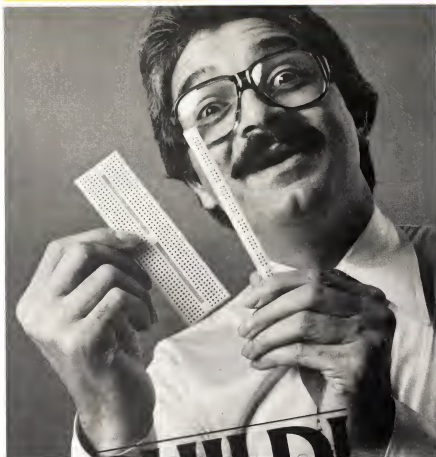

A P Terminal and Distribution Strips are ideal building blocks for your breadboarding.

Now you can put together as simple or as elaborate a breadboard as you want—and be sure of top quality all the way—and pay only for what you need. Using A P Terminal and Distribution Strips as modules is the world's most economical way to assemble full-performance solderless breadboards.

You know how our strips work. Your electronic components plug right into the spring clip terminals behind

each hole. You complete your circuits with ordinary solid wire jumpers—you don't need special patch cords. Terminals clip tight, make superb contact time after time. (They're noncorrosive copper alloy 770.)

These versatile building blocks come in a wide variety of shapes and sizes, and we include hardware and mounting templates with each strip. You get all the flexibility in the world.

Where? At your nearby A P Products dealer. Need the address? Phone (toll-free) 800-321-9668. And ask for the complete A P catalog, *The Faster and Easier Book*.



A P PRODUCTS INCORPORATED

Box 110-B • 72 Corwin Drive
Painesville, Ohio 44077
Tel. 216/354-2101
TWX: 810-425-2250

Faster and Easier is what we're all about.

CIRCLE 70 ON FREE INFORMATION CARD



A new introductory Electronics



DESIGNING WITH TTL INTEGRATED CIRCUITS. By IC Applications Staff of Texas Instruments, Inc. 322 pp., 399 illus. For general, technical, and non-engineer managers, all the information you need to get the most out of TTL devices—their design, economics, features, performance, applications.
537/458 Pub. Pr., \$31.50 Club Pr., \$22.50

HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN. By D. F. Stout. Edited by M. Kaufman. 434 pp., 223 illus. Compact, concise, highly concentrated, and containing a storehouse of information, this one-stop volume will help you solve any op amp circuit problem!
617/97X Pub. Pr., \$29.65 Club Pr., \$17.50

DESIGNING WITH OPERATIONAL AMPLIFIERS. Applications Alternatives. By J. G. Graeme. 269 pp., 203 illus. You can now guarantee that every electronics decision you make will be easier, more productive, freer of error—and more consistently cost-effective! Topics include signal amplifiers, signal conditioners, absolute-value circuits, signal generators, computing circuits, data transmission circuits, and test and measurement circuits.
238/91X Pub. Pr., \$21.50 Club Pr., \$15.50

STANDARD HANDBOOK OF ENGINEERING CALCULATIONS. By T.G. Hicks, Editor-in-Chief. 1,200 pp., 428 illus. Tells you what to do, when to do it, and how to do it—giving step-by-step solutions to the design and application problems that engineers encounter daily. Containing some 1,000 calculation procedures accompanied by worked-out numerical examples, it also features 4,000 related calculation procedures.
287/341 Pub. Pr., \$27.50 Club Pr., \$19.95

ELECTRONICS DESIGNER'S HANDBOOK. Edited by L. J. Giacoletto. 2nd Ed. 2,344 pp., 1,685 illus. Now doubled in size and with 90% of its material new, this famous classic (first edition by Landee, Davis, Albrecht) has been thoroughly revised and updated to give you not only the how and the why of all your design work but also the how much of every design step you take!
231/494 Pub. Pr., \$52.50 Club Pr., \$39.50

DIGITAL INTEGRATED CIRCUITS AND OPERATIONAL AMPLIFIER AND OP-ELECTRONIC CIRCUIT DESIGN. Edited by B. Norris. 206 pp., 400 illus. Having this vast amount of case-tested data, proven shortcuts, worked-out circuit designs, and circuit diagrams handy saves you valuable time for your other, more vital, areas of creative design—and cuts down costs in all areas!
637/539 Pub. Pr., \$19.50 Club Pr., \$14.50

CIRCUITS FOR ELECTRONICS ENGINEERS. Edited by S. Weber. 396 pp., 346 circuits. This book is filled with the circuits you need in 51 areas—from amplifiers to voltage regulators—arranged in alphabetical order and grouped for easy finding. Use them as is or adapt them. Each has been tested and proved in action.
191/573 Pub. Pr., \$19.50 Club Pr., \$16.00

MICROCOMPUTER-BASED DESIGN. By J. P. Peatman. 604 pp., 400 illus. Do all your best day-to-day and supercreative designs around today's microcomputers with the specific "how-to" help here! Big new printing has more pages, lots more new material, including data on such "hot" third generation micros as Intel 8048/8748, Zilog Z80, and a first and valuable overview of the Motorola 6809!
491/380 Pub. Pr., \$24.50 Club Pr., \$17.50

SEMICONDUCTOR ELECTRONICS

DESIGN. By F. K. Manasse. 562 pp., illus. Today the microelectronics industry is going places faster than ever before. Are you going with it? To get and keep yourself completely up to date, you will do well to keep this volume nearby. Its chapters on design techniques are among the most complete and detailed ever published.
772/622 Pub. Pr., \$21.95 Club Pr., \$18.25

MICROPROCESSOR APPLICATIONS

MANUAL. By Motorola Semiconductor Products, Inc. 720 pp., illus. Here's every piece of info you need to use MPU's to simplify your board layouts, lower your hardware costs, save precious time, design better and faster, and verify your designs from the start! Overflowing with illustrations!
435/278 Pub. Pr., \$32.50 Club Pr., \$24.00

OPTOELECTRONIC APPLICATIONS MANUAL.

By Hewlett-Packard
286/051 Pub. Pr., \$22.50 Club Pr., \$16.50

DIGITAL COMPUTER ELECTRONICS.

By A. P. Malvino.
398/615 Pub. Pr., \$14.95 Club Pr., \$10.95

A USER'S HANDBOOK OF D/A AND A/D

CONVERTERS. By E. R. Hrusak.
767/149 Pub. Pr., \$24.95 Club Pr., \$18.50

HANDBOOK OF ENGINEERING FUNDAMENTALS.

3/a. By O. Eshbach & M. Souders.
769/842 Pub. Pr., \$31.50 Club Pr., \$24.95

COMPLETE GUIDE TO DIGITAL TEST EQUIPMENT.

By W. Buchsbaum.
772/068 Pub. Pr., \$14.95 Club Pr., \$10.50

BE SURE TO CONSIDER THESE IMPORTANT TITLES AS WELL:

DIFFERENTIAL EQUATIONS FOR ENGINEERS.

By T. M. Creese & R. M. Harsick.
135/10X Pub. Pr., \$17.50 Club Pr., \$13.50

APPROXIMATION METHODS FOR ELECTRONIC FILTER DESIGN.

By R. W. Daniels.
153/086 Pub. Pr., \$31.50 Club Pr., \$19.50

MANAGEMENT OF ENGINEERING PROJECTS.


2/a. By V. G. Hajek.
255/342 Pub. Pr., \$16.95 Club Pr., \$12.50

HANDBOOK OF COMPONENTS FOR ELECTRONICS.

By C. A. Harper.
266/824 Pub. Pr., \$39.50 Club Pr., \$28.50

ENGINEERING CIRCUIT ANALYSIS.

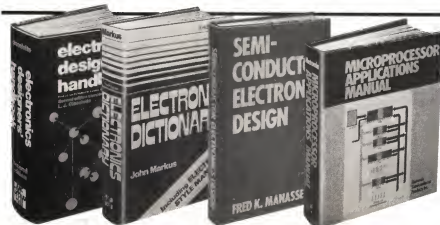3/a. By W. Hyatt & J. Kemmerly.
273/936 Pub. Pr., \$22.00 Club Pr., \$16.50



offer to new members of the and Control Engineers' Book Club

ELECTRONICS ENGINEER'S HANDBOOK. Editor-in-Chief, D. G. Fink. 2,104 pp., 2,028 illus. Huge in-avary sense, this instant-reference volume gives you every latest essential in the field. 2,100 formulas and equations, a 2,500-item bibliography, and every illustration you need to clarify all of modern electronics! 209/904 Pub. Pr., \$49.50 Club Pr., \$35.00

GUIDEBOOK OF ELECTRONIC CIRCUITS. By J. Markus. 1,018 pp., illus. Are you constantly on the lookout for circuits that will meet your needs? Here's a giant collection of them to use "as is" or to adapt to your own ideas. Complements with values. 404/453 Pub. Pr., \$33.50 Club Pr., \$25.00

PROFESSIONAL ENGINEERS' EXAMINATION QUESTIONS AND ANSWERS. By W. S. LaLonde, Jr. and W. J. Stack-Strakids. 3rd Ed. 601 pp., 276 illus. Over 500 questions and complete answers—suitable for all states—prepare you for passing your exams for the E.I.T. certificate and your P.E. license. 360/936 Pub. Pr., \$19.50 Club Pr., \$14.50

DESIGN TECHNIQUES FOR ELECTRONICS ENGINEERS. Electronics Book Series. By ELECTRONICS Magazine. 370 pp., illus. The whole gamut of complex techniques required when you're designing a circuit or system is explained and shown in the superb collection of the "best of the best" from Electronics magazine. 191/581 Pub. Pr., \$19.50 Club Pr., \$15.50

HANDBOOK FOR ELECTRONICS ENGINEERING TECHNICIANS. By M. Kaufman and A. H. Saidman. 520 pp., 695 illus. Rely on this technician's godsend for all your work with analog and digital integrated and discrete circuits. Here are the stiff brush-ups you want and the solutions to every possible problem. 334/013 Pub. Pr., \$23.50 Club Pr., \$16.50

MICROPROCESSORS & SMALL DIGITAL COMPUTER SYSTEMS FOR ENGINEERS & SCIENTISTS. By G.A. Korn. 390 pp. This exceptional book is your quick reference for expert advice on product selection, interfacing, and programming. Containing a huge variety of computer possibilities, system features, and costs, it's also a terrific tool for career updating. 353/670 Pub. Pr., \$27.50 Club Pr., \$18.95

ELECTRONICS DICTIONARY. Edited by John Markus. 4th Ed. 769 pp., 1,173 illus., 17,090 terms. With the new edition of this world-renowned dictionary you'll be able to quickly find the meaning and correct usage of any electronics term, no matter how obscure! 404/313 Pub. Pr., \$24.50 Club Pr., \$19.50

APPLIED ELECTROMAGNETICS. By M.A. Pionus. 615 pp., illus. A fascinating approach to theory through the use of totally up-to-date applications encountered in everyday situations. Covers solid-state electronics, physical electronics, linear and rotating machines, microwaves, and super-conductivity. 503/451 Pub. Pr., \$21.00 Club Pr., \$16.50

ELECTRONIC TROUBLESHOOTING, A Manual for Engineers and Technicians. By C.N. Harrick. 2nd Ed., 348 pp., illus. One of the best manuals ever published for engineers and technicians, this new edition moves you right along in practical steps from basics to more and more complex jobs. 784/639 Pub. Pr., \$16.95 Club Pr., \$14.25

MASTER OP-AMP APPLICATIONS HANDBOOK. By H.W. Fox. 467 pp., 320 illus. There's enough practical build-it information in this book to keep you breadboarding and experimenting and creating for years! It shows you how to put op amps to work in literally hundreds of different circuits, in hundreds of handworking applications. 784/477 Pub. Pr., \$16.95 Club Pr., \$13.50

any one
of these great
professional books
for \$1.89
only
values up
to \$52.50

Special \$1.89 bonus
book comes to you
with your first
club selection

ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB saves you both time and money!

Here is a professional book club designed to meet your on-the-job engineering needs by providing practical books in your field on a regular basis at below publisher prices. If you're missing out on important technical literature—if today's high cost of reading curbs the growth of your library—here's the solution to your problem.

The Electronics and Control Engineers' Book Club was organized for you, to provide an economical reading program that cannot fail to be of value. Administered by the McGraw-Hill Book Company, all books are chosen by qualified editors and consultants. Their understanding of the standards and values of the literature in your field guarantees the appropriateness of the selections.

How the club operates: Thirteen times a year you receive free of charge The Electronics and Control Engineers' Book Club Bulletin. This announces and describes the Club's featured book for that period as well as alternate selections available at special members' prices. If you want to examine the Club's featured selection, you do nothing. If you prefer one of the alternate selections—or if you want no book at all—you notify the Club by returning the card enclosed with each Bulletin.

As a Club member, you agree only to the purchase of four books (including your first selection) over a two-year period. Considering the many books published annually, there will surely be at least four you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

MAIL COUPON TODAY

ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB

P.O. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the two books indicated. I am to receive the bonus book at the introductory price of \$1.89 plus my first selection, plus tax, postage and handling. If not completely satisfied, I may return the books within 10 days and request that my membership be cancelled. If I keep the books, I agree to take a minimum of three additional books during the next two years at special Club prices (guaranteed 15% discount, often more). I will receive the Club Bulletin 13 times a year. If I want to examine the featured selection, I need take no action. It will be shipped automatically. If, however, I want an alternate selection—or no book at all—I simply notify the Club by returning the convenient card always enclosed. I will always have a minimum of ten days in which to return the card and you will credit my account fully. Including postage, if this is not the case. Membership in the Club is continuous but cancellable by me at any time after the four-book purchase requirement has been filled. This order subject to acceptance by McGraw-Hill. Orders from outside the continental U.S. must be prepaid. All prices subject to change without notice. Offer good for new members only. Postage and handling charges are added to all subsequent shipments.

WRITE BELOW:

Code No. of \$1.89 book

Code # of 1st selection

NAME

NAME

ADDRESS

CITY

STATE

ZIP

EXTRA SAVINGS: Remit in full with your order, plus any local and state tax, and McGraw-Hill will pay all regular postage and handling charges.

E33366

LETTERS

continued from page 17

Digital Micro Systems
Box 1212
Orem, UT 84057

Electronic Systems, Inc.
P.O. Box 212
Burlingame, CA 94010
(408) 374-7951

Micro Designs, Inc.
499 Embarcadero
Oakland, CA 94606
(415) 465-1861

Realistic Controls Corp.
404 W. 35th St.
Davenport, IA 52806
(800) 553-1863

Integrand
8474 Avenue 296
Visalia, CA 93277
(205) 733-9288

Vanden Box Data Products
P.O. Box 2507
Santa Maria, CA 93454
(805) 937-7951

PolyMorphic Systems
460 Ward Drive

Santa Barbara, CA 93111
(805) 967-0888

I realize this list isn't quite complete, but I thought you should update your list. I would like to add that Vandenberg Data Products has the only 16K RAM board available for the S-100 bus for \$330, fully static (kit) and rated at 250 μ s, quite suitable for a Z-80. Anybody else's static RAM costs roughly double that. I am currently running 32K of their memory and am thinking hard about another 16K. All components in my system (except the TV) were built from kits. MARCUS S. LEWIS
Omaha, NE

S-100 BUS ADDITIONS

I enjoyed the S-100 article (April 1978 Issue, page 48) and S-100 bus listing. In the listing you asked to be informed of other S-100 products not listed.

CGRS Microtech manufactures three boards for the S-100:

1. The 6502 MPU Board—to our knowledge, this is the only S-100/6502 board for the S-100. It has been in production for 18 months and is working very well.

2. The T.I.M. II I/O Board—this is a "system monitor board" that provides ROM, RAM, and parallel and serial I/O ports.

3. The Multi-I/O Board—provides I/O for the Persol 1070 floppy-disc controller card as well as 4K of ROM, two parallel ports and two serial ports.

WILLIAM M. GOBLE
CGRS Microtech
P.O. Box 368
Southampton, PA
(215) 757-0284

WHERE ARE THE ELECTRONIC DESIGNERS?

I wish to respond to your June 1978 editorial entitled "Where Have All The Designers Gone?"

Electronic designers have always been wiring up "black boxes" to form new devices. What are resistors, transistors, capacitors, inductors, transformers, etc., but "black boxes"? A black box is simply a device with known characteristics.

The designer today uses IC's to reduce the amount of drudgery and cost in his designs. How would you like to redesign the NAND gate hundreds of times for each digital project? If every general-purpose IC (i.e., gates, op-amps, latches, etc.) had to be built from discrete components, a digital clock, stereo, CB radio and any other electronic device would cost much more than it now does.

In answer to the question, "What does an electronic designer do?" I think I am qualified to respond since I am an electronics engineer with IBM. My job is to design, oversee construction and debug electronic circuits. It also requires taking sometimes as many as 100 separate inputs and creating the proper responses at the proper time. I use digital IC's to create these circuits and do consider each circuit to be a new one.

This is designing, just as engineers in the 1950's designed using only transistors, tubes and other less-complicated devices.

I don't think it has slowed either the development or development time of new devices; it has simply made it economically continued on page 24



PROFESSIONAL TOOL CASE

Interchangeable Screwdrivers, Nutdrivers, Other Tools and Handles—

99-1, 1/4, & 3/8 Handles (regular, straight and T-bar)
99-2 Square Adapter
99-3 & X10 Extension
99-4 & 30 Reamers
99-5 Anti-Rattle
99-6, 7, 20, 21, & 211 Shortened Screw Blades
99-820, 821, & 822 Phillips Screw Blades
Pliers, Wrenches, Cutters
401 Straight Nose Pliers
402 Adjustable Wrench (8")
80-20 Magnet Ring Joint Pliers (8")
80-21 Long Nose Pliers (8-1/2")
80-22 Utility Pliers (7")

80-23 & 80-24 Diagonal Pliers (6" & 8")
81-20 Chain Nose Pliers (8-1/2")
80-25 Chain Nose Pliers (8")
80-26 Chain Nose Pliers (8")
80-27 Wire Stripper/Cutter
80-28 Electrician's Knife
Sets & Kits
80-40-45 Hex Socket Screwdriver: Blades & Handles
80-46-50 Hex Socket Multiple Spline Screwdriver: Blades & Handles
80-50 Hex Driver
80-51 Compact Convertible Nutdrivers
80-52 Offset Pocket Screwdrivers

80-53 Combination Screwdriver/Nutdriver: Tools
Screwdrivers
Screwdriver
R-144 R-3223
R-148 R-3226
R-151 R-368
R-154 R-3711
R-214 R-5151
R-216 R-5156
EX-101 XST-101
XST-102 XST-103
R-18 & 19 (.038 & .036)
H-6, 8, 10, 11, 12, 14, 16, 18
Hollow Shaft
80 & 100 Magnets

MODEL TC-100

Larger, more elaborate of the two cases. Contains 81 individual tools, 18 Series 99 interchangeable screwdriver/nutdriver blades and handles, and 5 specialized screwdriver/nutdriver kits, as listed. Case (16-1/2" x 12-1/2" x 6-3/4") covered with attractive, tough, chemically resistant, weather-resistant, removable three-piece, vinyl pattern and tear resistant with elastic loop and transparent plastic pocket tool holders. Solid brass tools, sockets, and hardware. Padded handle. Partitioned bottom compartment for other tools.

CHRISTMAS SPECIAL

\$269.95

Shipping
not included.

Xcelite List price \$485.
Offer ends Feb. 28, 1979

THE TEST EQUIPMENT SPECIALISTS

TOLL FREE HOT LINE
800-223-0474

54 West 45 Street New York, N.Y. 10036 212-687-2224



**ADVANCE
ELECTRONICS**

NTS trains you on tomorrow's equipment. Today.

Microcomputers, digital systems and more...
from the first name in home study.



Now NTS training programs include an even wider choice of solid-state digital equipment than ever before offered in any electronic home study course. Advanced NTS/Heath digital color TV (25" diagonal with optional programming capability), NTS/Heath digital computer, digital test equipment, digital stereo receiver (70 watts per channel) plus much more state-of-the-art equipment to make your training exciting and relevant. Learn servicing and maintenance easily with step-by-step Project Method lessons and kits.

An all-new full color catalog shows you exactly what each of the fourteen courses cover, and every piece of equipment you receive.

Send for it today and see for yourself what's really happening in electronics training technology at NTS. It's free. Just send the coupon.

**NO OBLIGATION. NO SALESMAN WILL CALL.
APPROVED FOR VETERAN TRAINING.**

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 South Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS Dept. 206-128
4000 South Figueroa Street, Los Angeles, California 90037

Please send FREE Color Catalog and Sample Lesson.

- | | |
|---|---|
| <input type="checkbox"/> Color TV Servicing | <input type="checkbox"/> Electronics Technology |
| <input type="checkbox"/> B & W TV and Radio Servicing | <input type="checkbox"/> Audio Electronics Servicing |
| <input type="checkbox"/> FCC License Course | <input type="checkbox"/> Digital Electronics |
| <input type="checkbox"/> Electronic Communications | <input type="checkbox"/> MicroComputers/MicroProcessors |

Name

Address

Apartment Number Age

City

State Zip

- ☐ Check if interested in G.I. Bill information.
☐ Check if interested ONLY in classroom training in Los Angeles.

LETTERS

continued from page 22

feasible to develop more complicated products. For example, with IBM's Series III copier (yes, I know I'm biased), would so many functions have been possible without IC's? I think not.

Finally, an electronic designer is someone who extracts information from electrical signals (inputs) with electronic components, and who controls (via outputs) other devices with that information. The process of creating the device between the inputs and outputs (which, by the way, are usually defined before the design is begun) is electronic design.

DENNIS A. ROWE
Boulder, CO

With respect to your June 1978 editorial, I think that persons who use and apply integrated circuits are, indeed, designers. They may be using available devices to design something that is totally new, unique, and perhaps useful, too. I think that the IC has freed us to concentrate upon the task at hand without having to craft the tools that are necessary to accomplish it. Remember the days of the tube-based op-amp, the tube-based counters and flip-flops, etc.? They are gone, luckily.

If IC users aren't really designers, then neither are the solid-state physicists and semiconductor engineers, since all they are doing is moving around the same atoms in different ways. The silicon, gallium and

arsenic remain the same . . . the designers just do different things with them.
JONATHAN TITUS

In reply to your June editorial, I feel that the designer is still with us.

It seems to me that the designer's role has taken three different paths—on one path he devises all the IC's we use. On another path, he is a systems designer, responsible for the design of the complete complex system. And the third path is that of designing the new instrumentation used to service complex devices.

Today, the engineer can take the IC's and connect them together to make a circuit or simple electronic device.

I really don't envy the job of the instrumentation designer for he has to design instruments that are to be used repeatedly by people not in the electronics field. For example, automotive mechanics are finding more and more electronics in our modern cars. They cannot just exchange one module for another; because of increasing complexity, they must use instruments to troubleshoot the entire system to find the malfunction.

Twenty years ago, when I graduated from electronics school, we did not have very many test instruments. We could troubleshoot and repair just about everything electronic with an OS-8 oscilloscope, TS-352 VOM, TV-7 tube tester and BC-221 frequency meter.

I would hate to troubleshoot and repair

some of today's complex electronics systems with those Stone Age instruments. If you look at some modern instrumentation, you can see the designer has been busy. And there is always something new being released to make our jobs easier.

I feel that economics, not the integrated circuit, has slowed down the development of new electronic devices. The question is now when a new product is developed, is it to be made inexpensive enough to be disposable when it malfunctions or is it to be made repairable? And who will repair it? There are a few products on the market that are disposable because of their low cost—radios, LED watches and calculators. But now I feel that many manufacturers are taking a wait-and-see attitude before producing any more low-cost products.

JERRY W. CLARK
New Richmond, IN

HOME COMPUTERS

I have a hobby computer. I have not yet and probably never will wire it up to "run the house." Most household applications can be controlled just fine with a motor and cam for several operations per day. If I did "control the house" with my computer, I couldn't experiment with new programs since I might erase the household program.

What I really do with my computer is write game programs. After spending many hours writing and debugging the program, I

Vector

PLUGBORDS OFFER MORE. . .

- Unique time saving bus patterns
- Press-fit wrap-posts & solder terminals
- Many board and contact sizes



- Easy to wire hole and pad patterns
- .042" diameter holes on .1" grid
- P.C. plug or flexcable connections

4493-1 ANY DIP, \$16.95 Accepts all DIPs. Offset power and ground planes. 36/72 contacts. 4.5" x 9.6" (6.5" also available). 22/44 contacts also offered in both sizes.

8804 ANY DIP, \$21.95 Accepts all DIPs. Offset power and ground planes. 50/100 contacts spaced .125". S-100 size.*

4112-5 PAD BOARD, \$12.23. Pad per 3 holes. Ground plane on back-side. 4.5" x 4.5" or 4.5" x 6.5" or 4.5" x 9.6". 22/44 contacts spaced 0.156".

8802-1 PAD BOARD, \$21.95. Pad per 2 holes, each side, peripheral buses. 50/100 contacts spaced at .125". S-100 size.*

8801 PAD BOARD, \$19.95. Pad per each hole, each side, peripheral buses. 50/100 contacts at .125". S-100 size.*


8801-1, \$14.95. No pads — just holes. 50/100 contacts at .125". S-100 size.

*S-100 size is 5.3" high by 10" wide.

VECTOR ELECTRONIC COMPANY
12460 Gladstone Avenue
Sylmar, California 91342

Phone (213) 365-9661
TWX (910) 496-1539

Send for new data.

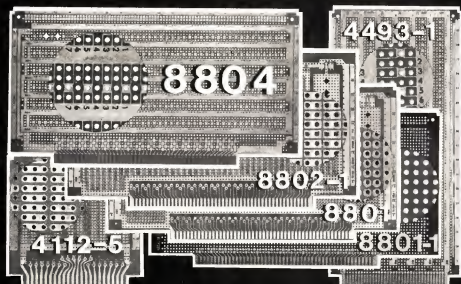

FULL LINE OF SUPPORTING PRODUCTS: Card cages and enclosures for all Plugboards, mating receptacles, interconnect products.

Prices subject to change without notice.

Vector P184 Slot-N-Wrap

Patented Vector P184 Tool is three times faster for inter-connecting wrap-post designs. \$29.95.

Our toll-free number which can be used by customers outside of California is 800-423-5659

CIRCLE 68 ON FREE INFORMATION CARD

play the game a couple of times and start writing a new program.

I agree with you that the "Home Computer" is nonsense. The only application I might have for it is to balance my checkbook. Even then I would pull out my pocket calculator.

Many people ask, "Well then, what good is your computer?" I guess the best answer is, "What good is your home TV set?"

E. MORRIS
Midland, MI

I do not own a hobby computer. I do have three hi-fi sets, a VCR, model railroad, darkroom and studio to support; so when I received several estimates of the cost of a computer system (\$8000) with enough memory and "crunch" to cross-reference my collection of 1000 LP records and songs into several categories, I bailed out.

I do know about computers since we use one to roll our film and tapes at the TV studio I work at. I also can remember anytime, anywhere that next month the real estate tax is due. I know how much I have in several savings and checking accounts. I don't need an expensive computer to remind me (if I happen to be near it), but if the price were \$200 for the system described above with a cassette, easily interchangeable programs, a video (or TV) monitor or hardcopy at additional cost, I might buy it.

I guess what I mean is I don't like to "play games" just for the sake of playing games, and if it takes possibly more time to program the computer to do a job than it might take to do the job the usual way, why bother? But if the cost of computers drops as it did with small calculators, we will have a different ball game.

DICK WARTENBERG
Brooklyn, NY

DARKROOM TIMER

With respect to my article in the July and August 1978 issues ("Build A Digital Timer for Your Darkroom"), the accuracy of the schematic was excellent. However, there were six errors that must be noted:

1. In the table shown in Fig. 3 that lists the power and ground connections for the IC's, I wrongly listed pins 14 and 7 as power and ground for IC13. The correct pins are 16 for power and 8 for ground.

2. In Fig. 3 again, an LED is missing between pins 10 and 1 of DIS4, but this is an internal LED contained within DIS4 as are the others.

3. The point at which S4 connects to the main PC board should be labeled "D."

4. The Parts List did not have numbers for the transistors. They can be any NPN silicon transistors whose beta is between 50 and 150, such as 2N2222, 2N957, etc.

5. The part number given for S1-S3 is incompatible with the PC board/front panel combination. The correct UID Electronics part numbers are: S1: RSW-0622-SD-BB-S-B1-BK; S2 and S3: RSW-0022-SD-BB-S-B1-BK.

6. One of the key cap part numbers should be 42-3100-03, not 40-3100-03. The "42" indicates double-width, which is what the "0" key cap is.

RAYMOND G. KOSTANTY


R-E

Q. Where should you start in your search for better sound?

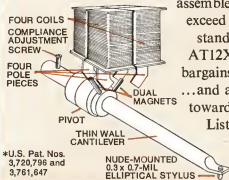A. At the beginning. With a new Audio-Technica Dual Magnet™ stereo phono cartridge.

Our AT12XE, for instance. Tracking smoothly at 1 to 1-3/4 grams, depending on your record player. Delivers smooth, peak-free response from 15 Hz to 28,000 Hz (better than most speakers available). With a minimum 24 dB of honest stereo separation at important mid frequencies, and 18 dB minimum separation even at the standard high-frequency 10 kHz test point. At just \$65 suggested list price, it's an outstanding value in these days of inflated prices.

Audio-Technica cartridges have been widely-acclaimed for their great sound, and for good reason. Our unique, patented* Dual Magnet construction provides a *separate* magnetic system for *each* stereo channel. A concept that insures excellent stereo separation, while lowering magnet mass. And the AT12XE features a tiny 0.3 x 0.7-mil nude-mounted elliptical diamond stylus on a thin-wall cantilever to further reduce moving mass where it counts. Each cartridge is individually



assembled and tested to meet or exceed our rigid performance standards. As a result, the AT12XE is one of the great bargains of modern technology...and a significant head start toward more beautiful sound.

Listen carefully at your Audio-Technica dealer's today.



audio-technica
INNOVATION □ PRECISION □ INTEGRITY

AUDIO-TECHNICA U.S., INC., Dept. 128E, 33 Shawnee Avenue, Fairlawn, Ohio 44133
In Canada: Superior Electronics, Inc.

CIRCLE 5 ON FREE INFORMATION CARD

equipment reports

Super Sleuth Descrambler



CIRCLE 118 ON FREE INFORMATION CARD

AS MORE AND MORE LAW-ENFORCEMENT CHANNELS are being monitored by unauthorized listeners using scanners, many agencies have attempted to improve voice security by using "scramblers." A scrambler is an audio frequency inverter. High frequencies become low

and low frequencies, high; the result is unintelligible.

The *Super Sleuth* descrambler is designed to reinvert audio signals to normal. It plugs into the external speaker jack of a scanner and is usually left switched to the normal mode. When conventional transmissions are received, the descrambler's internal speaker is connected directly to the scanner's speaker jack, and the descrambler circuitry is off. When a scrambled message is received, the *Super Sleuth* is switched to the scrambled mode, and an internal ring-demodulator circuit rearranges the inverted speech to normal speech.

The *Super Sleuth* is entirely self-contained, including eight internal AA batteries (not provided), and its three adjustable decoding controls are switch-selectable.

Many law-enforcement agencies use more than one audio code, switching codes at different times; the three switch-selectable controls allows the listener to individually adjust each control to correspond to a given code, and then leave it set so that rapid switch-selectable

decoding of the scrambled message is possible the next time it is encountered.

A FINE TUNE control allows an occasional adjustment of the audio for natural voice quality (however, it is seldom needed).

Since descramblers (and scramblers) inject an audio signal into their circuitry, that signal should be removed from the resultant audio output so that it doesn't cause annoying interference. The *Super Sleuth* has a CARRIER/BALANCE null control knob to accomplish this.

Finally, the volume control permits you to adjust the audio output to a comfortable listening level.

The *Super Sleuth* looks impressive, functions well and its audio quality is very natural. Although the top-mounted internal speaker would be inconvenient for under-dash mobile mounting, most listeners would probably use the unit next to a scanner in the home or office.

A 741 op-amp audio oscillator injects an
continued on page 32

CLIP AND STRIP



Model CAS-130

\$198

- CUTS AWG 30 WIRE TO DESIRED LENGTH
- STRIPS 1" OF INSULATION

MINIMUM BILLING \$25.00
ADD SHIPPING CHARGE \$2.00
NEW YORK STATE RESIDENTS
ADD APPLICABLE TAX



OK MACHINE & TOOL CORPORATION
3455 Conner St., Bronx, N.Y. 10475 • (212) 994-6600 • TELEX 125091

CIRCLE 20 ON FREE INFORMATION CARD

sophisticated soldering of space-age heat- & voltage-sensitive components

DEMANDS THE RELIABILITY OF

Weller® controlled output irons and stations

Modern, ultra-sophisticated electronic technology calls for totally dependable soldered connections. This requires not only sensing the soldering tip temperature, but applying and removing wattage at precisely the right moment to control the selected operating range of the iron.

That, in a nutshell, is what the Weller family of Controlled Output Soldering Equipment is all about. And that explains how it can avoid defects in soldered connections and damage to heat- and voltage-sensitive components and substrates, as well as deteriorating over-exposure from needlessly long soldering contact. In other words, dependence on the human element is eliminated. But there are other significant benefits from the Weller controlled output soldering technique. Soldering tips last longer. Much longer. And power consumption is less than that of uncontrolled irons.

What's the secret of Weller's controlled output? It's really no longer a secret. Today it's a time-proved principle: Closed loop, low voltage circuitry and a ferromagnetic sensor control temperature at a pre-selected range. Sounds simple? It is. That's why it's totally reliable!

Ready to meet the whole Weller Temperature Controlled family? This way, please for a brief introduction to the members presented below.

LINE VOLTAGE PORTABLE IRONS

Models W60 and W100: 60 and 100 watts. Operate from 120V outlet. Interchangeable 600, 700, and 800°F tips, grounded and non-grounded, available in 9 sizes. Optional de-soldering adaptor and non-heat-sinking tool holders.

COMPLETE SOLDERING AND DE-SOLDERING STATIONS

Include iron holder, tip-wiping sponge and receptacle, power on-off switch with indicator light, stepdown transformer dropping power to 24V in heating element, positive tip-grounding to prevent build-up of electrostatic charges that injure delicate components, non-burnable silicone rubber cord, and dozens of other Weller quality features.

Model WTCPN: Plug-in pencil soldering iron with comfort-cool heat shield, 17 available styles and sizes of interchangeable tips for 600, 700, and 800°F temperature control, integral tip storage tray. 120V, 60Hz, 60W. Optional de-soldering adaptor.

Model MP: For precision soldering of miniaturized electronics, especially PC work. Plug-in, true pencil shape 650 or 750°F iron with 1/8" diam. tips available in 8 sizes and styles. 120V, 60/40Hz, 22W.

Model DS100: De-soldering and re-soldering unit designed for PC board repair and re-work lines. Utilizes interchangeable 600, 700, and 800°F soldering tips and interchangeable 700 or 800°F de-soldering heads. Complete with footswitch, twin safety tool holder, vacuum adjustment gauge, and cleanable, replaceable see-thru solder collector. 8 de-soldering tiplet sizes and 17 soldering tip styles (in 3 temps) available. Operates from factory air and line voltage.

Yes, of course, the entire family is UL listed and OSHA compliant. Now that you've been introduced, any leading electronic distributor will display the units and fill you in on all the features. For technical information and consultation, write the factory on your company letterhead.



The Cooper Group
Electronics Division

WELLER® · WISS® · XCELITE®

P.O. BOX 728 APEX NORTH CAROLINA 27502 919-362-7511
FURNISHES THE MOST INFORMATIONAL ADVERTISING

At CIE, you get electronics career training from specialists.

If you're interested in learning how to fix air conditioners, service cars or install heating systems – talk to some other school. But if you're serious about electronics, come to CIE – The Electronics Specialists.

John E. Cunningham

**Special Projects Director
Cleveland Institute of Electronics**



My father always told me that there were certain advantages to putting all your eggs in one basket. "John," he said, "learn to do one important thing better than anyone else, and you'll always be in demand."

I believe he was right. Today is the age of specialization. And I think that's a very good thing.

Consider doctors. You wouldn't expect your family doctor to perform open heart surgery or your dentist to set a broken bone, either. Would you?

For these things, you'd want a specialist, and you'd trust him. Because you'd know if he weren't any good, he'd be out of business.

Why trust your education and career future to anything less than a specialist?

You shouldn't. And you certainly don't have to.

FACT: CIE is the largest independent home study school in the world that specializes exclusively in electronics.

We have to be good at it because we put all our eggs in one basket: electronics. If we hadn't done a good job, we'd have closed our doors long ago.

Specialists aren't for everyone.

I'll tell it to you straight. If you think electronics would make a nice hobby, check with other schools.

But if you think you have the cool—and want the training it takes—to make sure that a sound blackout during a prime time TV show will be corrected in seconds—then answer this ad. You'll probably find CIE has a course that's just right for you!

At CIE, we combine theory and practice. You learn the best of both.

Learning electronics is a lot more than memorizing a laundry list of facts about circuits and transistors. Electronics is interesting because it's based on some fairly recent scientific discoveries. It's built on ideas. So, look for a program that starts with ideas—and builds on them.

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson uses world-famous "programmed learning" methods to teach you important principles. You explore them, master them completely... before you start to apply them!

But beyond theory, some of our courses come fully equipped with the electronics gear to actually let you perform hundreds of checking, testing and analyzing projects.

In fact, depending on the course you take, you'll do most of the basic things professionals do every day—things like servicing a beauty of a Zenith color TV set... or studying a variety of screen display patterns with the help of a color bar generator.

Plus there's a professional quality oscilloscope you build and use to "see" and "read" the characteristic waveform patterns of electronic equipment.

You work with experienced specialists.

When you send us a completed lesson, you can be sure it will be reviewed and graded by a trained electronics instructor, backed by a team of technical specialists. If you need specialized help, you get it fast... in writing from the faculty specialists best qualified to handle your question.

People who have known us a long time, think of us as the "FCC License School."

We don't mind. We have a fine record of preparing people to take... and pass... the government-administered FCC License exams. In fact, in continuing surveys nearly 4 out of 5 of our graduates who take

the exams get their Licenses. You may already know that an FCC License is needed for some careers in electronics—and it can be a valuable credential anytime.

Find out more! Mail this card for your FREE CATALOG today!

If the card is gone, cut out and mail the coupon.

I'll send you a copy of CIE's FREE school catalog, along with a complete package of independent home study information.

For your convenience, I'll try to arrange for a CIE representative to contact you to answer any questions you may have.

Remember, if you are serious about learning electronics... or building upon your present skills, your best bet is to go with the electronics specialists—CIE. Mail the card or coupon today or write CIE (and mention the name and date of this magazine), 1776 East 17th Street, Cleveland, Ohio 44114.



Patterns shown on TV and oscilloscope screens are simulated.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

☐ **YES...** John, I want to learn from the specialists in electronics—CIE. Send me my FREE CIE school catalog—including details about troubleshooting courses—plus my FREE package of home study information.

RE-50

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G.I. Bill information: ☐ Veteran ☐ Active Duty

Mail today!

EQUIPMENT REPORTS

continued from page 27

adjustable tone into a diode-bridge ring modulator (mixer), where it heterodynes with the inverted audio from the scanner's speaker-jack output. The difference frequency (in this case, normal unscrambled speech) is fed to an LM380N amplifier IC for up to two-watts audio output.

The *Super Sleuth* weighs only 2 lb. and measures 10 W × 3 1/4 H × 5 inches D. Its power drain is 12 VDC at 25 to 300 mA depending upon audio-output level. The unit is available for \$79.95 from Krystal Kits, Box 445, Bentonville, AR 72712. **R-E**

Continental Specialties LP-2 and DP-2 Logic Probes

ALTHOUGH USING AN OSCILLOSCOPE AND expensive logic analyzers to solve knotty troubleshooting problems is really best, logic probes save time in most situations. Using very few controls, the *models LP-2 and DP-1* probes manufactured by Continental Specialties offer a combination of simple "go, no-go" testing and a high degree of diagnostic sophistication.

The *model LP-2* logic probe is a hand-held instrument that uses three LED indicators to display logic levels and pulse transitions via a dual-threshold window comparator and bipolar edge detector. The *model LP-2* probe is a less expensive version of the *model DP-1*; it has reduced frequency response, higher input im-

pedance, and it lacks a pulse-memory feature.

In the *model LP-2*, a single switch selects either DTL/TTL or CMOS/HTL levels. For static tests, the upper LED illuminates when the voltage at the probe tip is within the selected logic family's high-level range. The TTL and DTL logic 1 threshold is 2.25 volts \pm 0.15 volt, and for CMOS and HTL, the threshold is 70% of the supply (V_{cc}) or higher. Similarly, the lower LED indicates logic levels within the low range. Logic 0 levels are 0.8 volt \pm 0.1 volt for TTL/DTL, and 30% or less for CMOS/TTL. No LED illumination means there is an open circuit. Observing LED's near the probe tip is much simpler and less tiring than reading a voltmeter or oscilloscope screen, and then having to mentally translate that reading to

1 to 0 logic-level transition. A repetitive signal causes the indicator to illuminate constantly with an intensity that depends on duty cycle and frequency. Duty cycle is determined by observing the upper and lower LED's when the pulse light is lit. For example, if the upper LED illuminates, the signal is high most of the time and therefore consists of negative-going pulses. If both the upper and lower LED's have equal intensity, the duty cycle approaches 50% (or a squarewave).

Signals greater than 10 Hz but less than 100 kHz cause the LED to flash at a 10-Hz rate determined by the probe's 0.1-second pulse stretcher. With signals greater than 100 kHz and near 50% duty cycle, only the pulse LED is illuminated. The upper or lower LED's light as the waveform duty cycle deviates from symmetrical squarewave pulses at the higher frequencies.

The *model LP-2* operates with pulses as narrow as 300 ns and a maximum frequency of 1.5 MHz. Overload protection is effective up to 50 volts DC, or 117 volts AC, for 15 seconds. To use the probe, power must be provided through black and red clip leads that are connected to the power source supplying the circuit under test. The probe's drain is 30 mA at 5 volts and 40 mA at 15 volts; and the input impedance is 300,000 ohms.

Several accessories are available, including a 2.5-inch probe tip, hooks and adapters, and ground clips. The *model LP-2* can be used for troubleshooting an inoperative divider chain by quickly finding the defective binary stage. It could also be useful to determine the static and pulse logic conditions on IC terminals. Using this probe to examine a microprocessor's ad-



CIRCLE 119 ON FREE INFORMATION CARD

acceptable or abnormal limits.

The pulse indicator flashes for 0.1 second every time the input signal makes a 0 to 1, or a

Now! RCA offers you three time and money-saving options in Color TV Test Jigs.



dress leads could help pinpoint a grounded bus run when compared with the other active bus lines.



CIRCLE 120 ON FREE INFORMATION CARD

The *model DP-1* is a digital pulser probe with tristate output. It resembles the *model LP-2* physically, except it has only one LED pulse indicator plus a pulse-control pushbutton. A TTL/CMOS switch chooses output logic levels. The generator produces a single output pulse for each pushbutton operation. Depressing the pushbutton transmits a 100 pulse-per-second pulse train. Depending on the present logic level of the circuit area being probed, this produces differently formed logic pulses. If the probe senses a low logic level, it generates a positive-going pulse in an attempt to switch the logic-level state high. Conversely, if the logic level is high, the probe generates narrow negative-going pulses. Connecting the

probe to a variable-state point, such as a cross-connected feedback lead of a gate-wired flip-flop, generates a 50% duty cycle (continuous waveform).

In the TTL mode, the *model DP-1* produces a 1.5- μ s pulse with 100-ns risetime, and 500-ns storage and falltimes with a single TTL load. The storage and falltimes decrease with increased loading. The probe drives outputs as well as inputs, as long as the combined load is within the probe's 100-mA source and heat-sink capability.

The CMOS mode produces wider pulses for the higher-impedance (and generally slower) logic family. Pulse width is 10 μ s with a risetime under 100 ns, 8- μ s storage and falltimes with a 100K load, and sink and load capacity of 50 mA.

In both TTL and CMOS, the probe output is current-limited and generates continuous safety pulses into a short circuit. The LED indicator displays pulse-output states by flashing once for single pulse operation, and by constant illumination for continuous pulse-output trains.

If used with other logic probes such as the *model LP-2* or with a logic monitor that simultaneously displays all IC outputs, the *model DP-1* can test various types of logic devices. The probe is very useful in checking circuits that are only occasionally, or never activated. Using the logic pulser, these circuits can be activated repeatedly without elaborate test equipment and without disconnecting any auxiliary logic.

The *model DP-1* comes with a plug-in ground clip lead and the accessories that are available for the *model LP-2*. The output

impedance is greater than 300,000 ohms when the probe is in the open-output mode. And similar to the *model LP-2*, power is supplied to the *model LP-1* via color-coded clip leads, with less than 30 mA consumption.

The *model LP-2* sells for \$24.95 and the *model DP-1*, \$74.95. They are both available from Continental Specialties Corporation, 70 Fulton Terrace, P.O. Box 1942, New Haven, CT 06509.

R-E

Christmas Seals



Fight Lung Disease

Space contributed by the publisher as a public service

10J106AX



With the new RCA 10J106A Color TV Test Jig you can troubleshoot a TV chassis without bringing the cabinet and picture tube into the shop. The 10J106A helps you isolate picture tube or chassis malfunctions quickly, and without disturbing your customer's picture-tube alignment.

The 10J106A features a 19-inch shielded picture tube; built-in high voltage meter calibrated to 35 kV; two unique front-panel switches for easy changing of yoke impedances; and a built-in speaker. Yoke, picture tube socket, and high-voltage extension cables are supplied, plus a Set-Up Index and instruction book. With the 10J106A you can service thousands of sets whether tube, hybrid or solid-state — including Precision-in-Line types.


The new RCA 10J106AX Color TV Test Jig is exactly the same as the 10J106A except that it comes without a picture tube for those who prefer the economy of installing their own tube.

The RCA 10J107 Color TV Test Jig Adapter modernizes most older test jigs to perform like the 10J106A. And, if you're a do-it-yourselfer, you can build your own jig from a salvaged TV receiver.


See your RCA Distributor for all the details about which option suits you best. Or contact RCA Distributor and Special Products Division, Deptford, NJ 08096.

RCA Color TV
Test Jig

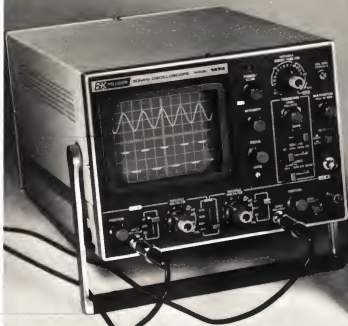Performance and Price... there's no tradeoff in B&K-PRECISION scopes.



Model 1474 \$999 including probes

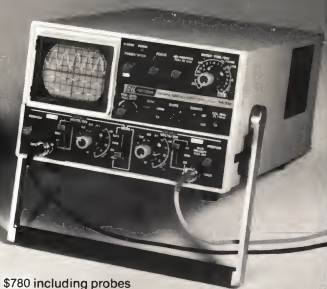

Model 1432 \$780 including probes

For field or lab work, Dynascan has a quality scope to fit your needs. B&K-PRECISION has taken a no-nonsense, cost-effective approach to oscilloscope design. Our scopes are rugged dependable instruments, designed to match the features and performance of far more expensive scopes, without matching their high prices. Typical of this approach is our Model 1474 30MHz dual-trace lab scope and our new Model 1432 15MHz portable dual-trace scope.



The B&K-PRECISION Model 1474 is the most cost-effective dual-trace scope available. No compromise features include a built-in signal-delay line, 5mV/cm sensitivity, switchable high- and low-pass triggering filters and a TTL compatible Z-axis input. Vertical response is typically down only -6dB at 49MHz. The 1474 is excellent for microprocessor work, as signal delay and the 30MHz minimum bandwidth allow you to examine short pulse waveforms.



The new Model 1432 portable dual-trace scope is one of our best values. This compact portable offers optional rechargeable battery pack and full lab-scope features. An automatic battery charger is built-in as a standard feature. Sensitivity is 2mV/division over a DC to 15MHz range. Bandwidth response is typically down only -6dB at 25MHz. Special features include algebraic addition and subtraction of two input signals, 19 calibrated sweep ranges and front-panel X-Y operation.

B&K PRECISION

DYNASCAN CORPORATION

6460 West Cortland Street, Chicago, Illinois 60635 • 312 / 889-9087

In Canada: Atlas Electronics, Ontario • Int'l. Sales: Empire Exporters, Inc., 270 Newtown Road, Plainville, L.I., NY 11603

Off-the-shelf delivery is another of our features, and it's the one you can take advantage of first. We're so sure that B&K-PRECISION scopes will fill your needs, that we can offer a no-obligation, ten-day free trial. Contact your local B&K-PRECISION distributor for immediate delivery or a demonstration.

BUILD THIS

SOLAR CONTROLLER

During the present energy crisis, the sun is in the running as the most viable alternate energy source. Here's how basic electronics can be adapted to solar heating in home and industry.

RODNEY A. KREUTER



SOLAR ENERGY, IT SEEMS, HAS BECOME almost a universal interest. Companies offering solar collectors and associated hardware are springing up like glitches on a TTL breadboard. However, most companies sell complete systems and most "do-it-yourself" magazines concentrate on collectors or storage system. Very little information seems to be available concerning the instrumentation or control portion of the systems.

This article attempts to proceed one step further by providing an understanding of a simple instrumentation and control system. It is not meant to be a blow-by-blow construction guide because no two solar systems are quite the same. It is hoped that it will enable you to design a system that will meet your special needs.

Hot-water preheater

A good way to get started in solar energy is with a solar hot-water preheater. A substantial amount of the average utility bill goes to feed standard preheaters. Another advantage of a solar preheater is that the payback time is not too great and the cash outlay to get started is within reason.

A preheater is a rather straightforward device. All it does is warm up the cold-water inlet to an existing hot-water tank

so that the tank itself won't need as much energy to warm the water to the required temperature. (Note the phrase "as much.") A small solar collector in a less-than-ideal climate will not supply all your needs; it will, however, help save a great deal of energy.

Figure 1 is a diagram of a hot-water preheater system. Basically, what happens is that the sun warms a water-anti-freeze solution in loop 1. The pump sends the warmed solution around from the collector to a storage tank that is filled with colored water. (Colored water can be used to warn of leaks in the system.) The water in the storage tank heats up and, if the tank is well insulated, will stay warm for quite some time.

When cold water enters into loop 2, it gains heat from the storage tank and enters the hot-water heater. If the system has been well designed, the water will need just a little more energy to bring it to the necessary temperature.

The system sounds simple enough, doesn't it? Well, it has a few flaws! The sun will warm the collectors only if there is sufficient radiant energy. The storage tank will only absorb heat from loop 1 if loop 1 is warmer than the water in the storage tank. Loop 2 will be warmed only if the tank is warmer than the cold-water

inlet and the hot water tank isn't full. If you don't know what the temperature of each component is, you shouldn't waste the energy used by the pump. This brings us to the LM3911.

Temperature transducers

National Semiconductor's LM3911 and the LX5600 are temperature transducers; they provide an answer to most of our temperature-measuring problems. The output of the sensors is 10 mV-per-degree Kelvin. Don't let the word Kelvin concern you; the output can be modified to read any temperature scale, but for a one-time system, the Kelvin scale is as good as any other scale. If you must convert the formula, it is: $^{\circ}\text{C} = ^{\circ}\text{K} + 273$.

The working temperature of the LM3911 is -25°C to 85°C (-13°F to 185°F); while the LX5600 has a range of -55°C to 125°C (-67°F to 257°F). Except for their range and cost, the two devices are similar.

The operation of the transducers is quite simple: Two diodes operated at two different current levels produce a voltage difference between them that is proportional to their absolute temperatures (hence, Kelvin). The output of the transducers will be about 3 volts or so, depend-

ing on how hot the IC is. (Very simple indoor-outdoor analog thermometer if you have a good VOM.)

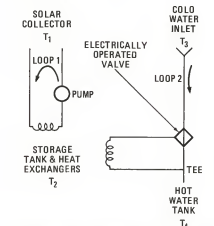


FIG. 1—BASIC SOLAR ENERGY hot-water pre-heater showing important temperature measuring points.

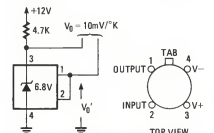


FIG. 2—BASIC SENSOR CONNECTION and pin location.

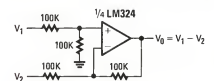


FIG. 3—DIFFERENTIAL AMPLIFIER; the power connections are not shown.

Figure 2 shows the basic connection and pin location of the transducers. Note that the output voltage of the devices is not referenced to ground but to pin 3.

Differential thermometer

It's useful to know the temperature of each component of the solar energy system, but it's not essential. What is essential is to know that component A is somewhat warmer than component B. This is the principle of the differential thermometer. The output of the thermometer is proportional to the difference of the two input temperatures. This requires a differential amplifier, which is easy to obtain using an op-amp such as the one shown in Fig. 3.

Note that the differential amplifier is based on two input voltages that are referenced to ground. Since the output of the transducers is not referenced to ground, this would seem to complicate the circuit somewhat. Luckily, there is a simple solution to this problem.

Referring to Fig. 2, note the 6.8-volt

Zener diode from pin 3 to ground. This Zener diode is internal to the transducer and maintains the voltage from pin 3 to ground at 6.8.

Since V_0 increases at a rate of 10-mV-per °K, and the sum of V_0 and V_0 must equal 6.8 volts, V_0 must decrease at 10-mV-per °K.

Using this data, we can arrive at the differential thermometer shown in Fig. 4. The output will be proportional to the difference between temperatures T_1 and T_2 and will rise as T_1 rises, assuming that T_2 remains constant. When T_1 equals T_2 , the output may not be exactly zero, because op-amps are not perfect and the 6.8-volt Zener diodes may not be exactly matched. This will not affect the operation of the circuit, and, as a matter of fact, may be used to an advantage. You should interchange the sensors if you don't get a small positive voltage (about 30 mV to 100 mV) when the sensors are at the same temperature.

Hysteresis

All control systems need some type of hysteresis, which is a type of "deadband" or buffer zone. For example, thermostats have a built-in hysteresis of about 2 °F. Assume that the hysteresis is plus or minus 1 °F of the setting. If the thermostat is set at 68 °F, the furnace will come on when the temperature falls to 67 °F and stay on until the temperature rises to 69 °F. If no hysteresis was built into the system, the furnace would cycle on and off continuously.

The hysteresis in a solar system should be fairly large—5 °F to 10 °F is not unreasonable. Figure 5 shows a comparator that is used to provide an adjustable amount of hysteresis. The LED lights as a status indicator and alarm when the set amount of temperature difference has been attained.

Interfacing

At this point, the system monitors temperature, subtracts one temperature from another, compares this value to some preset value, and lights an LED if all the conditions are met. It still won't pump much water or close a valve.

Lighting an LED has a purpose other than just providing an output of the system. When devices must be operated

at 117 VAC, such as a pump or a motor, it is necessary to isolate the control system from the AC lines. By using an LED and a phototransistor sealed in a light-tight tube, a very high degree of isolation can be achieved. You can even use two LED's—one as an output and the other as part of the photocoupler.

A circuit that handles the control of

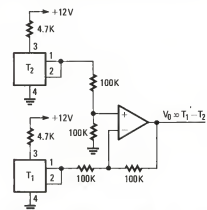


FIG. 4—DIFFERENTIAL THERMOMETER measures temperature difference.

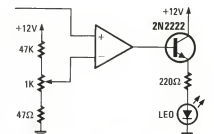


FIG. 5—COMPARATOR with hysteresis control.

the pump is shown in Fig. 6. The components might have to be scaled up or down depending on the amount of load current. And don't forget to heat-sink the triac.

Assembling the system

The complete control system is shown in Fig. 7. A regulated 12-volt power supply (see Fig. 8) is also necessary to power the system. The cost of such a supply is very low, so there is no reason to use an unregulated supply.

If you want to measure the actual temperature of one of the system components, you can use a good voltmeter.

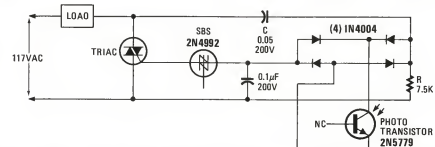


FIG. 6—LIGHT-CONTROLLED TRIAC circuit. For die triggering, $C = 0.22 \mu F$, $R = 10K$. Substitute diac for 2N4992 (silicon bilateral switch) and phototransistor with V_{ce} of 80 volts or two 2N5779's connected in series.

First, measure voltage V_i of each sensor. This (V_i) is measured from pin 3 to ground and should read about 6.8 volts. Write it down for each sensor because it will not change but will be different for each one. Any time that you want to know the actual temperature, measure voltage V_o from the output to ground. The temperature can be found from: $^{\circ}\text{C} = 100 (V_i - V_o - 2.73)$.

A voltmeter, calibrated in degrees, can even be permanently installed in your system if you desire.

Next, you must consider the sensor. The LX5600 costs a little more than the LM3911, but it has an extended operating range and slightly better absolute accuracy. Naturally, the sensors must be thermally connected to the device to be monitored. A recommended technique would be to fabricate a heat sink that the sensor will slip into. (Use the T0-5 case.) The heat sink can then be mounted to the device. Grease the sensor with heat-sink compound (silicon grease) and slip it into the heat sink. This will prevent damage to the sensor. A solar collector should be monitored in the center if possible.

It will also be necessary to insulate and weatherproof the sensor leads. Some RTV insulation should work well. It may be possible to immerse the sensor in water if you are careful. The top of the case should have very little RTV on it to make sure it isn't thermally insulated. Another method would be to seal it in a test tube. Just make sure that the leads are well insulated.

Run shielded cable to your sensors to reduce noise pickup since open wire runs of longer than a few inches tend to produce too much noise.

Check the pump and valve specifications and choose the triac accordingly. Many different types of triacs are available, and most should work with this trigger system. Don't be afraid to experiment with different triac types.

Make sure that the phototransistor is

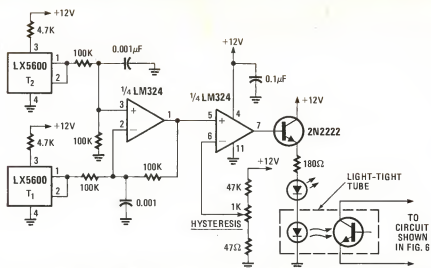


FIG. 7—SCHEMATIC DIAGRAM of complete control system. Note bypass capacitors for greater noise immunity and slight change of some component values. The LM324 contains four op-amps, so two complete loops could be handled by one IC.

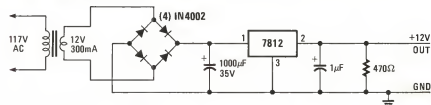


FIG. 8—12-VOLT POWER SUPPLY consists of bridge rectifier and regulator.

rated at 80 volts V_{ce} or more if you plan to use a diac to trigger the triac. The silicon bilateral switch (shown in Fig. 6) might be hard to locate, although a GE semiconductor parts supplier should have it and the 2N5779 photo-Darlington transistor.

Calibrating the hysteresis control will be somewhat time-consuming. Allow one sensor to reach room temperature. This will represent the cooler component (storage tank). Feed this output into the noninverting input of the op-amp.

Prepare a warm water bath and place the other sensor in the bath (insulate the

leads). This represents the warmer component (the solar collector). Feed the output of this sensor into the inverting input of the op-amp.

Now use a good thermometer to measure each temperature. Rotate the hysteresis control until the LED lights up. At this point, mark down on the dial the difference between the two temperatures. Repeat this at least five times. The total range, with the component values given, will be from about 1°C to 20°C . Therefore, do not raise the temperature of the bath to any warmer than room temperature plus 20°C .

R-E

Custom-built high-voltage Tesla coils now available

The Ultra High Voltage Division of Professional Sound Systems now manufactures a line of Tesla coils, kits and components that can be custom-built to fit individual needs. The coils are modular and symmetrically constructed, conservative in

design and can be used in high-voltage applications and for demonstrations.

There are 10 basic configurations from which to choose, with spark-discharge lengths ranging from 1.5 inches to over 15 feet. A full line of stock components is also available, from power-supply control consoles to oscillation transformer assemblies. All of these can also be tailored to a customer's special requirements. For information, write Professional Sound Systems, Ultra High Voltage Division, 4914 Baldwin Avenue, Temple City, CA 91780.


Report states service industry salaries are rising

It appears that salaries in the service industry are on the rise, according to a report entitled *Salaries and Related Matters in the Service Department—1978*, published by Abbott, Langer & Associates, Park Forest, IL.

For example, the report lists that the

average national service manager's salary is presently \$25,658 and that of field service representative, \$13,291. The report categorizes these and other job listings by type of product or service (also by the size of the service company or manufacturer involved), as well as containing data on various types of employers. More than 25,000 positions in over 200 organizations are listed, including salaries for national regional and local service managers; field service supervisors, engineers and senior representatives; parts managers; service training instructors; technical writing supervisors; and more. Employers represented include firms manufacturing business, electrical and communications equipment; consumer electronics; computers and allied products; and medical and scientific equipment.

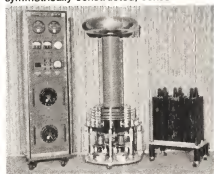The report is available for \$60 from Abbott, Langer & Associates, Box 275, Park Forest, IL 60466.





Time Compensated Hi-Fi Speaker System

THIS ARTICLE GIVES YOU AN OPPORTUNITY to keep up with the latest advances in loudspeaker design by showing how to build a pair of high-quality, time-compensated speakers for less than \$200.

Practically any multi-way speaker system can be improved by adjusting the drivers for signal arrival time. Sound from the high-frequency speakers usually arrives first. By moving the high-frequency speakers back, the sound from the woofer, mid-range driver and tweeter can be made to arrive at your listening position simultaneously. Many of the good sounds from electrostatic speakers can now be heard with nonelectrostatic systems. Time-compensation can help produce a smoother frequency response (compared with flat baffle mounting) by reducing interference between drivers at the crossover frequency. This also produces improved transient response as well as incredible depth and stereo imaging.

The secret of proper system design is to align the *acoustic center* of each driver, as seen from the side, so that they are in the same vertical plane. Each type and size of driver has its own effective acoustic center that can be located at either the voice coil, behind the coil, or in front of it.

To locate the acoustic centers and position them correctly relative to each other, I recommend using an oscilloscope, a Bruel & Kjaer condenser microphone and a bucket-brigade audio-delay line. Each driver selected for this system has very little shift of its acoustic center through its frequency range. The crossover network is adjusted for smooth frequency response. It also maintains a uniform time response when combined with

the driver time characteristics. Other kinds of drivers should not be substituted in this system since their time characteristics may not be the same.

Testing

The system should be tested for errors or a cold solder joint. Connect a 1½-volt battery across the input terminals, with the positive end going to the red terminal. The woofer cone should move out. Connect the system to your amplifier and put on FM interstation hiss. A distinct band of frequencies should be heard from each speaker—lows from the woofer, mid-frequencies from the mid-range and highs from the tweeter. These frequencies should be of approximately equal amplitude. The system can be fused with a 1½-amp normal-blow or fast-acting fuse.

The time-compensated system can be driven without stress by musical peaks of up to 100 watts. Of course, the continuous or RMS power rating of the drivers is less. Use an amplifier of 35 watts or more to avoid clipping on peaks. A severely clipping amplifier can damage the drivers and the crossover network.

Using the system

The best location for the speakers is on the floor against the long wall of the listening room. The distance between the speakers should be equal to or less than the distance from either speaker to your listening position. Avoid placing the speakers in the corners because this may provide too much bass and cause excessive room standing-wave problems. You may want to toe the speakers in toward the listening position to maintain the best

time response for each speaker.

Now, you are in for a real stereo treat. In playing various types of stereo material, you will notice an unusually well-defined stereo image. You will also notice this image will vary considerably from one recording to another. Recordings made with microphones close to the instruments may sound almost monophonic in the left and right channels. A solo instrument or voice will sound almost monophonic in the center. With the microphone placed farther back and adding more of the reverberant field, recordings will have an incredible spaciousness and an evenly spread stereo image.

I have made many true stereo recordings using only two omnidirectional microphones. The recordings range from katydid on a summer night to church choirs. The realism of these recordings is increased dramatically with the time-compensated system. Another benefit is in transient performance. Try guitar, harp, or harpsichord recordings; then try cymbals, triangles, or snare drums.

The high frequencies in this system have been adjusted for the smoothest response. Depending on how recordings are made, however, the high-frequency balance will seem to vary. The easiest and best way to compensate for this is to use the treble control: By varying the setting from 10 o'clock to 2 o'clock, you can adjust the frequency balance for the best sound in each recording.

Once you get hooked on the superior sound from the time-compensated speaker system, you won't settle for anything less from any other system.

Here's your chance to own a state-of-the-art stereo speaker system designed so the sounds from the three drivers reach your ears simultaneously. Build it for less than \$200 using ordinary hand tools.

ROGER H. RUSSELL



Cabinet construction

FOR CORRECT SIGNAL-ARRIVAL TIME, THE MID-RANGE driver must be placed so that it is $7\frac{1}{4}$ inches back from the woofer. The tweeter must be placed so that it is $2\frac{1}{2}$ inches back from the mid-range. The result is a stepped-back arrangement whose construction is only slightly more complicated than that of a normal flat baffle design. The improvement in sound is well worth it. (Figs. 1, 2 and 3 are the construction

diagrams for the front, sides and back of the speaker cabinet.)

With careful layout, many of the parts for the pair of cabinets can be made from a single 4-foot by 8-foot sheet of wood. Some lumber yards have smaller sheets available at lower cost that can be used to construct the remainder of the cabinet. A portable circular saw, a saber saw, or even a handsaw can be used to cut the panels. Visible surfaces can be painted or covered with vinyl, or wood veneer can be used.

Three-quarter-inch chipboard (also

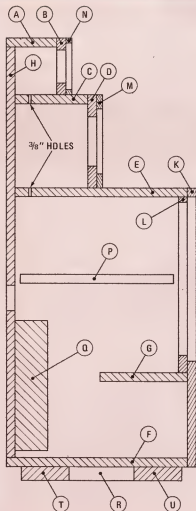


FIG. 1

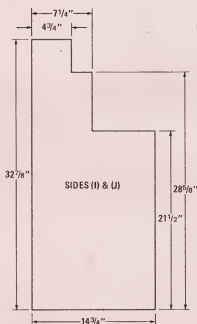


FIG. 2

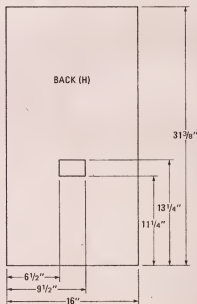


FIG. 3

called flakeboard and particle board) is recommended for strength and rigidity. You can use plywood, but voids in some plywood boards can be a nuisance when they appear at exposed edges. Oak or other hardwood bracing is necessary to further prevent cabinet vibration. To avoid counter-boring holes for each of the drivers, two different boards with different-size cutouts are glued together (see Fig. 4) and the base is constructed

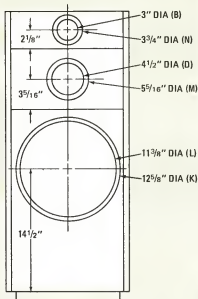


FIG. 4

from a common 2X4 (see Fig. 5). Before assembling the cabinet, cut all the required holes. Each piece should be checked for fit before it is glued and nailed in place. Check the cutouts for the speakers as well.

BASE (R) (S) (T) & (U)

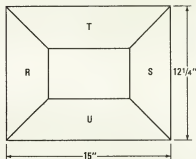


FIG. 5

Start assembling the cabinet by joining the woofer panel (shown as K in Fig. 1) to the bottom panel, F. Prior to gluing the panels together, three or four finishing nails should be hammered partway into the woofer panel. White glue should then be spread on both surfaces, the panels aligned properly and the nails driven into place.

Next, assemble one of the side panels (I or J). Nails can be partly driven into the side panel on two edges

before installing. Use white glue again, this time on the side of the woofer and bottom-panel assembly. Again, align the panels and drive the nails into place (see Fig. 6). These three panels form a rigid assembly that can be put aside for the glue to set.



FIG. 6

Next, add the other side panel, which can be installed similarly (see Fig. 7). The remaining panels can be added, working toward the top of the enclosure. Continue to check each



FIG. 7

part for fit before adding it to the assembly. The last major part to assemble is the back, H. Before installing the back permanently, be sure the woofer subpanel, L, and braces G, O and P are in place (see Fig. 8). Run a bead of glue around the joints in the woofer section to form a good seal. Finally, make sure the two 3/8-inch holes are drilled in panels C and E to allow passage of wires from the crossover network to the mid-range driver and tweeter circuits. After the back is installed, brace Q can be glued in place (see Fig. 9).

This completes the cabinet assembly. All the remaining components are installed from the outside. The cabinet can be completely finished at this time. I painted the entire enclosure with several coats of white vinyl Latex paint (see Fig. 10). Prior to painting,

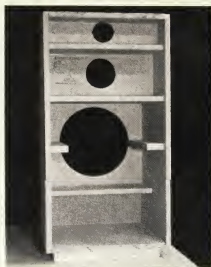


FIG. 8



FIG. 9



FIG. 10

you should fill all cracks with wood filler compound and sand the entire enclosure thoroughly.

Crossover

The heart of any good multi-way


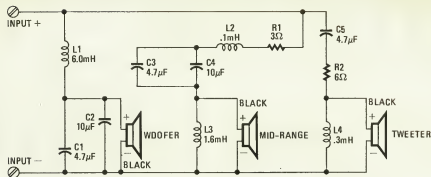


FIG. 11

speaker system is the frequency-dividing network. Numerous listening tests as well as acoustic response measurements were made to insure that each speaker output complements the others closely in frequency range and amplitude. The frequency-dividing (crossover) network, (see Fig. 11) was adjusted for best performance using Norelco (Philips) drivers (Fig. 12).

The network board is made of 1/2-

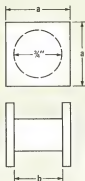

COIL	a	DOWEL LENGTH ^b	WIRE SIZE	NUMBER OF TURNS
L1-6.0mH	2 1/2"	1 1/2"	#18	675
L2-.1mH	1"	1/2"	#24	77
L3-1.6mH	1 1/2"	1"	#22	338
L4-.3mH	1"	1/2"	#24	133

FIG. 14



FIG. 12

inch particle board and is 7 inches square. A push-type connector is mounted on the opposite side of the components (see Fig. 13) so that it will be in the hole in the enclosure's back

Masonite glued to 3/4-inch-diameter dowels. Three different coil forms are used for the four coils in the network, which are made of ordinary enameled magnet wire. The number of coil turns is based on "scramble" winding. This means neat orderly rows of turns are not necessary. However, windings should be kept reasonably tight. The finished 6-mH coil weighs about 1 1/4 lb. Gluing the ends of this coil form will not be sufficient. Drive brass screws through the faces into the dowel to be sure the coil form stays together.

Coils can be started by winding a few turns of wire around your finger and then taping this wire to one face of the coil form (Fig. 15). The coil can

well glued to the board to hold them in place and prevent vibration. I recommend using RTV silicone adhesive for this purpose.

Wiring of the board is a perfectly straightforward procedure using terminal strips and mounting hardware. Component placement is shown in Fig. 16. Number 20 stranded wire with color-coded insulation is adequate as leads to the speakers. Use black-colored wire for the negative lead on all the drivers. The following wire lengths should be used: the tweeter, 24 inches; the mid-range, 20 inches; and the woofer, 21 inches.

Final installation

Place caulking compound around the inside of the crossover opening in the back panel and then push the crossover panel into place. The compound holds the board while you center the terminal in the cutout. Start drilling 7/8-inch-diameter screw holes in the back of the cabinet using the holes in the crossover panel to locate them (see Fig. 13). Drill only partway into the cabinet back. Using No. 8 X 1-inch sheet-metal screws, fasten the crossover panel in place. Dress the purple and black tweeter wires from the crossover through the 3/4-inch holes in E and C and out of the tweeter cutout. The orange and black wires go through the 3/4-inch hole in E and out of the mid-range driver cutout. Seal this 3/4-inch hole with caulking compound to create an airtight woofer compartment. The red and black woofer wires can be brought out and taped to the front of the cabinet.



FIG. 13

panel (H). The four coils are wound as detailed in Fig. 14. Coil forms are made from squares of 1/4-inch thick



FIG. 15

then be wound. After the coil is wound, wrap tape around the turns to hold them in place. The tape holding the wire on one coil form face can then be removed and both leads cut off at a length of about 3 inches from the

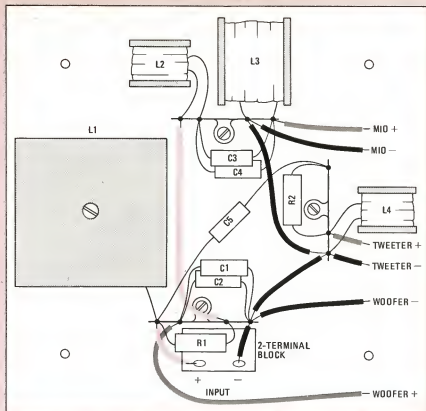


FIG. 16

With a driver in place, use the mounting holes as guides to drill the screw holes into the mounting board. For the mid-range driver and tweeter, use a $\frac{1}{8}$ -inch drill. The mounting holes for the woofer are $\frac{1}{4}$ inch.

Next, fill the woofer compartment with glass-fiber insulation material (Fig. 17). Ordinary pink home insulation material 2 or 3 inches thick can be



FIG. 17

used. A roll of this insulation costs less than the small packages of acoustic glass-fiber material needed to fill two systems. Insulation performance is the same or better, and you can use the remainder in your attic or under the hood of the family car.

Remove the vapor-barrier backing and cut the glass-fiber into small pieces. This will produce the smooth-

est bass response. Three-inch cubes will do nicely, although size is not too critical. Wear rubber gloves to avoid possible irritation to your hands. Fill the enclosure completely with loosely packed insulation material. And make sure to fill under the brace, G. No material is needed in the upper compartments because both the mid-range driver and the tweeters have sealed backs. The drivers can now be connected and installed.

Solder the color-coded wire to the positive terminal and the black wire to the negative lead. A red mark on or near the terminal indicates it is positive; if no mark appears, briefly connect a 1½-volt battery to the terminals. When the speaker diaphragm moves away from the magnet, the positive end of the battery is connected to the positive lead of the speaker. The mid-range driver and tweeter can be installed using No. 6 \times $\frac{1}{2}$ -inch sheet-metal screws. The woofer can be installed with No. 10 \times $\frac{3}{4}$ -inch sheet-metal screws. Place caulking compound only around the woofer; it should be placed between the woofer basket and the woofer subpanel, L (see Fig. 18). Again, this insures a seal in the woofer compartments.

The foam grille can be cut and installed using the self-adhering strip that comes with the grille along with cutting instructions. Three grille packages are all that are needed to cover two systems. This completes the assembly. R-E

SPEAKER SYSTEM PARTS LIST

The following items are available from McGee Radio & Electronic Corporation, 1901 McGee Street, Kansas City, MO 64108:

Part No. AD12250 W8: Two 12-inch Norelco woofers, two for \$77.

Part No. AD0211 SQ8: Two 2-inch soft-dome Norelco mid-ranges, \$19.95 each. (This part not in McGee catalog but available.)

Part No. AD0162 T8: Two 1-inch dome tweeters, \$9.95 each.

Two 3-ohm 5-watt resistors, \$20 each. Two 6-ohm 5-watt resistors, \$4.99 each.

The following items are available from Radio Shack stores:

Part No. 272-999: Four 10- μ F, 50-volt nonpolar capacitors, \$9.99 each.

Part No. 272-998: Six 4.7- μ F, 50-volt nonpolar capacitors, \$8.99 each.

Part No. 274-688: Two 5-lug terminal-strip packs of 4, \$6.99 each.

Part No. 274-621: Two terminal boards, \$9.99 each.

Part No. 40-1951: Three foam grilles, \$5.95 each.

Miscellaneous: One roll of glass-fiber insulation (approximately \$5.95); two 4-foot by 8-foot sheets of $\frac{1}{4}$ -inch particle board (\$17); five $\frac{1}{2}$ -lb (100-foot) rolls No. 18 magnet wire; two $\frac{1}{4}$ -pound (93-foot) rolls No. 22 magnet wire; two $\frac{1}{4}$ -pound (150-foot) rolls No. 24 magnet wire; white glue (\$1.79); eight No. 8 \times 1-inch sheet-metal screws; 16 No. 10 \times 1-inch sheet-metal screws; 14 No. 6 \times $\frac{1}{2}$ -inch sheet-metal screws; 2 flat-head brass wood screws; hookup wire; solder; paint; caulking compound; hardwood bracing; 8-foot-long two-by-four; $\frac{1}{4}$ -inch finishing nails.

CABINET LUMBER DIMENSIONS

To construct the cabinet for the time-compensated speaker system, the following lumber should be purchased:

$\frac{1}{4}$ -inch-thick flakeboard:

Top panel (A): 3½ inches \times 16 inches
Tweeter board (B): 4¼ inches \times 16 inches

Tweeter bottom (C): 5½ inches \times 16 inches

Mid-board (D): 7½ inches \times 16 inches
Woofer top (E): 13¼ inches \times 16 inches

Woofer bottom (F): 14 inches \times 16 inches

Mid-board (G): 6½ inches \times 16 inches
Back panel (H): 31½ inches \times 16 inches

Side panels (I & J): 32½ inches \times 14¼ inches (see Fig. 2)

Woofer board (K): 21½ inches \times 16 inches

Woofer board (L): 13¼ inches \times 16 inches

$\frac{1}{4}$ -inch-thick flakeboard:

Mid-board (M): 7½ inches \times 16 inches
Tweeter board (N): 4¼ inches \times 16 inches

$\frac{1}{2}$ -inch hardwood:

Braces (O & P): 12 inches \times 2½ inches
Brace (Q): 10 inches \times 2½ inches

2 \times 4 inch fir:

Base (R & S): 12½ inches
Base (T & U): 15 inches

Making



Work For You

The programmable read-only memory is becoming the workhouse of modern digital electronics and will play an ever-increasing role in your everyday activities. Here is what it's all about.

ROBERT H. PENOYER

THE PROM (PROGRAMMABLE READ-ONLY Memory) is increasingly being accepted as a circuit element. The electronic hobbyist or home computer owner should become familiar with this very useful device. Because there have been numerous articles written about both the PROM and the EPROM (Erasable PROM), this article will just briefly mention their theory of operation, and concentrate on the ways these devices can be put to use.

What is a PROM?

Figure 1 shows the basic configuration of a 16×4 -bit PROM; that is, there are 4 address lines, and, therefore, $2^4 = 16$ states can be represented. Each of these 16 states is decoded into a single control line that leads to a set of junctions in the memory array. These junctions are either closed or fused open depending upon how the PROM is programmed. The logic state of the junctions selected by the address decoder passes through the buffer and appears at the output. Figure 1 shows 4 output lines; thus, there are $2^4 \times 4$ or 16×4 junctions. This PROM can also be described as containing 16 words with 4 bits-per-word. There are as many words as there are address states. Therefore, if the PROM had eight address lines

and one output line, it would be a $2^8 \times 1$ -bit or a 256×1 -bit PROM, or containing 256 1-bit words.

Just as there are closed or fused-open junctions in a PROM array, the EPROM uses static charges on MOSFET transistors to achieve the effects of an open or closed junction. The charges on the MOSFET's can last for years or be erased in a few minutes by special ultraviolet lamps.

Using the PROM

The PROM serves two main purposes: First, a single PROM IC can replace an entire multiple-gate logic array. Say, for example, you needed a set of gates that would perform the function described in the truth table of Fig. 2. If standard gates were used, a complex network would result. Instead, let the four left-hand columns of Fig. 2 represent the address lines, and let the column on the right represent the output line of a 16×1 -bit PROM. Thus you would achieve the desired function using only a single IC. The result is a savings in wiring time, troubleshooting time and board space.

The second main use of a PROM is as a "look-up table." For example, suppose you wanted a counter to count in the sequence shown in the right-hand side of

Fig. 3. This could be extremely difficult to accomplish using ordinary logic. Instead, you can apply the output lines of an ordinary binary counter to the address lines of a PROM. Upon reaching any of the 16 possible states, the counter causes the internal logic of the PROM to "look up" the desired output state and pass it through its buffer to the output, according to the truth table. Only two IC's, a 4-bit binary counter and a PROM are needed to arrive at a rather complicated sequential output.

Another example of using a PROM as a look-up table is a Baudot to ASCII code translator. The Baudot code can act as the address for a PROM, and the PROM output can yield equivalent ASCII characters.

Propagation delay and access time

As with any logic device, propagation delays in PROM's are important, particularly so if a PROM's output lines are used to drive counters or clocked logic of any type.

A specifically limited amount of time is required to receive an address, decode it, drive a set of junctions in the PROM array and transmit the result through the buffers to the PROM output. This is called the PROM's access time, and is

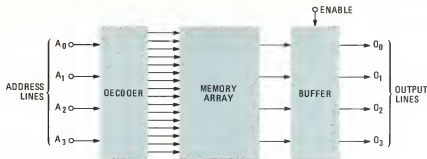


FIG. 1—PROM consists of an address decoder, output buffer and memory array.

A ₀	A ₁	A ₂	A ₃	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

FIG. 2—COMPLEX LOGIC FUNCTIONS such as the one shown in the above truth table can be easily handled by a PROM.

A ₀	A ₁	A ₂	A ₃	O ₀	O ₁	O ₂	O ₃
0	0	0	0	0	0	1	0
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	0
0	0	1	1	1	0	1	1
0	1	0	0	1	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	1	0	1	1
0	1	1	1	1	1	0	1
1	0	0	0	1	1	1	0
1	0	0	1	1	1	0	1
1	0	1	0	1	0	1	1
1	0	1	1	0	1	1	1
1	1	0	0	1	1	1	1
1	1	0	1	0	0	0	0
1	1	1	0	1	0	0	1
1	1	1	1	1	0	1	0

FIG. 3—COUNTERS with an unusual counting sequence can easily be designed using a PROM.

listed in the manufacturer's data sheet. During the access delay time, the state of the output lines on a PROM is unpredictable. A set of outputs can pass through several states during the transition from one address to the next. Therefore, if the outputs are driving clocked logic, the logic could receive undesired data. Obviously, this should not be allowed to happen. Luckily there are methods to get around this problem.

Buffer and latch isolation

As shown in Fig. 1, the output buffer of the PROM often has an enable control line. Typically, this enable line is used to select the device that is to be connected to a parallel bus system when many such tri-state devices are used. When enabled, the buffer outputs are at normal logic levels. When not enabled, the buffer outputs appear to be open circuits. If all the buffer output lines are pulled to +V

through, say, 10K resistors (in the case of TTL logic) then when the output lines are disabled they will be at a known high logic level. Therefore, no output line can go low unless that particular bit was programmed low and the PROM output was enabled. Thus, it is only necessary to disable the output when changing addresses. Using such an arrangement, no glitches appear at the output and low-going pulses appear only when desired. Figure 4 shows a typical circuit using this technique.

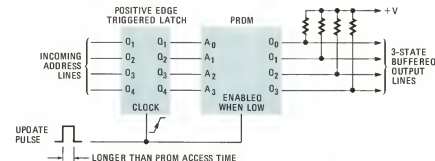


FIG. 4—DISABLING PROM during access time prevents glitches from appearing at the output.

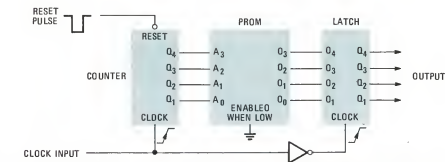


FIG. 5—CLOCK SIGNAL in synchronous circuits can be used to inhibit output during access time.

You can use a similar more desirable technique that requires no pull-up resistors on the buffered output lines. Let's say, for example, you want a circuit that counts as shown in the Fig. 3 truth table. Also assume that you could not arbitrarily allow the outputs to go high, as shown in Fig. 4.

Figure 5 shows an alternative technique: a synchronous binary counter drives the address lines of a PROM that is programmed according to the truth

table shown in Fig. 3. Therefore, as the counter passes through each binary state, the desired output appears on the PROM output lines. These lines are always enabled as shown in Fig. 5. Note that both the counter and the latch are triggered by positive-going clock edges, and there is an inverter in the latch clock line. This means that while the counter still triggers on the positive-going edge of the clock, the latch will trigger on the negative-going edge. This provides a delay of one-half clock period between the time the counter is updated and the resulting PROM output appears at the latch output. If the PROM access time is shorter than one-half clock period, its output will be settled by the time the latch uses it. The result is a clean accurate set of waveforms at the latch output.

PROM sources

PROM's and EPROM's are available in many configurations. Just check through manufacturers' catalogs for the type of PROM you need for your application. Sometimes the required number of

words and word length are not available and you have used a PROM with more words or bits than you need. In this case, you should consider the economics of wasting PROM capability.

Most large distributors can program a PROM for you if you purchase it from them. Find out all the necessary information before placing the order for your PROM; often the distributors will program the device for a small fee or at no additional cost.

R-E

NOM Card For The 1802

Add-on math board for an 1802-based microcomputer.

Based on a number-crunching IC, this board speeds execution time, reduces software overhead and saves memory

L. STEVEN CHEAIRS

NOW THAT YOU HAVE YOUR RCA 1802-based microcomputer up and running, what do you do next? You might consider putting it to some serious work, but in doing so, you will probably run into the software wall. In other words, for most applications a good deal of programming will be required, and a good portion of it will be for mathematical operations. It's also a known fact that you can age very rapidly writing all the software needed to perform the required mathematical operations.

One alternative is to use hardware instead of software to perform these operations. The first idea I had was to use a scientific calculator IC. This would certainly reduce the software development time, leaving me only the interfacing to worry about. While this apparently solves the software problem, it creates a Pandora's box full of new ones.

First, most calculator IC's have on-chip debounce circuitry designed to solve the problems generated by multiple character entry due to noisy keyboard switches. This is a very positive feature for a calculator, but, unfortunately, it tends to slow a microprocessor down.

Second, a calculator IC in its natural habitat is interfaced to a keyboard via a set of multiplexed input/output (I/O) pins. This requires complex interfacing to convert incoming data into the signals necessary to imitate a keyboard switch. While this is not an impossible task, it is a bit messy.

Third, a calculator is designed to stand alone, not act as a slave processor for a microcomputer system. The data is outputted in a multiplexed 7-segment, non-TTL format. Multiplexing data is not only acceptable but desirable. On the other hand, a 7-segment format is not

exactly the easiest format for a computer to manipulate. It could of course be converted to a BCD (Binary-Coded Decimal) format by several methods, such as a software look-up table, or a PROM could be programmed to convert a minimum of five input lines into the four BCD output lines. Another point to consider is that the calculator IC's do not have the control lines required to interface it to the processor.

You could try another approach, such as dedicating a CPU and a ROM as a mathematical processor. National Semiconductors has done just that with its new

Number-Oriented Microprocessor (NOM). This special-purpose microprocessor, the MM57109, is available through distributors. This single IC will provide most, if not all, of the mathematical operations needed for any computer system. The software overhead is drastically reduced when this processor is used.

The MM57109

Figure 1 is the internal block diagram of the MM57109, showing both the signal lines and their point of origin. The internal register file is composed of five

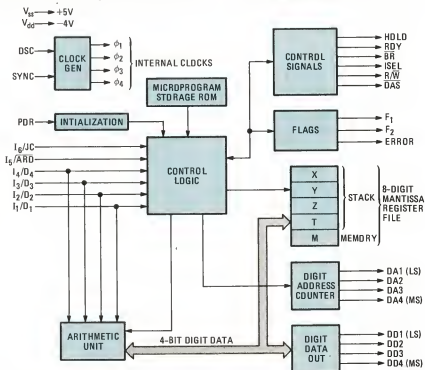


FIG. 1—BLOCK DIAGRAM OF THE MM57109 number-oriented microprocessor.

registers (X, Y, Z, T and M); each has eight mantissa digits, two exponent digits, a decimal-point position indicator, and the mantissa and exponent sign bits. The program-storage ROM stores about 1500 eight-bit micro-instruction words. The 6-bit-long program instructions enter through the I_{14} -lines and are converted into a sequence of these micro-instructions. The BCD data words enter the control logic via the I_{14} -lines.

Data is outputted, after receiving the OUT instruction, through the digit-data-out block. The digit-address-counter block sequences each digit during the I/O operations. The Read/Write control line is used during the OUT instruction to latch the data words into the interface register.

Figure 2 shows a table of the MM57109's important features. These features can be classified into four categories: scientific calculator-type instructions, I/O, branch control and interface.

Basically, the MM57109 looks like an RPN (Reverse Polish Notation) scientific calculator. The only major difference is in the I/O and control-interface circuitry. National Semiconductor engineers state that the MM57109 is a *modified* scientific

Instructions	Input/Output	Branch Control	Interface
RPN	HOLD for asynchronous and single step operation	Conditional and unconditional program branching	Single phase clock
1 to 8-digit mantissa	Asynchronous digit input instruction (AIN) with AIN ready (ADR) input	Increment/decrement branch on non-zero for program loops	Low power operation
2-digit exponent	Multidigit I/O instructions (IN, OUT)		Generation of I/O control signals
Four-register stack, one-memory location	Floating point or scientific notation		Separate digit input, output, and address bus
Trigonometric functions, logarithmic functions, Y^x , e^x , π , etc.	Programmable mantissa digit count for IN, OUT instructions		
Error Flag	Sense input and flag output		

FIG. 2—FEATURES OF THE MM57109 that are important to the NOM card constructor.

calculator. First, we'll take a look at the 1802-type interface; then, the instructions and programming techniques will be discussed. If you are not yet convinced that the MM57109 is the way to go, then look at Table 1. As stated earlier, the NOM is very easy to interface to almost any computer system. The MM57109 is

TABLE 1—Comparison of MM57109 to the Average Microprocessor and Calculator IC's

	MM57109	MICROPROCESSOR	CALCULATOR
Speed (math or I/O)	0.5–400 ms	0.5–500 ms	14–400 ms
Data length	Variable (1- to 8-digit mantissa)	Fixed	Fixed
Data format	Floating point, and scientific notation	Binary	Floating point, and scientific notation
I/O	Multidigit, asynchronous digit and single bit	Data bytes and single bit	Keyboard/display
Program	External ROM/PC, μP or FIFO	External ROM, internal PC	Key sequence

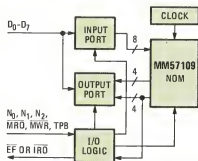


FIG. 3—1802 MICROPROCESSOR INTERFACE for the MM57109.

only one of two NOM interfaces that Qestar Engineering is marketing; the other is for the S-100 bus.

Circuit operation

The basic circuit operation is shown in the block diagram of Fig. 3, while the complete schematic is shown in Fig. 4. The I/O signals (N_0 , N_1 , N_2 , TPB , MRD , MWR) from the 1802 are decoded, and are used to move data into and out of the NOM via two 8-bit data latches. One-half of the data output port, D_0 – D_3 , is the

PARTS LIST

All resistors $\frac{1}{2}$ watt, 5% unless noted.

R1–R5, R17, R18—10,000 ohms
R6—300 ohms, $\frac{1}{2}$ watt
R7—1000 ohms
R8—18,000 ohms
R9, R10, R12–R15—2000 ohms
R11, R16—9100 ohms
C1, C5—1- μF , 35-volt, electrolytic
C2, C3, C8, C11, C12—0.01- μF , disc
C4, C9, C10—100-pF, disc
C6, C7—10- μF , 20-volt, electrolytic
D1—1N703 Zener diode (or equal), 3.9 volts
IC1, IC2—4508, dual 4-bit latch
IC3, IC13—4069, hex inverter
IC4—4073, triple 3-input and gate
IC5, IC6, IC8—4013, dual D-type flip-flop
IC7—4049, hex inverter buffer
IC9—4528, BCD-to-decimal decoder/binary-to-octal decoder
IC10—DS8800, dual TTL-to-MOS voltage

converter
IC11—MM57109, NOM
IC12—4072, dual 4-input or gate
S1–S4—DIP switch (8 SPST switches)
Misc.—One 28-pin DIP socket for IC11, and a PC board.
The following are available from Qestar Engineering Co., 50 S. MacDonald St., Mesa, AZ 85202:
PC board, predrilled and etched, \$33
Complete kit of all parts, \$98
EIF II to SB-44 converter card, \$6.95
MM57109 NOM IC, \$18
DS8800 TTL-to-MOS converter IC, \$6.45.
Qestar also has a PROM containing a subroutine that will perform all the power-up housekeeping and FIFO interface between the 1802 and the NOM. Also included on the PROM is a monitor-type software package, \$28.50.
Note: The decision to use a dual 22-pin

card was based on the fact that this card has been a standard component of the electronic field for many years. The Vector-size card and hardware are readily available and less expensive than other components. There are a variety of other printed-circuit cards using this same bus, a few of which will be available in the future. These PC cards include a Vector-type graphic display that uses an oscilloscope as a display; a 2K-byte EROM/2K-byte low-power RAM card; and a nonvolatile 4K-byte RAM board; the EROM's are programmed in place on the card. This permits the EROM to be treated like a RAM, plus a program can be developed in RAM and transferred to EROM without unplugging any components. The program can then be executed immediately from the EROM.

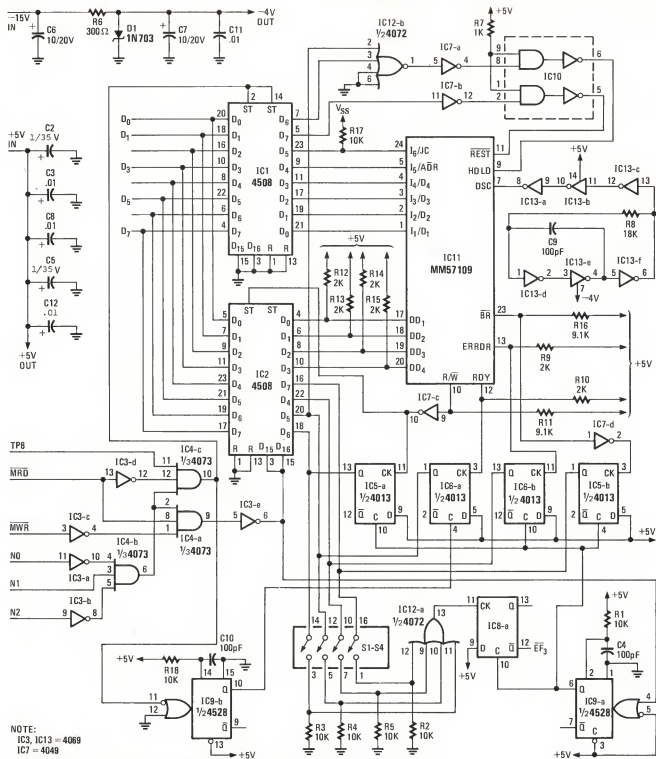


FIG. 4—COMPLETE SCHEMATIC FOR THE NOM interface. The top end of R17 goes to +5 volts which is equivalent to V_{cc} . The -4-volt level is equivalent to V_{ee} .

BCD data from the NOM, while the other 4 bits are used to provide status information to the 1802 CPU. Note that the address counter digit from the NOM is not provided. This is because the address digit requires 4 bits of the I/O port (thus requiring a second output port). This may seem like a poor decision just to save one output port, but it is not. The output format of the NOM is defined by the internal architecture, and with a minor amount of software added to the 1802's program, the same informa-

tion may be derived. Figure 5 shows the data formats for both the scientific-notation mode and Fig. 6 shows the floating-point mode.

The other 4 data bits inform the 1802 of the NOM's status; also any of these 4 bits can be configured to output an active low signal, which should be used to set one of the event flags or initiate an interrupt. Bits D_0 - D_3 of the input port supply the instructions to pins I_1 - I_4 pins; input data is placed on the D_0 - D_3 lines and enters through I_0 - I_3 . The 1802 uses the

upper input data, bits D_6 and D_7 , to reset and/or halt the NOM. This data is shown in Fig. 7, along with port decoding information.

The control logic is actually quite simple; and in fact, the whole circuit is also very simple. It can be described in three parts—the input decode, the NOM status register and the interrupt request circuitry.

The input decode circuit is formed by IC3, IC4 and IC9-a. These IC's are used to decode \bar{N}_0 , N_1 , \bar{N}_2 , MRD, and TPB

($\bar{N}_0, N_1, \bar{N}_2, \text{MRD}, \text{TPB}$), and to clock data and/or instruction into the input buffer. The product of $\bar{N}_0, N_1, \bar{N}_2, \text{MRD}$, and MWR ($\bar{N}_0, N_1, \bar{N}_2, \text{MRD}, \text{MWR}$) is used to enable the output buffers allowing status information and data from the $\text{DO}_0\text{--}\text{DO}_3$ output of the NOM to be transferred to the 1802. One-shot IC9-a produces a pulse on the falling edge of control line N_2 , which is used to reset input-ready flip-flop IC6-a.

The NOM status register is formed by one-half of the output buffer, IC₂ (bits $D_7\text{--}D_3$), and four D-type flip-flops along with two inverters. The least significant bit, D_0 , is the error flag; eight possible types of errors are shown in Table 2.

TABLE 2—Error Conditions of the MM57109 NOM

1. LN X and LOG X when X 0
2. When any result is 10^{-99} or 10^{100}
3. When TAN 90° , 270° , 450° , etc.
4. SIN X, COS X, TAN X for X 9000°
5. SIN $^{-1}$ X, COS $^{-1}$ X for X 1 or X 10^{-90}
6. For SQRT X when X 0
7. For $\sqrt{}$, INV, $1/X$ when X = 0
8. In the floating-point mode for the our instruction if the number of digits to the left of the decimal point is equal to the Mantissa Digit Count.

Whenever an error occurs, an ECLR (Error Flag Clear) instruction must be executed. The error flag can be tested at any time by the TERR instruction, a branch-type instruction (branches if ERROR = 1). The 1802 can also check this condition by reading the D_0 bit of the output port; this bit is reset after its access. Bit D_3 is the input-ready signal; it indicates the NOM is ready to execute the next instruction or to get the second word of a two-word instruction.

In order to permit asynchronous operation between the 1802 and the NOM on the rising edge of bit D_3 , the NOM is placed into a hold state, hold = 1. When flip-flop IC6-a is reset by control line N_2 (as stated earlier, this occurs on the falling edge of control line N_0 , which is used to load new instructions into the input port) the NOM will execute the next instruction. When the user's program is informed by bit D_3 that the input is ready, then the program provides the next instruction to the NOM.

Bit D_6 is the output-ready signal. Upon receiving this information, the user program stores the data into a software FIFO—a table in memory that acts like a first-in/first-out memory. The reason that a software FIFO is needed is due to the method in which the NOM outputs data. An OUT instruction is sent to the NOM, which, in turn, causes the NOM to output the first digit. Ten microseconds later, the output-ready flip-flop is set, and the $\text{DO}_1\text{--}\text{DO}_4$ output bits are clocked into the lower bits ($D_7\text{--}D_3$) of the output port. This data must be read and

DA ₄ –DA ₁	IN: D ₄ OUT: DO ₄	D ₃ DO ₃	D ₂ DO ₂	D ₁ DO ₁
0	Most Significant			
1	Least Significant		Exponent Digit	
2	Sign (Mantissa)	0	0	Sign (Exponent)
3	Unused			
4	Most Significant Mantissa (Followed by Decimal Point)			
.
.
Mantissa Digit Count + 3	Least Significant Mantissa Digit			

FIG. 5—IN/OUT INSTRUCTIONS (Scientific Notation Mode).

DA ₄ –DA ₁	Decimal point position	IN: D ₄ OUT: DO ₄	D ₃ DO ₃	D ₂ DO ₂	D ₁ DO ₁
2					
3		Sign (Mantissa)	0	0	0
4	11	Decimal Point Position			
.	10	Most Significant Mantissa Digit=0-9			
.
.
Mantissa Digit Count + 3	12-Mantissa Digit Count	Least Significant Mantissa Digit=0-9			

Where: DA₁–DA₄ is the digit address

DO₁–DO₄ is the digit data out

D₁–D₄ is the digit data in

Also:


The mantissa digit count is set by the SMDC instruction, initially it is equal to eight.

For the sign of the mantissa zero represents positive and one represents negative.

The sign of the exponent is equal to zero in the floating point mode.

The decimal point position indicator is a value in the range from 11 down to (12-mantissa digit count), which indicates a digit, as given by the decimal point position indicator column in the table. The decimal point is located to the right of this digit.

FIG. 6—IN/OUT INSTRUCTIONS (Floating-Point Mode).

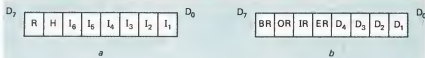

At: TPB=1

When: $N_0=0, N_1=1, N_2=0, \text{MRD}=0$

Where:

R is reset,

H is hold,

$I_1\text{--}I_6$ is the instruction inputs,

$D_1\text{--}D_3$ is the digit data out,

BR is the branch output,

OR is the output ready,

IR is the input ready,

ER is the error output.

At: $\text{MWR}=0$

When: $N_0=0, N_1=1, N_2=0, \text{MRD}=1$

FIG. 7—PORT FORMAT. a) Input; b) Output.

the flip-flop cleared (by reading the port) within $140\ \mu\text{s}$ because the second digit will be outputted at that time. Every $140\ \mu\text{s}$, a new digit will be made available, along with a data-ready signal, until the full number is outputted. The last bit, D_7 , is the branch signal. This signal indicates a program branch has been encountered; input ready is set during this signal.

The interrupt-request circuitry is formed by the 4-input OR gate, IC12-a, and the D-type flip-flop, IC8-b, along with a DIP switch and four pull-down resistors. The four status signals (error, input ready, output ready and branch) are connected to a 4-input OR gate via a set of SPST switches, along with the pull-down resistors. This permits any of the status

signals to clock a logic 1 into the D-type flip-flop, providing a total of 16 possible interrupt (or event-flag) conditions. For example, if you're only interested in knowing when the output is ready (this implies that no branch instructions are to be used, that the data/instructions inputted are free of errors, and sufficient time is allowed between instructions so that a new instruction can never be inputted in the middle of an instruction already being executed), then all but the output-ready switches are opened. Thus, a logic 1 is clocked into IC8-b only when the output-ready signal is active. The \bar{Q} output relays this information to the 1802 via either the $\bar{\text{IRQ}}$, or one of the four event flags (EF_1).

continued on page 79

Radio-Electronics

Tests Sansui G-9000

AM/FM Receiver

LEN FELDMAN

CONTRIBUTING HI-FI EDITOR

SANSUI'S TOP RECEIVERS THIS YEAR ALL feature a DC-configured power-amplifier section. This means that there are no input coupling capacitors to the power section, and that all capacitors in the feedback network have been eliminated. The advantages claimed for this circuitry are in improved transient response (lower transient intermodulation distortion) and a frequency response that goes right down to DC. The audible difference between an AC-coupled amplifier and a DC-coupled one may be subtle to inexperienced listeners, but serious audiophiles report somewhat cleaner and more accurate sound reproduction from such DC-configured circuits.

From our point of view, the Sansui model G-9000 offers a good deal more than just a DC amplifier. The front panel, shown in Fig. 1, is loaded with features that will delight the audio buff seeking maximum control and flexibility. The light-colored, sloped frequency scales (the FM scale is linearly calibrated with markings at every 200 kHz) are surmounted by four well-illuminated meters, two of which are power-output meters, logarithmically calibrated from 0.1 watt to 300 watts (referred to 8-ohm loads). The other two meters are signal-strength and center-of-channel indicators for the tuner. To the left of the meters are four

indicator lights, two showing which speaker pair is activated; the other two serve as a power-on indicator and a "protector" indicator. The protector indicator flashes intermittently for a few seconds when the power is first turned on until voltages have been fully stabilized, after which sound is heard from the speakers.

Five indicator lights to the right of the meters denote the program source selected. A series of positive-feel toggle switches just below the dial area to the left handle power, speaker selection, bass and treble control turn-over frequencies (200 Hz or 400 Hz for the bass control, 3 kHz or 5 kHz for the treble), tone control defeat and -20 dB audio muting. Similar toggle switches to the right handle FM muting, stereo or mono listening modes, 25- μ s or 75- μ s de-emphasis, FM noise filter and wide or narrow bandwidth for the FM IF circuits. A microphone mixing level control and microphone input jack are located at the extreme lower right-hand side of the panel.

Major controls along the bottom of the front panel include BASS, TREBLE and MID-RANGE tone controls (each with fixed, detented steps for easy resetting), balance control, program SELECTOR switch and TAPE MONITOR switch (with positions for monitoring either of two connected tape decks or dubbing from one to another). Two massive knobs in the center of the panel take care of frequency tuning (the



FIGURE 104 ON FREE INFORMATION CARD

smoothest-acting flywheel-dial arrangement we've ever experienced) and master volume-control settings. The volume control contains an index tab that can be set at preferred maximum listening levels. Its clutch-like action prevents the volume control from being accidentally turned to overload or excessive listening levels—a nice feature if there are young children in the house who might inadvertently turn the volume all the way up and destroy speaker voice coils in the process! Three square pushbuttons between these two large controls activate subsonic and high-cut filters as well as the loudness compensation circuits. A similar pushbutton near the program selector switch provides a third circuit-interruption point for the insertion of a four-channel adapter, graphic equalizer, audio time-delay unit, or a Dolby noise-reduction adapter. A headphone jack just below the POWER switch on the lower left completes the panel layout.

The rear panel of the model G-9000 contains three AC convenience outlets (one switched, two unswitched). One of the most pleasing physical features of this receiver is how the input/output jacks and terminals are positioned. These connections are located in recessed areas in the side wood panels of the unit, rather than at the rear. All input and (tape-out) terminals, as well as AM and FM antenna terminals, can be reached from the right side of the unit, while two sets of spring-loaded speaker terminals, preamplifier-output/main amplifier-input terminals and a switch that separates the two major receiver sections electrically are located on the opposite side panel (see Fig. 2). A cleverly designed channel along each side of the unit keeps cables

MANUFACTURER'S PUBLISHED SPECIFICATIONS:

FM TUNER:

Usable Sensitivity: mono, 8.7 dBf (1.5 μ V); stereo, 15 dBf. **50-dB Quieting:** mono, 12.5 dBf; stereo, 34.0 dBf. **S/N Ratio:** mono, 80 dB; stereo, 76 dB. **Harmonic Distortion (wide):** mono, 0.06% at 1 kHz and 100 Hz; 0.08% at 6 kHz; stereo, 0.1% at 100 Hz and 6 kHz, 0.08% at 1 kHz. **Selectivity:** 90 dB (narrow); 55 dB (wide). **Capture Ratio:** 0.9 dB. **Image, IF and Spurious Rejection:** 110 dB. **Frequency Response:** 30 Hz to 15 kHz, +0.2, -1.0 dB. **Stereo Separation:** 50 dB at 1 kHz; 40 dB at 100 Hz and 10 kHz.

AM TUNER:

Usable Sensitivity: 300 μ V/M internal antenna. **Selectivity:** 30 dB. **S/N Ratio:** 50 dB. **Distortion:** 0.45%. **Image and IF Rejection:** 70 dB.

AMPLIFIER:

Power Output: 160 watts-per-channel into 4 or 8 ohms, 20 Hz to 20 kHz at no more than 0.03% total harmonic distortion. **IM Distortion:** 0.03%. **Damping Factor:** 60. **Frequency Response:** power amplifier section, DC to 200 kHz, +0, -3 dB; overall, auxiliary inputs, 5 Hz to 50 kHz, +0.2, -1.5 dB; phono, RIAA \pm 0.2 dB. **Input Sensitivity:** phono 1 & 2, 2.5 mV; high level, 150 mV; mike, 6.0 mV. **S/N Ratio:** phono, 78 dB ("A" weighted); high level, 95 dB. **Bass Control Range** (400-Hz turnover): \pm 10 dB at 50 Hz. **Treble Control Range** (1.5 kHz turnover): \pm 10 dB at 10 kHz. **Mid-Range:** \pm 5 dB at 1.5 kHz. **Subsonic Filter:** -3 dB at 16 Hz (6 dB-per-octave). **High-cut filter:** -3 dB at 3 kHz (6 dB-per-octave).

GENERAL SPECIFICATIONS:


Rated Power Consumption: 680 watts. **Dimensions:** 22 1/2" W X 8 H X 19 1/2" D. **Net Weight:** 59.3 lb. **Suggested Retail Price:** \$1050.



neatly tucked out of sight. This innovative arrangement makes installation extremely simple, especially for a large, heavy unit such as this one, which might be difficult to hook up if all connections had to be made at the rear panel.

No schematic diagram was supplied with our sample test unit, but it is clear from the receiver's internal layout (shown in Fig. 3) that

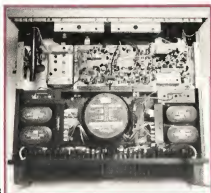the huge toroidally wound power transformer has two separate secondary windings, each of which supplies power to a single channel; voltages are filtered separately by two pairs of large filter capacitors.



The power amplifier, as mentioned earlier, is a DC-coupled circuit from input to output, with no capacitors either in the signal path or in the overall negative-feedback loop. If components are connected directly to the main amplifier (by separating the preamplifier and main amplifier sections electrically), and if the outputs of those components contain any DC signal, the protection circuit immediately disconnects the speakers from the output stages. In that event, the switch separating the preamplifier output from the main-amplifier input has a third setting that introduces an input capacitor so that operation can be resumed.

FM measurements

Table 1 summarizes FM measurements made for the *model G-9000*. Where measurements differ between the wideband and narrowband positions, both sets of measurements are shown separated by a slash (/). For example, while 1-kHz mono distortion measured an incredibly low 0.03% in mono using the preferred wideband setting, when using the narrowband setting (used only if adjacent-channel interference is encountered in crowded FM listening areas), distortion increased to 0.15%.

Sansui evidently decided to make the narrowband IF response very narrow indeed because distortion rises markedly when this setting is used, particularly in the stereo mode. Wideband distortion readings, on the other hand, are among the lowest we've ever encountered for an FM tuner section or, for that matter, for a separate component tuner.

Separation capability of the *model G-9000* also varies depending upon whether the narrow or wideband settings are used. Figure 4 shows the frequency response of the left channel as well as crosstalk in the opposite channel (lower trace). The vertical scale is 10 dB-per-division, and we measured static separation of nearly 50

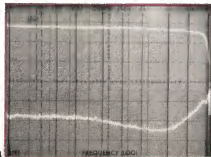


TABLE 1
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Sansui


Model: G-9000

FM PERFORMANCE MEASUREMENTS

SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE	R-E Measurement	R-E Evaluation
IHF sensitivity, mono (μ V) (dBf)	1.5 (8.7)	Superb
Sensitivity, stereo (μ V)	5.5 (20.0)	Very good
50-dB quieting signal, mono (μ V)	1.5 (8.7)	Superb
50-dB quieting signal, stereo (μ V)	18 (30.3)	Superb
Maximum S/N ratio, mono (dB)	80	Excellent
Maximum S/N ratio, stereo (dB)	76	Excellent
Capture ratio (dB)	1.0	Excellent
AM suppression (dB)	65	Excellent
Image rejection (dB)	100+	Superb
IF rejection (dB)	100+	Superb
Spurious rejection (dB)	100+	Superb
Alternate channel selectivity (dB)	92/53	Excellent
FIDELITY AND DISTORTION MEASUREMENTS		
Frequency response, 50 Hz to 15 kHz (\pm dB)	+0, -1.5	Good
Harmonic distortion, 1 kHz, mono (%)	0.03/0.15	Superb
Harmonic distortion, 1 kHz, stereo (%)	0.06/0.5	Superb/see text
Harmonic distortion, 100 Hz, mono (%)	0.06/0.07	Superb
Harmonic distortion, 100 Hz, stereo (%)	0.09/0.7	Superb/see text
Harmonic distortion, 6 kHz, mono (%)	0.06/0.13	Superb
Harmonic distortion, 6 kHz, stereo (%)	0.10/0.45	Excellent
Distortion at 50-dB quieting, mono (%)	3.0/5.0	See text
Distortion at 50-dB quieting, stereo (%)	0.8/0.6	Good
STEREO PERFORMANCE MEASUREMENTS		
Stereo threshold (μ V) (dBf)	3.0 (14.8)	Very good
Separation, 1 kHz (dB)	48/36	Excellent
Separation, 100 Hz (dB)	43/34	Very good
Separation, 10 kHz (dB)	42/30	Excellent
MISCELLANEOUS MEASUREMENTS		
Muting threshold (μ V) (dBf)	4.5 (18.3)	Very good
Dial calibration accuracy (\pm kHz at MHz)	Perfect	Superb
EVALUATION OF CONTROLS, DESIGN, AND CONSTRUCTION		
Control layout		Excellent
Ease of tuning		Very good
Accuracy of meters or other tuning aids		Superb
Usefulness of other controls		Good
Construction and internal layout		Excellent
Ease of servicing		Good
Evaluation of extra features, if any		Very good
OVERALL FM PERFORMANCE RATING		Excellent

dB at mid-frequencies.

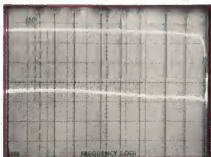Note that our test equipment is now equipped to provide flat frequency-response readings (compared with the response readings shown in previous test reports that include the de-emphasis characteristics of the tuner) so the




scope traces represent actual response.

When the narrowband setting is used, separation is somewhat diminished, as shown in Fig. 5, although overall frequency response remains unaltered and quite good.

In recent months, we have received requests to report on the AM sections of the tuners and receivers we test. While the harmonic distortion and signal-to-noise ratio measured for the

AM section of the *model G-9000* were both within specifications, the AM frequency response (not specified by Sansui) was as poor as it is on most "hi-fi" receivers. To demonstrate this, we swept modulating frequencies such as we do for FM response measurements; the results (although hard to believe) are shown in the scope photo of Fig. 6. Perhaps Sansui and other manufacturers will pay more attention to

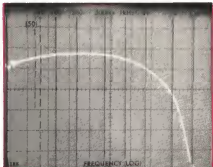

their AM bandwidth if and when stereo AM becomes a reality in the near future. For the moment, the less said about AM response in typical high-fidelity receivers and tuners the better.

peak-to-peak swing of 96 volts is possible under full-load conditions. This corresponds to an RMS AC value of 33.94 volts (peak-to-peak value divided by 2.828, or multiplied by 0.5×0.707). The continuous power output of this first amplifier, before clipping, would be approximately 144 watts. ($P = E^2/Z$, where $E = 33.94$ volts and Z , the impedance, is assumed to be 8 ohms.)

Now let's calculate the continuous power output for the amplifier being powered by the supply shown in Fig. 2, where the available supply voltage has dropped to plus and minus 40 volts. The permissible peak-to-peak swing of the output signal voltage is 80 volts. This corresponds to an RMS value of only 28.29 volts, or an equivalent power across 8 ohm loads of 100.03 watts.

Thus we see that even though both power supplies (under no-load conditions) provide the same operating voltages to their associated amplifiers under no-signal (or low-signal) conditions, their maximum continuous power output ratings will differ substantially, with the amplifier powered by the supply shown in Fig. 2 able to deliver only 69% as much continuous power as the amplifier powered by the supply shown in Fig. 1.

Power supply regulation

There are several reasons why the voltage output of the supply shown in Fig. 2 dropped more quickly than the voltage delivered by the supply shown in Fig. 1. For one thing, its filter capacitors are of considerably lower value. The primary filter capacitors in such a supply act as a power or energy reservoir. The greater their value, the greater the amount of energy that can be stored in them. Note, too, that the primary and secondary windings of each of the power transformers used in the two supplies may have different internal resistances and, therefore, different AC voltage drops may appear across these windings before the AC voltages are ever rectified. The bridge rectifiers, too, may differ in internal resistance and may therefore develop greater voltage drops across their terminals as the current demand increases.

Short-term signals

If we were to apply a very short signal burst to each of the amplifiers associated with the power supplies, the situation would be quite different. If the signal burst were short enough, the filter capacitors would maintain their full (or nearly their full) charge for the duration of the short pulse and the available voltage at the power output stages of each amplifier would be very close to the no-load value of plus and minus 50 volts. Under these circumstances, each amplifier would be able to provide a peak-to-peak signal swing of 100 volts, which would correspond to a short-term power output of 156.3 watts!

These short-term musical signals are exactly what an amplifier is called upon to reproduce when it is hooked up to speakers and fed with program sources in a "real-world" high-fidelity system. No one (at least no one we know of) spends much time listening to continuous sine-wave test signals. Yet, if we were to be guided by the continuous power ratings of the two amplifiers used in our example, one would have a rating of just over 100 watts-per-channel while the other would be rated at 144 watts-per-channel. In auditioning these two amplifiers you might well conclude that the 100-watt unit (which would undoubtedly sell for less money than the higher powered model) "sounds" just as loud as the higher powered unit before audible clipping takes place.

At the present time, the Institute of High Fidelity is completing its work on a new amplifier measurement standard. One of the most important new measurements that is being incorporated in this new standard has been given the tentative name, Dynamic Headroom. This measurement seeks to take into account the wide discrepancies that may occur between the continuous power ratings of amplifiers and their ability to deliver power over the short terms typically required during music signal reproduction. In order to simulate these short-term conditions, studies were conducted by the IHF committee regarding the actual duty-cycle and power distribution of musical signals. A test signal was arrived at which, it is felt, approximates what an amplifier must be able to handle when reproducing typical music signals. This new test signal is shown in Fig. 3. It consists of a 1-kHz signal which is at an

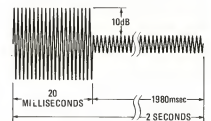


FIG. 3—NEW TEST SIGNAL for determining dynamic headroom of an amplifier. Signal consists of 1-kHz sinewaves with a 10 dB amplitude change.

arbitrary level for 20 milliseconds (twenty cycles of this signal will therefore appear) and the same frequency at an amplitude 10 dB lower for another 190 milliseconds. This complex signal is repeated, therefore, every two seconds. A portion of the test signal is shown in the scope photo of Fig. 4.



FIG. 4—NEW TEST SIGNAL as it would appear on an oscilloscope.

We decided to use this new test signal to check out the Dynamic Headroom of an amplifier which happened to be in our lab at the time this article was being written. The amplifier had a continuous power output rating of 25 watts-per-channel. To confirm this, we first ran a continuous test signal into the amplifier and adjusted our scope display so that one vertical division equalled 10 volts peak-to-peak. We reached clipping when the amplitude of the sinewaves reached 40 volts (4 divisions), as shown in Fig. 5. This corre-

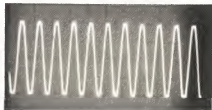


FIG. 5—CONTINUOUS POWER OUTPUT can be determined by determining the input level required to drive an amplifier into clipping with a 1-kHz input signal.

sponded to an RMS value of 14.14 volts, or just over 25 watts across an 8 ohm load.

Next, we applied a signal similar to that shown in Figs. 3 and 4. The oscilloscope's sweep rate was increased so that we might be able to examine the crests of the sinewaves during the 20-millisecond duration of the higher amplitude pulses.

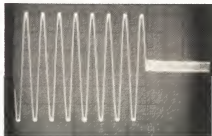


FIG. 6—OUTPUT OF AMPLIFIER that is being driven just to the point of clipping by new test signal.

Again, the gain was increased until evidence of clipping appeared, without changing the vertical sensitivity of the scope input. The results are shown in Fig. 6. Using our new test signal, the peak-to-peak amplitude of the sinewaves reached 60 volts. This corresponds to an RMS value of 21.22 volts, or a short-term power output capability of 56.27 watts!

Specifying dynamic headroom

The IHF Amplifier Standards Committee was faced with the problem of how best to specify the new measurement results. They could, of course, simply list a second power rating and call it "dynamic power." If that were to be done, however, the Federal Trade Commission requires that such a "secondary" power rating must be printed in the spec sheets (or in any advertising material) using


Understanding Dynamic Headroom

Dynamic headroom, a new addition to the Institute of High Fidelity amplifier measurement standards. Tells why amplifiers with the same rated power may perform differently under varying signal levels.

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

EVER SINCE THE FEDERAL TRADE COMMISSION issued its rule regarding disclosure of the power output ratings of audio amplifiers, manufacturers of high-fidelity amplifiers and receivers have been faced with a mixed blessing. On the one hand, the requirement that amplifier makers list the continuous power rating of their amplifiers has forced less-than-honest manufacturers to abandon such meaningless

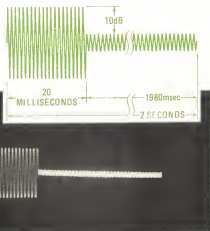power output terms as "peak power," "instantaneous peak power," "music power," "dynamic music power" and more. The continuous power rating, coupled with a statement of load impedance, power bandwidth (the frequency extremes over which the product will actually deliver its rated power) and harmonic distortion has enabled prospective buyers of audio amplifiers to compare brands



and models on a reasonably equal basis. This uniformity of specifications is all to the good.

On the other hand, it didn't take the experts long to conclude that two amplifiers that have exactly the same continuous power output rating (including the same power bandwidth and even the same rated harmonic distortion) may not necessarily deliver the same program *loudness* to identical speaker systems when fed with actual program signals. Obviously, to properly define the useful power output capability of an amplifier, more information is needed than the simple statement of "continuous power output" capability.

Power supply reserve

The reason for this can be found by examining the two power supply diagrams of Figs. 1 and 2. Note that both supplies have nominal output voltages of plus and minus 50 volts under no-load (no-signal) conditions. The alternate voltages (designated with an asterisk) are those that are present when the amplifier is delivering a large amount of current to the speaker loads. Under a full-load condition, the power supply shown in Fig. 1 delivers plus and minus 48 volts, while the power supply shown in Fig. 2 delivers a much lower output of only plus and minus 40 volts. What does this mean in terms of continuous power output capability?

Assuming that the output signal can swing over the entire peak-to-peak value of the power supply voltage, we see that in the case of the power supply of Fig. 1, a

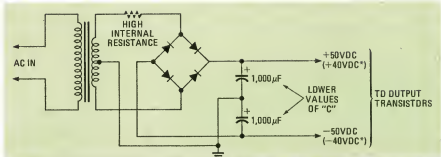


FIG. 1—POWER SUPPLY for hi-fi amplifier has large filter capacitors. There is little variation in output voltage between no-load and full-load conditions.

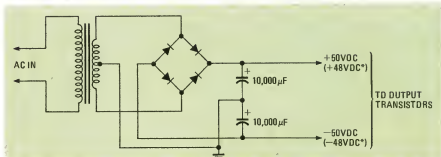


FIG. 2—POWER SUPPLY for hi-fi amplifier has small filter capacitors and a high internal resistance in either the transformer or bridge rectifiers. This supply delivers an output voltage with a wide variation between no-load and full-load conditions.

Lectrotech Model PPI-400

Peak Power Indicator

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR



CIRCLE 105 ON FREE INFORMATION CARD

THE LECTROTECH MODEL PPI-400 PEAK-POWER indicator is an accessory device intended for connection either to the amplifier output terminals or to the speaker terminals of a high-fidelity component system. It indicates instantaneous peak-power output from a stereo amplifier by means of flashing LED's, each calibrated to light at a different input voltage to the unit.

The front panel of the model PPI-400 is shown in Fig. 1. The left side of the panel contains a pushbutton POWER on/off switch. The dark-colored center of the panel contains two vertical rows of LED's, calibrated from 0 dB at the top to -30 dB for the lowest indication in each row. The bottom four LED's in each row are green, the next pair are yellow and the top two LED's in each row are red.

A selector switch on the right-hand side of the panel selects the sensitivity range of the indicators, as related to the nominal impedance of the speakers being used. For 4-ohm speakers, the six calibrated switch settings provide a power range (for 0-dB indications) from 25 watts to 600 watts-per-channel. For 8-ohm speakers, the ranges are from 12.5 watts to 400 watts; whereas for 16-ohm speakers, the power ranges from 6.25 watts to 200 watts. This arrangement demonstrates that the unit actually responds to input voltage rather than to true power input and, therefore, will not take into account any variations in speaker impedance with frequency. The device, therefore, displays errors depending upon a speaker's departure from nominal impedance at different audio frequencies.

A seventh selector switch setting permits you to calibrate the instrument to any desired 0-dB reference level other than those already provided. This switch position, labeled AUX on the panel, is calibrated by installing two appropriate resistors across two sets of terminals at the left of the rear panel that come supplied with jumpers. The jumpers are removed and resistors are substituted. You select the resistors in accordance with the formula, $R =$

TABLE 1
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Lectrotech

Model: PPI-400

OVERALL PRODUCT ANALYSIS

Retail price	\$129.95
Price category	Medium
Price/performance ratio	Fair
Styling and appearance	Good
Sound quality	N/A
Mechanical performance	Good

Comments: Certainly this accessory device does what it is supposed to do with a fair degree of accuracy. It provides an approximate indication of instantaneous peak-power output from a stereo audio amplifier. The LED indicators do not suddenly light up or go out. Rather, there is a transitional region for each LED that spans between 2 dB and 3 dB. You must decide subjectively when a given LED is really lit. A vague area of indication that is 3 dB in amplitude represents a power difference of 2:1—which can be trying when you are judging whether or not your amplifier is going into clipping or not!

In addition, by just adding a bit more circuitry and switching, the model PPI-400 could have been made to read voltages that are typical of those applied to tape-deck inputs. Thus, the unit could have served as a peak indicator to augment most cassette or open-reel tape-deck VU meters. We are told by the people at Lectrotech that such a dual-purpose unit is evidently planned, but it will undoubtedly cost more than the single-purpose model PPI-400 we tested. Presently, the minimum sensitivity of 3.13 mW across 8 ohms is equivalent to 0.16 volt, somewhat more than is usually available at the record-out jacks of most amplifiers or receivers, and greater than the amount of drive usually required by most tape-deck line inputs.

If you want to know approximately how much power you are feeding to your loudspeakers at all times, the model PPI-400 will serve that purpose, and if your hi-fi component system is fairly expensive and lacks peak-power indication, the added cost of a device such as the model PPI-400 may not seem unreasonable—especially if it prevents speaker burnout even once in the life of your stereo system.

$2\sqrt{P/Z} - 10$, where P is the desired power for 0-dB reference, Z is the loudspeaker impedance and R is the required resistor, in 1000 ohms.

This additional switch position makes it possible to calibrate and use the instrument with two monophonic amplifiers (for example, musical instrument amplifiers) even if the power-output rating of each amplifier is different (two different resistance values can be used).

Measurement and use tests

To test the model PPI-400 we hooked up a suitable amplifier with which to evaluate the unit.

Since the device is most useful in measuring short-term or instantaneous power, we used a variety of tone bursts to determine whether the LED's respond quickly enough to music-like transients. Specifically, we used the new test signal required in the dynamic headroom test of the recent IHF Amplifier Measurement

Standards (IHF-A-202). This signal consists of 20 ms of a 1-kHz test tone at full amplitude, followed by 480 ms of the same test frequency reduced by 20 dB. The signal's repetition rate is twice per second. Under these test conditions, a standard output meter reads approximately 12 dB below the full-amplitude value of the signal, while the LED's continued to read correct peak instantaneous power.

It was somewhat difficult to judge the accuracy of the device since individual LED's do not light up completely when triggered, but start dimly and then with increased signal amplitude, begin lighting up fully. The change in amplitude of applied voltage between the barely visible illumination of an LED and the full brightness of the same LED ranged from about 2 dB to 3 dB. It is possible, of course, to calibrate the model PPI-400 so that when the LED's are either barely lit or fully bright, this corresponds to the desired power level, but some eyeball judgment is necessary.

Summary

Our overall product evaluation, together with a summary of its usefulness, is shown in Table 1. The model PPI-400 is not a precision instrument, but then it is not very expensive for a device of this type. It could prove useful if you own an amplifier with higher power-output capabilities than your speakers can handle. Setting the 0-dB calibration point for the speakers' maximum power-handling value could protect the speakers against possible overdrive damage.

R-E


MANUFACTURER'S PUBLISHED SPECIFICATIONS:

Input Impedance: 20,000 ohms, minimum. **Accuracy:** ± 0.25 dB. **Frequency Response:** 20 Hz to greater than 20 kHz. **Maximum Input Power:** 1250 watts continuous at 8 ohms. **Minimum Input Sensitivity:** 3.13 mW at 8 ohms. **Loudspeaker Impedance Range:** 2 to 35 ohms. **Power Range and Impedance Combinations:** 18 plus auxiliary. **Dimensions:** 14 W \times 3 1/4 H \times 8 inches D. **Weight:** 3 1/2 lb. **Power Requirements:** 105 to 125 V, 50 to 60 Hz, 7 watts. **Suggested Retail Price:** \$129.95 (optional walnut cabinet, \$24.95 extra).

Amplifier measurements

Table 2 lists amplifier measurements made on the *model G-9000*. The amplifier delivered more than its rated output at all frequencies before significant distortion was observed. The reason for the two power readings at 20 kHz (into 8-ohm loads) in Table 2 is because we were uncertain whether Sansui wishes to rate distortion at 0.02% or 0.03% (rather an academic point, since neither level of harmonic distortion would be audible). In any event, if the figure is 0.03%, the amplifier delivers greater than its 160-watt rating even at the 20-kHz extreme; if 0.02% is really the rated specification, it falls a bit short of the 160-watt mark at the high-frequency extreme.

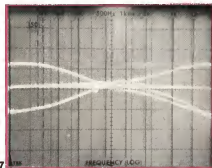We were pleased to find variable turnover tone controls on this high-powered, high-quality stereo receiver because the user then has much greater tone control capability. The range of tone controls using inner 400-Hz and 2.5-kHz turnovers is shown in Fig. 7, along



with the high-cut filter action. This filter, with its very moderate slope, clearly offers no advantages over treble-cut filters since the two curves almost coincide. Sansui could have provided a steeper slope (12 dB-per-octave) or at least raised the cutoff frequency of their high-cut filter.

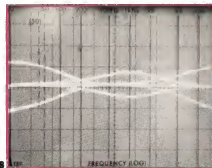


Figure 8 shows the bass and treble control range when the 200-Hz and 5-kHz turnover points are selected. Superimposed on these curves is the mid-range tone control range whose well-centered frequency provides the type of presence control action expected of it.

The loudness compensation circuit at various listening levels has a fairly typical response.

Summary

Table 3 contains our overall product evaluation along with our summary comments. We believe the Sansui *model G-9000* represents the most advanced circuit design yet seen in all-in-one receivers, and, considering what separate components offering the same quality, power and flexibility can cost, turns out to be very fairly priced. R-E

TABLE 2

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Sansui

Model: G-9000

AMPLIFIER PERFORMANCE MEASUREMENTS

	R-E Measurement	R-E Evaluation
POWER OUTPUT CAPABILITY		
RMS power/channel, 8-ohms, 1 kHz (watts)	174.8	Excellent
RMS power/channel, 8-ohms, 20 kHz (watts)	169.3	Excellent
RMS power/channel, 8-ohms, 20 kHz (watts)	158.0/162.0	See text
RMS power/channel, 4-ohms, 1 kHz (watts)	256.0	Excellent
RMS power/channel, 4-ohms, 20 kHz (watts)	232.0	Excellent
RMS power/channel, 4-ohms, 20 kHz (watts)	203.0	Very good
Frequency limits for rated output (Hz-kHz)	10-30	Good

DISTORTION MEASUREMENTS

Harmonic distortion at rated output, 1 kHz (%)	0.006	Superb
Intermodulation distortion, rated output (%)	0.009	Superb
Harmonic distortion at 1-watt output, 1 kHz (%)	0.018	Very good
Intermodulation distortion at 1-watt output (%)	0.025	Excellent

DAMPING FACTOR, AT 8 OHMS

100 Excellent

PHONO PREAMPLIFIER MEASUREMENTS

Frequency response (RIAA \pm dB)	+0, -0.5	Very good
Maximum input before overload (mV)	340	Superb
Hum/noise referred to full output (dB) (at rated input sensitivity)	78 ("A" weighted)	Excellent

HIGH LEVEL INPUT MEASUREMENTS

Frequency response (Hz-kHz, \pm dB)	3-80, 3.0	Superb
Hum/noise referred to full output (dB)	93	Superb
Residual hum/noise (minimum volume) (dB)	102	Excellent

TOTAL COMPENSATION MEASUREMENTS

Action of bass and treble controls	See Fig. 7	Excellent
Action of secondary tone controls	See Fig. 8	Excellent
Action of low-frequency filter(s)		Excellent
Action of high-frequency filter(s)	See Fig. 8	Fair

COMPONENT MATCHING MEASUREMENTS

Input sensitivity, phono 1/phono 2 (mV)	2.5/2.5
Input sensitivity, auxiliary input(s) (mV)	150
Input sensitivity, tape input(s) (mV)	150
Output level, tape output(s) (mV)	150
Output level, headphone jack(s) (V or mW)	100 mW

EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN

Adequacy of program source and monitor switching	Excellent
Adequacy of input facilities	Excellent
Arrangement of controls (panel layout)	Excellent
Action of controls and switches	Excellent
Design and construction	Very good
Ease of servicing	Good

OVERALL AMPLIFIER PERFORMANCE RATING

Excellent

TABLE 3

OVERALL PRODUCT ANALYSIS

Retail price	\$1050
Price category	High
Price/performance ratio	Excellent
Styling and appearance	Very good
Sound quality	Superb
Mechanical performance	Very good

Comments: If ever a manufacturer could boast that a receiver offers all the features and performance of high-priced separate components, Sansui has certainly earned that right with their *model G-9000*. The DC-amplifier configuration of the power section provides sound quality as good as any we have heard from the most sophisticated separate power amplifiers. To judge this quality, in our listening tests we used several mint-condition direct-to-disc recordings.

As for control flexibility, the *model G-9000* has it all; so much, in fact, that the front panel may seem somewhat intimidating on first use. Soon, however, the logical front-panel arrangement becomes familiar, and easy to use and enjoy.

Sansui was among the first to offer variable IF bandwidth for FM in a tuner, and they have extended that feature into this receiver. We found, however, that while the wide setting offers about the lowest distortion FM we've ever measured, the narrow position (useful when stations are very close together on the dial) is almost too narrow and should be avoided unless there is just no alternative for a desired incoming signal.

The well-calibrated power-output meters should insure against inadvertent overload and clipping, although that is hardly likely to happen because of the receiver's high power-output capability. Since many otherwise excellent speakers cannot handle the full power output of this receiver, prospective users are urged to check out the maximum power-handling capacity of the speakers they intend to use with it. The *model G-9000* is truly one of the best "component" systems we have ever checked.

letters that are no greater than two-thirds the size of the letters used to specify the continuous power rating. In addition, the appearance of an alternate power rating in watts might, in time, lead to the same sort of confusion that arose years ago and that prompted the Federal Trade Commission to promulgate the power rule for audio amplifiers in the first place.

The committee therefore decided that Dynamic Headroom should be specified in terms of decibels above the rated continuous power. Not only does this get around the problem of having multiple (and confusing) wattage listings for the same amplifier, but it serves to give the potential purchaser some idea as to how much louder the amplifier will sound when reproducing music signals as compared with its ability to reproduce a continuous sinewave test tone.

In the example just taken from our actual measurements in the lab, since the short-term power was 56.27 watts and the continuous power rating was 25 watts, the ratio of those two numbers is 2.25, which translates to a Dynamic Headroom of 3.52 dB. Based upon our experience with a variety of amplifiers, that degree of Dynamic Headroom is very great indeed. Generally, you can expect the Dynamic Headroom of typical audio amplifiers to range from 0 dB to around 3.0 dB. A Dynamic Headroom of 0 dB would mean that the amplifier has a very stiff power supply—one whose voltage does not vary at all from "no-signal" to full-signal conditions. An amplifier with a Dynamic Headroom of 3 dB would be one with a very "soft" or poorly regulated power supply whose voltage drops by a factor of approximately 30% when full current is delivered to the load.

Checking dynamic headroom

You can check the dynamic headroom of your own amplifier or receiver even if you lack the test equipment needed to produce the special signal we have described. All you need is an accurately calibrated oscilloscope and an audio oscillator which can apply a single-tone 1-kHz signal to the high level inputs of your equipment. First, determine the amplitude of a 1-kHz output signal that causes the amplifier to barely clip. Record the amplitude in peak-to-peak volts, as observed on the scope. Then, apply a music signal to the set (either from a recording or from an FM tuner) and observe the new clipping level, which should be somewhat greater than that obtained during the first sinewave test. Even if your scope is not calibrated, you can still determine the Dynamic Headroom of your equipment quite accurately, in dB. For example, we used still another amplifier and, without regard to its continuous power rating, we applied a 1-kHz test tone until clipping occurred. We set the sensitivity of the vertical amplifier of the scope so that this amplitude occupied four divisions, vertically (see Fig. 7). Then, applying a music signal to the amplifier, we noted that at clipping, the vertical amplitude was 4.6 vertical divisions on the scope (positive peaks were about 3/10ths of a division higher than before, and so were negative clipped peaks). These results are shown in the scope photo of Fig. 8. To calculate the Dynamic Headroom of this amplifier, divide 4.6 by 4.0 to obtain a voltage ratio of 1.15. This corresponds to a dB difference of 1.21. So, the Dynamic Headroom of this amplifier is 1.21 dB.

The concept of Dynamic Headroom is

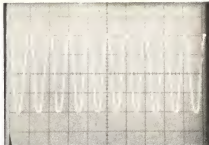


FIG. 7—AMPLIFIER'S DYNAMIC HEADROOM can be obtained by first determining the input level required to drive the amplifier into clipping with a 1-kHz input signal.

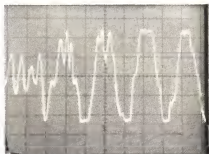


FIG. 8—CLIPPING LEVEL of program material is used to determine amplifier's dynamic headroom.

just one of the new measurement ideas which will be incorporated in the new IHF Amplifier Measurement Standards, but it is one which should help to clarify one of the seeming discrepancies which still exists when comparing the performance of similarly power-rated audio products that, under actual use, "sound different." As soon as the members of the IHF approve of the entire new standard, we will detail the other important measurement techniques incorporated in that standard in a future article.

R-E

Pioneer Electronics receives award for contribution to arts

U.S. Pioneer Electronics, a leading audio component manufacturer, was a first-time winner this year in the 12th annual "Business in the Arts" awards program, co-sponsored by *Forbes* magazine and the Business Committee for the Arts, a national organization that promotes greater business and industry involvement in the arts. The award this year was an original print by American artist Romare Bearden.

Pioneer was awarded its prize for a national campaign to raise funds for the Metropolitan Opera. Not only did the company match every dollar contributed by the general public and authorized Pioneer dealers, but obtained matching funds from the National Endowment for the Arts; this helped quadruple the original public donations. The company footed the bill for all advertising and promotional campaigns. A quarter of a million dollars was raised for the Met.

Electronic town meeting via 2-way cable TV

Upper Arlington, OH, a suburb of Columbus, recently experienced its first electron-

ic "town meeting of the air." This was made possible by Warner Cable's participatory two-way cable QUBE system, which allows viewers to express their opinions on the air on matters of public interest, such as municipal services, public utilities, etc., in their areas.

Here's how QUBE works: Town officials, broadcasting live from QUBE's TV studios, posed questions to which viewers responded by pressing a button on their home terminals, registering their opinions or criticisms. The results were then tabulated by a computer for display on home TV screens. A special hookup to the QUBE studios also made it possible for participants to phone in their own questions to the town officials. Random numbers were assigned so that no individual home was known or identified with the opinions expressed.

National satellite network transmits public service programs

This past September, the Public Service Satellite Consortium (PSSC) used Denver, CO, as the "launch site" of a new continuing education program transmitted via a communications satellite. This transmis-

sion was a pilot demonstration of the non-broadcast use of the public television satellite system.

The program was a special education presentation created for members of the American Dietetic Association who viewed it at more than 100 selected locations in eight major cities across the U.S. Pretaped portions of the program were linked up with a panel of experts in Denver, and the dietitians viewing it on screens in auditoriums, schools and hospitals could question the experts via telephone.

The signal was beamed to Western Union's communications satellite Westar I, which then retransmitted it to public television stations in Anchorage, AK, San Diego, Indianapolis, Las Vegas, Columbus, OH, Cleveland, OH, Columbia SC and Spokane, WA.

According to the PSSC, this new satellite system will connect all PBS stations by the end of 1978. Because the system allows each station to receive up to four transmissions simultaneously, this will allow PBS to transmit nonbroadcast programs for its members, more than 100 nonprofit organizations and other nonprofit groups. The system is expected to be operative by early 1979.

R-E

Hobby Computer



STATIC RAM MEMORY from Vector Graphic is designed for the S-100 bus structure. Four Motorola MC7805CP 3-terminal voltage-regulator IC's are along the right-hand edge.



TYPICAL POWER SUPPLY for hobby computers has a heavy power transformer and computer-grade electrolytic filter capacitors. The voltage regulators are mounted on the motherboard.



VECTOR model 1+ microcomputer has power supply along right side of cabinet. Cooling fan in right rear corner exhausts hot air.

The power supply is perhaps one of the most critical of all often used in microcomputer circuitry, operate from a DC supply be allowed to go above 5.6. This is the story of high-current power

MICROCOMPUTERS BUILT WITH THE S-100 BUS USE DISTRIBUTED regulation to supply +5 volts DC to the various circuits. Distributed regulation uses one or more three-terminal IC regulators (i.e., LM309, 7805, LM340-5) mounted on each printed circuit board. The main high-current power bus on the S-100 motherboard is unregulated +8 volts DC.

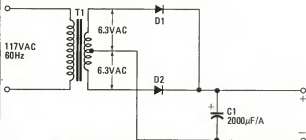


FIG. 1—SIMPLE FULL-WAVE RECTIFIER uses two diodes and a center-tapped transformer.

But certain other mainframes use +5 volts DC *regulated* on the main power distribution bus, and obtaining that type of supply at a reasonable cost is quite a chore! At current levels of around 5 amperes, you cannot use a simple three-terminal IC regulator. Finding a series-pass transistor able to handle the load current and possessing a β high enough to allow use of the simple Zener-controlled base circuit type of regulator is almost

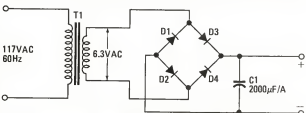


FIG. 2—BRIDGE RECTIFIER provides full-wave rectification.

impossible. In this article we will discuss several approaches to solving the problem of high-current supplies.

Pseudo-distributed system

The microcomputer kit I purchased recently uses a motherboard with the +5 volt DC and ground foil traces connected to the individual card-edge connectors. The total current demand of a fully populated motherboard is approximately 16 amperes. In trying to develop a power supply, one solution I tried with moderate success was to cut the +5-volt foil trace on the motherboard at strategic points, and then mount external three-terminal IC regulators nearby. One regulator served each section of the board. The three types mentioned earlier are suitable for current drains of 1 ampere in the TO-3 case, and 750 mA in the plastic case. The LM323 will handle 3 amperes, and the Lambda LAS-1905 will handle 5 amperes.

The pseudo-distributed system works well, but is sloppy. In some cases, this approach is made more difficult by the fact that not all motherboards are laid out in the nice straight lines of the S-100 bus! The +5-volt DC line may wander, breaking off at points, and then rejoining later on. These difficulties often force us to look at other alternatives.

Rectifiers and filters

In the regulator circuits to follow we will show only the regulator and associated circuitry, since this is where the main problem in design is. All these circuits will be preceded by a rectifier and filter circuit such as those shown in Figs. 1 and 2.

Both of the circuits shown in Figs. 1 and 2 are full-wave rectifiers, meaning that they make use of both alternations of the AC sinewave from the power mains. This type of rectifier is not only easier to filter (the traditional justification) but also results in a higher average DC output voltage, and requires less power (i.e., $V \times A$) from the transformer primary for any given load current.

The rectifier circuit in Fig. 1 uses two solid-state diodes and a center-tap transformer. The center tap is taken as the


Power Supplies



VECTOR'S VP2 ENCLOSURE permits you to design and house your own microcomputer. Card-guides are provided. Power supply can be installed in smaller compartment.



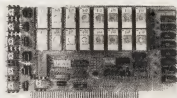RAM MEMORY BOARD from Electronic Control Technology mates with S-100 bus. Type LM340T regulator IC's are on massive heat-sink in upper left corner.



COMBINATION RAM AND ROM memory board is designed for S-100 bus configuration. Distributed voltage regulation uses six 3-terminal voltage-regulator IC's.

hobby computer components. TTL (Transistor-Transistor Logic) IC's, with a nominal level of 5 volts and a maximum level that must not supply regulation and how you can design and build your own supply.

JOSEPH J. CARR

common (or ground) terminal, while the positive output is taken from the junction of the two diode cathodes. The alternate circuit, shown in Fig. 2, is a bridge rectifier that can be made from four discrete diodes, or be purchased as a prepackaged bridge.

Almost all voltage regulator circuits require a DC input that is at least 2.5 volts higher than the rated output voltage. In our case, with +5-volts DC output, the DC input voltage should be not less than +7.5. In case you have wondered, this is probably the reason why Altair, the original S-100 bus designers, specified +8 volts for the main power bus. An ordinary 6.3-volt AC (RMS) filament transformer will deliver this potential when full-wave rectified and filtered. The filter will charge to $1.4 \times E_{RMS}$, which in this case is $1.4 \times 6.3 = 8.8$ volts. In most cases, a 6.3-volt high-current filament transformer is sufficient.

The standard 6.3-volt filament transformer is a good choice for use in a circuit such as Fig. 2 because the bridge rectifier uses the entire secondary. Keep in mind, however, that the transformer can deliver only half its rated current in the bridge configuration. In the case of Fig. 1, a 12.6-volt transformer will provide 6.3 volts AC either side of the center tap, so it is a good choice. It will deliver the same output potential as the bridge rectifier used with a 6.3-volt transformer, and will supply its rated current.

Fortunately, 6.3 and 12.6 volts AC are the filament ratings of many high-power transmitting tubes used in commercial and military transmitters. Many such transformers are still available on the surplus market, although the supply is down from its heights of only a few years ago. You should be able to save a considerable amount of money by checking the local electronic surplus outlets, ham friends (who tend to save such items), or by attending hamfests and auctions. If a push comes to a shove, or you have money to spend, then go to your local parts distributor and buy a new transformer outright. I have used several Triad types that are particularly useful because their tapped primary offers secondary AC voltages of either 6.3 or 7.5. Table 1 gives the type numbers and ratings.

The rectifier diodes or bridge-rectifier stacks should be rated to handle more current than is expected at full load, but keep in mind that they will tend to run very hot if operated at a point near their maximum ratings. It is preferable to select diodes with a 25 or 50 percent margin. For example, for a 20-ampere power supply select a 25- to 30-ampere diode. Also keep in mind that the minimum peak inverse voltage (PIV) rating must be not less than 2.82 times the applied RMS voltage. This is not too much of a problem in +5-volt circuits operated from 6.3-volt transformers, but is very definitely a factor at higher voltages. You cannot, for example, use a 25-volt PIV rectifier in a 12-volt DC supply!

TABLE 1—TYPICAL FILAMENT TRANSFORMERS

Triad No.	Secondary voltage	Amperes
F-22U	6.3VAC	20
F-24U	6.3/7.5 VAC	8
F-28U	6.3/7.5VAC	25
F-56X*	25.2 VAC	2.8

*Ideally suited to making the ± 12 volt regulated supplies needed for most microcomputers. Use a fullwave bridge and the transformer center tap to form two halfwave bridges. This supply will deliver up to 1 ampere at each voltage.

Capacitor C1 in Figs. 1 and 2 should have a capacitance of not less than 2000 μ F-per-ampere of load current. In a 20-ampere supply, then, the filter capacitor should be at least 40,000 μ F. It should have a DC working voltage rating of at least 15 volts (WVDC). I used an 80,000 μ F/15 WVDC capacitor in testing these circuits with a 15-ampere load. The 2000 μ F-per-ampere spec is a *minimum*, not an *optimum*, rating.

The 5-volt, 5-amp supply

The Lambda Electronics (515 Broad Hollow Rd., Melville, L.I., N.Y., 11746) model LAS-1905 is one of the most powerful



SPEAKER

how various types

*Recently audio engineers have found that ordinary
that a loudspeaker sounds. Newly developed*

THERE IS A GROWING BODY OF OPINION IN some audio circles that speaker cables have been neglected when considering the performance of a high-fidelity system. However, when one prominent speaker engineer was asked what part he felt cables contributed to speaker performance, his answer was: "Ever since I discovered that no one—not you, not I—can hear the difference between 10-kHz sinewaves and squarewaves, I've been cynical of the claims made by the ultra-wide band and no-phase-shift advocates." He was referring to the fact that research has shown that even the best-quality conventional speaker cable cannot pass a squarewave, and causes phase rotation at high frequencies.

Today's thinking has it that the inductance and capacitance of lamp cord (zip cord) should not present a problem in today's audio systems. However, it is generally conceded that for very long runs of speaker wire that is connected to low-impedance speakers, it might be necessary to artificially lower the cables' typical impedance. Therefore, if we assume there is no significant magnetic coupling to other cables capable of absorbing power in low-impedance circuits, there is no reason to believe that speaker cable should significantly affect frequency response.

If you visit some hi-fi stores today, you'll find an increasing number of so-called "super cables," such as Disc Washers' *Smog Lifters*, Polk's *Sound Cables*, Audio Source's *High Definition Cables*, M & K's *Mogami* cables, or the Fulton line of cables. These represent several different types. For instance, 140-strand braided cable (*Smog Lifters*); 10 pairs of braided insulated wires (Audio Source's *High Definition*); a stacked coaxial cable (M & K's *Mogami*); the Fulton cable, which is a very large paral-

lel multishroud type, or the Polk cable, which is also braided with a very fine intertwine. The price of these cables runs from 50 cents-per-foot to \$1.50-per-foot and more, making them considerably more expensive than conventional zip cord that costs 15 cents or less per foot. Zip cord is usually recommended by most audio stores and industry authorities.

It is stated in a typical amplifier instruction manual that No. 18 lamp cord is sufficient for normal lengths (to about 30 feet) between speaker and amplifier. However, No. 16 wire is generally recommended depending on distance. A leading speaker manufacturer has prepared a recommended connection-wire chart that is shown in Table 1.

The wire lengths listed in Table 1 were calculated on a maximum audible coloration of ± 0.5 dB. Following the guide lines provided, the most discerning listener will be unable to detect any coloration introduced by the speaker wire. Most listeners will not notice any effect even if wire lengths are increased as much as 50%.

Audio critics like Leonard Feldman, *Radio-Electronics'* Contributing High-Fidelity editor, have stated that the

damping factors of a good amplifier can be practically eliminated by a poor hookup to the speakers, and you should play it safe by using heavy wire and making good connections. Even the finest cables can be rendered ineffective with poor connections.

Speaker designer Roy Cizek has emphasized in a series of articles and speeches to audio groups that "even the 'heavy' gauges No. 14 and No. 16 lamp cord are often insufficient." Mr. Cizek discovered that even small amounts of resistance can affect frequency response by destroying the effective damping of the amplifier-speaker system. He also pointed out the effects of a speaker-line fuse, and recommended using No. 12 or No. 10 wire.

Both Mr. Feldman and Mr. Cizek have pointed out that using heavier speaker wire should not be just the concern of the audiophile trying to extract the last bit of performance out of a hi-fi system. Most audio systems sold have 25 watts of amplifier power or less, and combined with a low-impedance speaker, certain wire lengths may throw away up to 30% or 40% of the amplifier power. As Mr. Cizek states, "contrary to common practice, it can be especially important to use heavier wire with smaller amplifiers or receivers, since they have low power output and low damping factors to begin with."

What the advocates of better cables point out is that many speakers are designed to provide good efficiency and transient response when effective damping is high. The low internal impedance of today's modern transistorized amplifiers reduces the amplifier's damping capability. With a low damping factor, the speaker continues to vibrate after the signal is cut off, which results in muddiness and overhang. Good speaker damp-

TABLE 1—Recommended Connection Wire

Maximum wire length (ft)	Wire gauge
30	18 gauge, zip cord (or two-conductor wire)
45	16 gauge, two-conductor wire
70	14 gauge, two-conductor wire

CABLES affect sound

speaker cables can adversely affect the way cables of unique construction solve the problem.

HARRY MAYNARD

ing plays the same role as a shock absorber on a car, preventing the suspension system from overscattering on a bumpy road. The damping factor of a good amplifier can be critical to reproducing sharp, clean transients and to the integrity of the bass.

Those who champion the new super cables claim that the damping factor can be rendered ineffective because the speaker impedance can be increased by up to two or three measurable ohms by using zip cord. The goal is to keep the impedance of the speaker cable low.

The damping factor is defined as the ratio between speaker impedance and amplifier output (or internal) impedance. Mr. Cizek's recommendation of No. 12 or No. 10 wire is based on the assumption that "if you decrease the effective damping factor by using a small wire and fuse in the line you tend to produce peaks in the frequency response corresponding to those in the impedance curve as well as poor response and increased ringing." (See Fig. 1.)

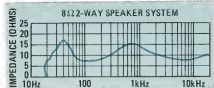


FIG. 1—SMALL WIRE DECREASES the effective damping factor and produces peaks in the frequency response.

Now the plot thickens. On several trips to Japan I discovered that leading Japanese companies presently offer for sale super cables of varying configurations; for example, J.V.C.'s *Super Cord* (sold only in Japan, not in the U. S.). You will also find Pioneer cable and several other brands. The merits of various cables is a topic of much discussion among Japanese

audiophiles, who are a match in their enthusiasm for high-quality audio with any audiophiles in the world. Much of the advanced research on the effect of speaker cable on hi-fi systems has been done in Japan.

Using a pair of J.V.C. *Super Cords*, my not-too-golden ears detected a significant improvement in sound quality coming through my speakers as compared with the No. 16 wire I had been using. I have since experienced the same improvement in sound quality with a wide variety of super cables compared with conventional cables.

Research conducted by J.V.C. showed that conventional cable could not pass a 100-kHz squarewave and that there was phase rotation. In addition, the magnetic fields of wires running parallel to each other set up what is known as self-inductance. Parallel wires create phantom channels to each other and round off high frequencies. In tests, several researchers have discovered this results in a loss of audio articulation.

In discussing the merits of super cable and various experiments conducted by J.V.C. and other electronics manufacturers, several leading Japanese executives admitted that there was much that the audio industry has yet to learn about the complex interfaces of different speaker cables and amplifier-speaker combinations. To condemn certain amplifiers because they do not perform properly with certain speakers is similar to condemning certain high-performance cars when given improper fuel—it is an unfair judgment.

Perhaps the most extensive research was performed by Kenwood in Japan in developing their *model L-07M* amplifier and *model L-07C* preamplifier. Discovering the effects of "the neglected cable," as described by Kenwood engineers, oc-

curred quite by chance. Kenwood feels that the super cables "have yielded improvements in sound quality on account of their superior transmission qualities," but this is only part of the picture. A speaker cable has to be considered an extension of the amplifier.

The problem is carefully defined and fully explained in the 47-page owners' manual (No. 7454859-0084-00) for the *model L-07M* amplifier and *model L-07C* preamplifier system. For those who wish to delve deeply into the complex interface problem of speaker/wire/amplifier, I strongly recommend getting this manual. We can only summarize its main points here.

Kenwood engineers, using very elaborate testing techniques, found that the speaker-cable impedance plays a significant role in high-frequency response and that the DC resistance contributes significantly to distortion (see Fig. 2). Furthermore, they claim that there is "surprisingly large distortion at the speaker inputs that is caused by speaker cables of even high quality and emphasizes the importance of solving this problem." (See Fig. 3.)

The importance of the neglected cable was discovered by measuring various energy losses for different lengths and kinds of cables. The greatest losses, even when using the best cables, could be held to from 0.5 dB to 0.6 dB below 10 kHz but there were still problems above 10 kHz. As described by Kenwood engineers, "when we made actual listening tests, we sensed there was something missing. It was like a bucket with a hole near the top and performance never went above the level of that hole."

"So our engineers devised a new test using a 30-kHz tone burst and measuring cable performance at the speaker terminals. They found that although the pulse



signal was perfect, there was a deformation of the waveform. The difference in wave height and overshoot is actually caused by the counter-electromotive force from the speaker, the result of greater resistance and weaker damping of the long cable. Fundamentally, even very low distortion, which cannot be measured, can be detected by our sense of hearing."

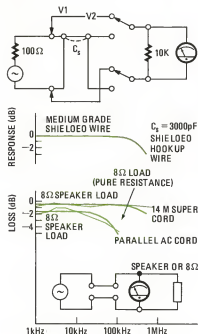


FIG. 2—SPEAKER-CABLE IMPEDANCE has a significant effect on high-frequency response.

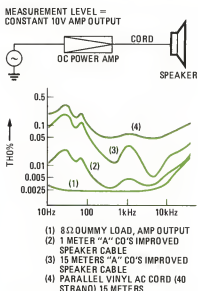


FIG. 3—SPEAKER CABLE CAN CAUSE surprisingly large distortion at the speaker inputs.

The most disturbing finding was that the amplifier should ideally be located much closer to the speakers—this is hardly reassuring for the millions who can't or find it inconvenient to do so. The farther the speaker is from the amplifier the slower the slew rate.

Obviously, to do away with the speaker

TABLE 2—Comparison of Audio Cable and Speaker Cord

	Audio cable	Speaker cord
Role	Voltage transmission	Power transmission
Transmitting impedance	10 ohms ~ 1000 ohms	Almost zero
Load conditions	20 ohms ~ 100,000 ohms. Changes somewhat with frequency and is constant without regard to signal level; slight input capacitance only; no reactance.	Indication 4~14 ohms. Changes considerably with frequency; changes with signal level; reactance component is large and complex; counterelectromotive force produced by speaker.
Effect on performance	Small	Large
Effect on tonal quality	Small	Large
Change with length	Small	Large
Extraneous induction	Easy	Difficult
Effect of cord characteristics	Since the load conditions other than component C are large, effect is small.	Components L, C and R have a large effect.

Note: In the past the quality of the system was not improved while pursuing the characteristics on the amplifier side because the dynamic characteristics with the speaker connected such as these were not considered. As shown in Fig. 7, the deterioration in distortion when the speaker is connected exceeded our imagination.

cable is impractical. Kenwood found however that their specially developed cable (not sold in the U. S.) could be used up to one meter (3.25 feet) from the speaker system, with virtually no effect on tonal quality. On the other hand, the audio cable between power amplifier and control amplifier can be long since it is merely a signal transmission line (see Table 2). I know some people who have suffered from RF problems, which they claimed was only eliminated by using specially constructed (expensive) audio cables like Verion, who might suggest that audio cables are important too. But that's another subject.

The Kenwood solution is obviously directed at the perfectionist audiophile (assuming you agree with their analysis of the problem). There are alternative solutions if you agree that the problem of transmission losses does exist and can be heard. If you don't like the price of the super cables, for less cost you can use the heaviest zip cord you can find, if your amplifier is not bothered by capacitance problems. Don't be afraid of reducing the size of the wire at the speaker terminals (by no more than half) so it will fit into spring-loaded speaker or amplifier terminals. But be careful, since the total resistance of the length of the wire must be considered.

If you believe that there is a problem of self-inductance, you'll usually find that the super cables are sold on a money-back basis. So if you don't hear a difference you can return them. Most of the special cables are sold by specific lengths and several have special tip ends that allow you to make excellent uniform connections.

For example, Disc Washers' *Smog Lifters*, shown in Fig. 4, have special plastic Y-finished tip ends that resist poten-

tial shorting, these cables sell for \$1.40-per-foot.

The M & K *Mogami* cable (sold for \$1.50-per-foot) must be debraided, and should not be tinned if splicing is neces-



FIG. 4—DISC WASHERS' *Smog Lifter* cables have special plastic tips.



FIG. 5—M & K *MOGAMI* cable must be debraided; no tinning before splicing.

sary. (See Fig. 5.) A firm connection between the wire ends to be joined should be made before soldering. You are also warned to avoid speaker switches,

continued on page 93

How To Design Digital Circuits

Part 1—With digital circuitry becoming an increasingly important factor in our everyday lives, it's time that we learn how to design logic circuits.

Get in on the start of this series as the author discusses digital logic design—beginning with Boolean algebra and Karnaugh maps.

JERRY WOOLSEY

TODAY'S ELECTRONICS HOBBYIST HAS available to him a previously undreamed-of assortment of hardware for his projects. Whereas 15 or 20 years ago electronics magazines ran construction articles on simple two- or three-tube circuits, using point-to-point wiring, the projects of today consist of computer CPU boards and computer terminals on complicated double-sided PC boards. Digital circuits are now appearing in almost everything electronic, including "linear" applications such as tuners, TV sets and synthesizers.

To enjoy fully the electronic technology of today, a hobbyist needs to know not only how to bias transistors and match impedances, but also how to analyze and design digital circuits. Although most experimenters can do this using brute-force methods, *there are some fairly simple methods for reducing the number of gates in*, and hence the complexity of, a digital circuit.

Digital electronics is the realization of Boolean algebra, and some knowledge of it is required to design a digital circuit. Since the subject of Boolean algebra has been covered in magazine articles as well as in many textbooks, it is assumed the reader has a fair knowledge of it, and is able to write his desired function in both equation and truth-table form. In this article, we will see how to apply the fundamentals of Boolean algebra to construct both parallel and series circuits from a truth table, and then *reduce the gates to the minimum needed*. Throughout this article, the AND function will be

implied between two variables if no operator is given between them, i.e., $x \cdot y$ will be written simply as xy .

Combinational switching circuits

A *combinational switching circuit* is a digital circuit whose output at any time is dependent only on its input at that time, regardless of any previous input or output. Thus, no "memory" circuits are included. (A flip-flop is considered a memory circuit.) The first part of this article is concerned only with these circuits.

A Boolean equation, no matter what form, can always be reduced or expanded to give an equation in either a sum-of-products (S-P) or product-of-sums (P-S) form. In the S-P form, the equation is an OR (sum) of several AND (product) groups. In the P-S form, the equation is an AND of several OR groups. As an example, take the following equation:

$$a = x(y + z) + y \quad 1)$$

This can be expanded by multiplying through the x to get

$$a = xy + xz + y \quad (S-P) \quad 2)$$

which is in S-P form, or may also be written in P-S form as

$$a = (x + y + z)(x + y + \bar{z})(\bar{x} + y + z) \quad (P-S) \quad 3)$$

A primitive implementation of equation 1 is shown in Fig. 1, using the S-P form of the equation. So we pick up the IC data book and notice one peculiar thing: almost all the gates available are NAND, with several AND, but few OR and NOR types. Why should this be so when most functions are written as strictly AND

and OR? To understand why, we can apply DeMorgan's theorem to equation 2. This theorem states that if we invert the individual members of one side of an equation, then change the signs between members from AND to OR and vice-versa, then invert the entire side of the equation, the equation is still true. To illustrate, let's apply this theorem to equation 2. First, we invert the individual members to obtain

$$a = \overline{xy} + \overline{xz} + \bar{y}$$

Now we change the signs between members and get

$$a = \overline{xy} \cdot \overline{xz} \cdot \bar{y}$$

Finally inverting the entire string, we get

$$a = \overline{\overline{xy} \cdot \overline{xz} \cdot \bar{y}}$$

This says that to obtain the result a , we NAND x and y , NAND x and z , INVERT y , and NAND the three results. Figure 2 shows the logic circuit. Thus, the NAND gates can perform the AND and OR functions. When a group of NAND gates feed another NAND gate, the first gates perform an AND function, and the gate they feed performs the OR function on each AND'ed group. We thus only need to keep a supply of NAND gates to realize any equation in S-P form. In this case, an extra inverter is needed, but inverted variables are often already available from another output, and even if not, this could be performed by a NAND, keeping the three input gates on one package.

It should be noted that the P-S form can be implemented in circuit form by using NOR gates, the first input gates

perform the OR function, and the second set of gates perform the AND function. However, P-S forms can always be expanded to S-P forms, so the remainder of the article will deal only with S-P forms.

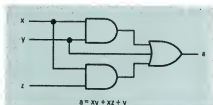


FIG. 1—LOGIC CIRCUIT that performs the Boolean algebra expression shown.

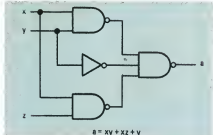


FIG. 2—NAND GATES can be used to perform the same function as shown in Fig. 1.

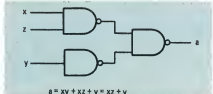


FIG. 3—SIMPLIFIED LOGIC CIRCUIT is equivalent to circuit shown in Fig. 2.

Using the theorems of Boolean algebra, it can be seen that equation 2 can be reduced to:

$$a = xz + y$$

This means that the circuit shown in Fig. 3 is equivalent to the one shown in Fig. 2. Obviously, this is much simpler, and can be done on only one IC.

Reduction of mathematical expressions by Boolean algebra theorems is tedious and often hit-and-miss. To alleviate the problem, we turn to a tool that eliminates much of the work.

The Karnaugh map

The Karnaugh map is simply a rearranged truth table that can readily give valuable information for circuit design and reduction. There are 2^n boxes in the map, where n is the number of inputs to the circuit. Each row and column is

numbered in binary, and the value in each box is the output of the circuit when the coordinates of the box are the input. The numbering of the columns starts at the left at zero, and is arranged such that the number of the next column to the right differs in only one bit position. Thus, 00 is followed by 01, which is followed by 11, which is followed by 10. The rows are numbered similarly. Figure 4 illustrates the numbering and the corresponding decimal coordinates of the boxes for functions with two, three and four inputs. Beyond four inputs, the Karnaugh map becomes too cumbersome, so other methods have been designed for these situations.

As an example, suppose a three-input circuit with inputs x , y and z were to produce a logic-1 output when $x = 0$ and $y = z = 1$. Then we would enter a 1 into the box numbered 3 in Fig. 4-b ($xyz = 011 = 3$). If a zero were to be produced when $x = y = 1$ and $z = 0$, the box numbered 6 would contain a zero. In certain cases, such as BCD circuits, some input combinations are meaningless (1010 is not a BCD number). In these instances, we enter a "d" in the appropriate box to indicate a "don't-care" condition. This tells us the output may be either 0 or 1 with the given input, since that input would never occur. This may be used to further aid in circuit reduction.

Figure 5-a shows the truth table for equation 1, and Fig. 5-b shows the Karnaugh map derived from it.

Now we come to the interesting property of the map. By definition of the structure of the map, any two adjacent boxes (horizontally or vertically, but not diagonally) differ in coordinates, i.e., in input conditions, by only one bit. For example, the boxes where $(x = 0, y = z = 1)$ and $(x = z = 0, y = 1)$ are adjacent, and differ in coordinates in only the z -input. This property also holds when "wrapped-around," i.e., the top right-hand box ($x = z = 0, y = 1$) is adjacent to the top left-hand box ($x = y = z = 0$), since they differ only in the y -bit of the coordinate. The same holds true for vertical wrap-around. Two of these adjacent boxes are said to form a 1-cube, since there are 2^1 boxes in the cube.

Now refer to Fig. 5-b. If we take two adjacent boxes that contain a 1, for example $(x = z = 1, y = 0)$ and $(x = z =$

$= 1$), we find that the output of the circuit must be a 1 whenever $x = z = 1$, independent of the value of y . That is, whenever xz is true, the equation is true. Similarly, box $(x = 0, y = z = 1)$ and box $(x = z = 0, y = 1)$ are adjacent and contain ones, so we see that the output is true whenever $x = 0$ and $y = 1$, independent of z . Thus, xy being true will cause the equation to be true, or a 1 to be output. Taking all combinations of two adjacent boxes, both of which contain a 1, the following equation is derived

$a = xz + xy + xy + yz + yz$ which is equivalent to equation 1, but is obviously not reduced. The reason for this is that several conditions for an output have been duplicated by more than one term of the equation. For example, if $x = y = z = 1$ is entered, the three terms xy , xz and yz will all be true, causing the output to be true, but it is only necessary to have one term true to cause the output to be true. Thus, we have redundant members in the equation. If we take only three adjacent sets of boxes to cover all the 1-outputs, we can obtain the equation

$$a = xz + \bar{x}y + xy$$

Now all the boxes containing a 1 have been covered by at least one of the terms of the equation, which means that the equation is a true representation of the truth table. But the equation is still not completely simplified. If we look at the 1-cube (two adjacent boxes) consisting of $(x = 0, y = z = 1)$ and $(x = z = 0, y =$

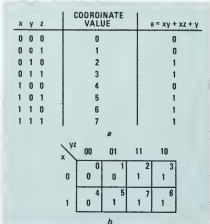


FIG. 5—TRUTH TABLE for equation $a = xy + xz + y$ is shown in a and resulting Karnaugh map derived from the truth table is shown in b.

1), and the 1-cube consisting of $(x = y = z = 1)$ and $(x = y = 1, z = 0)$, we see that the output of the function is always 1 whenever $y = 1$, regardless of the value of x or z . Thus, we have formed a 2-cube (2^2 boxes), and have found that $y = 1$ satisfies the conditions for generating a logic-1 output for each of the four boxes. Note that, in looking at the coordinates of each of these boxes, y is the only coordinate that does not change, and is always 1. We need now to cover only one more box where a logic-1 output is to be generated, box $(x = z = 1, y = 0)$. To do this, we

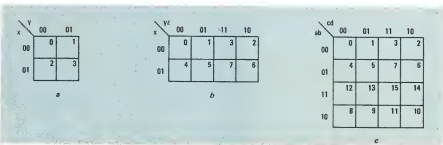


FIG. 4—KARNAUGH MAPS are used to simplify logic circuits. A Karnaugh map for a 2-input circuit is shown in a, a 3-input circuit is shown in b and a 4-input circuit is shown in c.

could simply say we need $\bar{x}yz$ to be true for the output to be a logic 1, but we have another adjacent 1-labeled box ($x = y = z = 1$) and if we use this to form a 1-cube, that term of the equation reduces to xz , since a 1-output is independent of y if x and z are 1. Thus, we obtain

$$a = y + xz$$

as our final equation, and implement it as shown in Fig. 3.

When "d" (don't-care) outputs are specified, these are included as 1-outputs if it enables us to make larger cubes with other 1-outputs, hence simplifying the equation, or as 0-outputs if they are not used in making larger cubes.

Even larger cubes may be found in four-input functions. A 1-cube is two adjacent boxes containing either a 1 or "d"; a 2-cube is two adjacent 1-cubes (i.e., a 2×2 box or 4×1 horizontal or vertical row); and a 3-cube is two adjacent 2-cubes (i.e., a 4×2 horizontal or vertical box). If a map consists only of 1- and d-labeled boxes, the function is always true, or a constant 1.

The step-by-step procedure for circuit reduction, then, is as follows:

- 1) Draw the truth table, and fill in the boxes of the Karnaugh map with a 1, 0 or d, using the inputs as coordinates and the outputs as box entries. For example, see Figs. 6-a and 6-b.
- 2) Examine the map for any 3-cubes, i.e., a 4×2 box containing no zeroes. Don't forget to check for possible wrap-around. In Fig. 6, a 3-cube is formed by decimal coordinate boxes 0, 1, 2, 3, 4, 5, 6 and 7 (see Fig. 4-c). The coordinates $abcd$ of these boxes are examined, and it is found that b , c and d take on all

values (0 and 1) while a is always 0. Thus, when $a = 0$, the output is always 1 independent of b , c and d , so one term of the final equation is simply \bar{a} . Place a check in each of the boxes of this 3-cube to indicate that they have been covered. When the coordinates of any of these boxes are input, the output will be 1 simply because \bar{a} is 1. The map now appears as in Fig. 7-a.

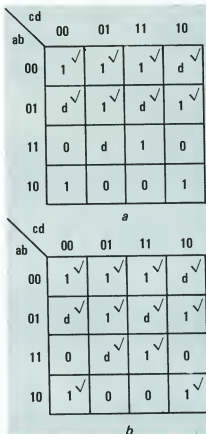


FIG. 7—KARNAUGH MAPS are reduced by first looking for a 3-cube (4×2 box containing no zeroes). When a 3-cube is found, check the individual boxes as shown in a. Next, look for 2-cubes and check these boxes as shown in b.

- 3) Examine the map for any 2-cubes, that is, any 2×2 or 4×1 box containing no zeroes, and at least one 1-labeled box not yet checked. In our example, decimal boxes 5, 7, 13 and 15 form such a cube. Examining the binary coordinates of these boxes, we find that b and d are always 1, while a and c may take on any value. Thus, our second term of the equation is bd , giving $f = \bar{a} + bd$.

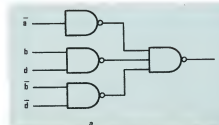


FIG. 8—LOGIC CIRCUIT is derived from reduced Karnaugh map and is shown in a. Inverter can be eliminated as shown in b.

bd so far. Check off the boxes covered by the second term. Check for more 2-cubes. In the example, we have another 2-cube that is not so obvious, due to wrap-around. This is the cube containing decimal boxes 0, 2, 8 and 10. From the binary coordinates, we find b and d are always 0, while a and c can take on any value. Thus our next term for an output of 1 is $\bar{b}\bar{d} = 1$, and our function is now $f = \bar{a} + \bar{b}\bar{d} + \bar{b}d$. Check off the boxes covered. The map now looks like Fig. 7-b.


- 4) Examine the map for any 1-cubes, i.e., two adjacent boxes each containing a 1 or a d that also contains one 1-labeled box not checked. Write down the nonvarying coordinates as a term of the function, and check for more 1-cubes. No 1-cubes remain in the example.
- 5) If any 1-labeled boxes remain unchecked, write down their coordinates as a term of the function. For example, if the box with coordinates ($a = 0$, $b = c = d = 1$) contained a 1 but was not yet checked off, we would write the coordinates as $abcd$ and insert it as a term in the equation. At the completion of this step, all boxes with a 1 in them should be checked off.
- 6) By inspection, make sure no cube is completely covered by other cubes. Each cube, no matter what size, must contain at least one 1-labeled box not contained in any other cube. If it does not, discard its corresponding term from the equation.
- 7) OR all the terms derived above to get the final reduced function. In our example we get:

$$f = \bar{a} + bd + \bar{b}\bar{d}$$

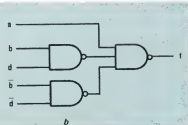- 8) Feed each term into a NAND gate, and feed the outputs of the NAND gates to another NAND gate. The circuit is complete. See Fig. 8-a.


In searching for cubes to cover an unchecked 1-labeled box, the largest possible cube should be chosen, even if it covers other boxes already checked, so that the number of inputs to each gate is minimized.

Note that Fig. 8-a has \bar{a} as an input that simply gets inverted before going to the output gate. Instead of this, it would be simpler to feed a directly to the output gate, as in Fig. 8-b. Also note that the



a	b	c	d	OUTPUT	DECIMAL
0	0	0	0	1	0
0	0	0	1	1	1
0	0	1	0	d	2
0	0	1	1	1	3
0	1	0	0	d	4
0	1	0	1	1	5
0	1	1	0	1	6
0	1	1	1	d	7
1	0	0	0	1	8
1	0	0	1	0	9
1	0	1	0	1	10
1	0	1	1	0	11
1	1	0	0	0	12
1	1	0	1	d	13
1	1	1	0	0	14
1	1	1	1	1	15

a

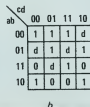

b

FIG. 6—TO SIMPLIFY a logic circuit, first draw a truth table that represents the circuit function as shown in a. Next, a Karnaugh map is derived from the truth table as shown in b.

output of the gate fed by bd cannot be used as input $b\bar{d}$ to the gate below it since $b\bar{d} \neq bd$.

As was noted earlier, the Karnaugh map method is too difficult beyond four inputs. The designer has to start considering mirror-images, and mistakes are easily made. It also does not reduce the circuit fully if multiple outputs are desired, as in a BCD to seven-segment decoder. Fortunately, there is another fairly simple method to use in these cases.

Quine-McCluskey method

The Quine-McCluskey method works on the same principle as the Karnaugh map, but is performed in tabular form. As an example of this method, we will construct a circuit to produce a 1-output, called f , whenever a 2-bit number A , whose bits are designated as a_1 and a_2 , is larger than a 2-bit number B , whose bits are b_1 and b_2 . The truth table for this function is given in Fig. 9.

a_1	a_2	b_1	b_2	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

FIG. 9—QUINE-McCLUSKEY METHOD is used when a circuit with four or more inputs must be designed. First a truth table describing the circuit function is generated as shown.

NO. OF 1-BITS	INPUT (DECIMAL EQUIVALENT OF $a_1 a_2 b_1 b_2$)
1	4 8
2	9 12
3	13 14

FIG. 10—ADJACENT BOXES and cubes are determined in a table generated from the truth table shown in Fig. 9.

The Karnaugh map obviated adjacent boxes and cubes. In the Q-M method, we write down a table to help show adjacency (see Fig. 10). The decimal value of each set of inputs that will generate either a 1- or don't-care output is listed in ascending order in groups according to the number of 1-bits in the input. For example, $A = a_1 a_2 = 10$ and $B = b_1 b_2 = 01$ produces a 1-output, and the number of

1-bits in A and B is two, so a 9 ($a_1 a_2 b_1 b_2 = 1001$) is placed in the 2-bits group. Within each group, the decimal inputs are listed in ascending order. It can now be seen that two inputs producing a 1-output are adjacent, in the same sense as in the Karnaugh map, if three conditions are met:

- 1) The number of 1-bits of each input differs by exactly one.
- 2) The decimal input with the smaller number of 1-bits must be smaller than the input with the larger number of 1-bits.
- 3) The difference of the two decimal inputs must be a power of two.

According to condition 1, inputs listed in the 3-bit group can only be adjacent to inputs in the 2-bit or 4-bit groups; inputs in the 1-bit group can only be adjacent to inputs in the 0-bit or 2-bit groups, etc. This is consistent with the definition of adjacency being a difference in only one bit of the input.

According to condition 2, the decimal input 4 may be adjacent to decimal input 12, since 4, having fewer 1-bits than 12, is smaller than 12. If, for example, the decimal input 3 produced a 1-output, it would be placed in the 2-bits group, but could not be adjacent to 4, since it has more 1-bits but is less than 4. This would cause more than one bit in the input to be different.

Condition 3 is obvious, since only one input bit may differ for adjacency. If the difference of the two numbers is not a power of two, more than one bit differs.

NO. OF 1-BITS	INPUT	1-CUBES
1	4 ✓ 8 ✓	4,12 (8) 8,9 (1)
2	9 ✓ 12 ✓	8,12 (4) 9,13 (4)
3	13 ✓ 14 ✓	12,13 (1) 12,14 (2)

FIG. 11—SIMPLIFICATION starts by listing the 1-cubes.

We now use these rules to make a third column, consisting of a list of adjacent boxes, or 1-cubes. We take the first input number in the table, 4, and check it for adjacency with the entries in the next bit group. Box 4 is not adjacent to 9, since the difference, 5, is not a power of two. Box 4 is, however, adjacent to 12, since the difference is 8, and 4 is less than 12. Thus, we enter into the third column with the numbers 4 and 12 together, with their

difference in parentheses (see Fig. 11). Since the inputs 4 and 12 have been covered by a higher cube, we place a check next to them in the column labeled input.

The input 4 cannot be adjacent to any other bit group, so we look at input 8. Box 8 is adjacent to 9, since the difference is a power of two, so we enter the numbers and difference as a 1-cube and place a check next to the 8 and 9 inputs to indicate they have been covered by a higher cube. Box 8 is also adjacent to box 12, so we repeat the process for them. Since we are through checking the 1-bit group, we place a line under 8,12(4) in the 1-cube column and start checking the 2-bit group. Box 9 is adjacent to box 13 but not to box 14. Box 12 is also adjacent to box 13, as well as 14, and we are finished creating 1-cubes. The 1-cube column now contains a list of all the possible 1-cubes that could be extracted from the Karnaugh map. Since all the inputs in the input column have been checked off, they are all contained in higher cubes.

We now have two groups of 1-cubes, and use these to form 2-cubes. The same conditions hold for forming adjacent cubes, except now the numbers in parentheses must also match. Looking at the first 1-cube entry, 4,12(8), we see that it is not adjacent to any 1-cube in the second group, since none have an 8 in parentheses. Going to 8,9(1), we find an entry, 12,13(1) in the second group that has the same number in parentheses. Since the difference of 8 and 12 (or 9 and 13) is also a power of two, and 8 is less than 9 and in a lower group, we enter this in the next column as a 2-cube, and indicate both the first and second differences in parentheses. The two entries that formed this cube are checked, since they are covered by the higher cube (see Fig. 12).

Another entry, 8,12(4), is adjacent to the entry 9,13(4), so it is entered as a 2-cube and the separate 1-cubes are checked. However, this is identical to the previous 2-cube and is thus stricken. No further adjacency is found, and there are no more groups to check for adjacency, so the checking of the 1-cube column is complete.

We now go to the next column and continue until no adjacencies are found. The same rules are followed in each column, checking each entry against each

continued on page 92

NO. OF 1-BITS	INPUT	1-CUBES	2-CUBES
1	4 ✓ 8 ✓	4,12 (8) 8,9 (1) ✓ 8,12 (4) ✓	8,9,12,13 (1,4)
2	9 ✓ 12 ✓	9,13 (4) ✓ 12,13 (1) ✓ 12,14 (2)	
3	13 ✓ 14 ✓		

FIG. 12—ALL 2-CUBES are listed. Second 2-cube is crossed off since it is covered by first entry.

REMOTE TELEPHONE EAR— Listen via Long Distance

*This device—the fourth in a series of phone gadgets—
lets you monitor sounds in your home or office
when you call your telephone from a remote location.*

JULES H. GILDER

IN THE APRIL AND MAY 1977 AND MAY 1978 issues, we showed how to construct add-on telephone accessories that let you turn on and turn off various household appliances by remote control, build a hands-off telephone amplifier and assemble an autodialer and cassette interface that dialed authorities or neighbors in case of a fire or intruders in your home.

If you were interested in these items, you'll flip over the Remote Ear that lets you dial your home phone and then listen for the sound of running water or a radio that was inadvertently left on. Or maybe you just want to check your house and see that everything is quiet and no one has broken into it.

The Remote Ear is an adaptation of the Teleswitch circuit (April 1977). It automatically connects a microphone and amplifier to the telephone so that you can monitor a remote location. As you will quickly see from the schematic, the Remote Ear uses the same type of signal detectors as the Teleswitch. However, instead of having controlled outlets to turn devices on and off, the Remote Ear has a small three-transistor amplifier connected to it.

This amplifier is identical to the one described in the Speakerphone circuit (May 1977). Its signal is very clear and audible. The output of the amplifier, which is located in the area that you want to monitor, is fed to a small speaker that is acoustically coupled to the telephone mouthpiece.

Since it is unlikely that remote listening will be done for long periods of time, the Remote Ear has a built-in timer that allows you to listen for about three minutes. Longer or shorter listening times

can be set by adjusting the timing resistor in the emitter circuit of unijunction transistor Q2.

About the circuit

Sound switch 1 and the unijunction timer that is associated with it (Q1) are the same as were used in the Teleswitch. Sound switch 2, however, is slightly modified. Instead of having one relay connected to the 2N3904 collector, there are two relays, RY2 and RY4.

The operation of the Remote Ear involves several steps. When the telephone rings the first time, sound switch 1 triggers and causes RY1 to close. This applies power to sound switch 2 and to the two timing circuits consisting of unijunction transistors Q1 and Q2.

If the phone rings more than once, within 20 seconds sound switch 2 triggers and RY 2 closes. Contact RY2-1 disconnects the power from the first unijunction transistor timing circuit and from sound switch 1. This prevents the Remote Ear from being activated and makes it necessary to wait three minutes before the next attempt.

If, however, the phone rings only once, there is enough time for a charge to build up on C1 and for Q1 to trigger, activating RY3. When RY3 is activated it switches the RY2 coil out of the control circuit of sound switch 2 and replaces it with the RY4 coil.

The first time the telephone rings only once it arms the circuit. The next time the telephone rings it turns on the listening circuitry. This is done by sound switch 2 activating RY4, which, in turn, controls the amplifier and the answering solenoid.

Relay RY4 latches closed and is held in that position until a reset pulse from unijunction timer Q2 turns off the 2N3904 controlling RY2 and RY4 and unlatches SCR2.

The telephone is actually answered by a solenoid that pulls up when RY4 closes. This releases the cradle switch and answers the phone. The handset of the telephone is placed on the table alongside the telephone. The loudspeaker connected to the output of the amplifier is held next to the mouthpiece (rubber bands can be used). Thus, the sound picked up by the crystal microphone is amplified and acoustically coupled to the telephone.

After three minutes, or whatever time period you selected has elapsed, a reset pulse is generated and the bases of the control 2N3904's are brought to ground potential, turning these transistors off and unlatching the SCR's. The unit is now ready for its next monitoring period.

Construction

This project is constructed from four modular circuits. The first two circuits are sound switches identical to those built in the Teleswitch (April 1977). After the sound switches are built, they should be mounted in a metal chassis that is large enough to be placed under the telephone. A 5 × 9 × 2-inch aluminum chassis was used for the prototype. A 1/4-inch hole should be drilled where each of the crystal microphones is mounted so that sound will reach them more easily.

After the sound switch modules are mounted, assemble the control module using the circuit shown in the schematic. The circuit can be fabricated by wiring

the components on perforated board or you can design a printed circuit.

After the control module is completed, mount the board, using spacers, at any convenient spot under the chassis. The only component left to be mounted is the amplifier. The amplifier used here is identical to the one used for the Speakerphone. Mount this module also on the chassis, using spacers.

Once all four modules are mounted, do the relays. Now connect all the wires

solenoid until the fully extended plunger holds the cradle switch down. Attach the solenoid to the wooden support with two screws.

Now attach two conductors of conventional lamp cord to the two terminals on the solenoid. Then, insulate these terminals with electrical tape. Bring the lamp cord down the support, attaching it to the wood in several places with staples. Be careful that staples do not pierce the insulation of the wire, causing a short circuit.

radio. Place the speaker next to the telephone mouthpiece.

Ask a friend to call and let the telephone ring several times. On the first ring, RY1 should close. On the second ring, RY2 should close, opening RY1. After three minutes, a reset pulse from Q2 should reset the lower SCR opening, RY2.

After another three minutes have passed and RY2 has reset, have your friend call again, tell him to ring only

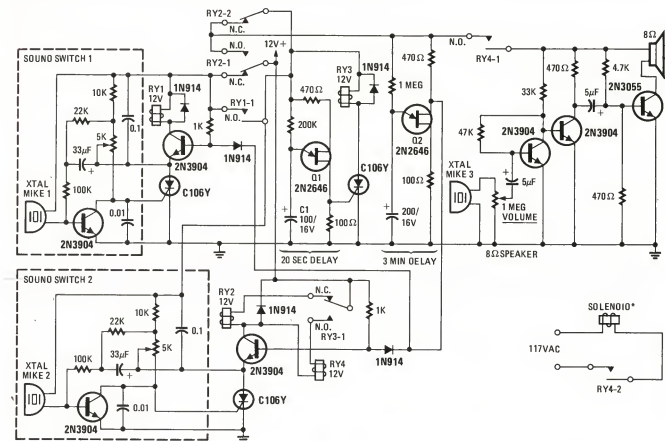


Fig. 1

from the modules and the relays that go together directly to the positive side of the supply. If an external battery is going to be used to supply power, connect these leads to a screw terminal that is insulated from the chassis. If the power supply described for the Teleswitch is used, connect the leads to the positive terminal of the supply. Do the same for all ground leads. Connect all remaining wires to their proper locations.

Cut a piece of 1×2 -inch wood to a length of 10 inches. This will be used as a vertical support for the solenoid that will hold the phone in the unanswered position until the proper command signal is given. To position the arm, place the telephone on top of the phone cradle where the handset is normally placed. Mark the spot, because that is where you want to mount the arm, and mount the arm using at least two screws. Next, place the solenoid on the inside of the arm and take the handset off the telephone. Position the

Bring the wire into the bottom portion of the chassis through a grommet-lined hole and attach one of the two strands to one set of normally open contacts on RY4. Attach another piece of single-conductor lamp cord to the other contact of the set. This wire, along with the unused wire from the solenoid, will be connected to the AC line.

Mount two miniature jacks to the chassis for the microphone and the speaker. The speaker can be acoustically coupled to the telephone by simply holding it next to the telephone mouthpiece with a few rubber bands. The microphone should be located in the spot you want to monitor.

Installation and operation

Installing the Remote Ear simply requires placing the telephone on the chassis, removing the handset and allowing the solenoid to hold the cradle switch down. Now, place the microphone in the room you want to monitor and turn on the


once, and then call back 20 seconds later. On his second call, the phone should be answered automatically after the first ring. This is done by RY4, which becomes activated by sound switch 2 when the phone rings the second time. Relay RY4 closes the circuit to the solenoid and causes it to lift up, releasing the cradle switch of the telephone.

Relay RY4 was activated because after 20 seconds had elapsed, Q1 produced a pulse that activated RY3 and switched the power line from RY2 to RY4.

When the call is answered your friend should hear the radio playing. If he does not, check to make sure that the speaker is properly placed next to the mouthpiece of the telephone. Three minutes after the first ring, Q2 generates a reset pulse and releases RY4. This causes the solenoid to drop and hang the phone up. Simultaneously, it opens the circuit to the amplifier. The Remote Ear is now ready to use again.

R-E

We wrote the book(s)

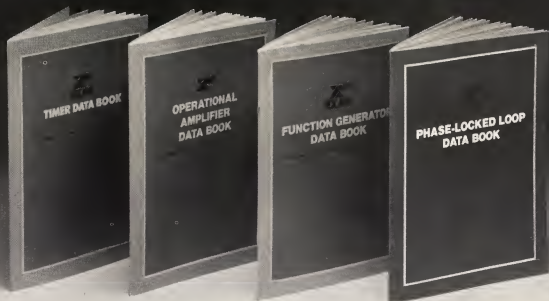

Exar designs and manufactures linear integrated circuits - custom, semicustom, and standards. We also make digital IC's such as our Darlington array drivers, and we are expert at putting both linear and digital functions on the same chip. No wonder then that we have innovated some of the most ingenious IC's on the market today and that we support our circuit families with a set of invaluable "Data Books."

For example, the Exar Timer Data Book describes our XR-2242 long-range timer, which provides delays from microseconds to years, and our L-555 micro-power timing circuit, capable of operating in remote locations for up to 1500 hours on two tiny NiCd batteries. Outstanding circuits like that, plus our broad line, make Exar your first source for timers.

But that's just a sample. Check our Phase-Locked Loop Data Book. This book is complete with PLL fundamentals, application notes, selection hints, plus specifications of some of the industry's most popular circuits like the 567 and our own new XR-2212. See why our PLL's may be the best in the industry.

The Exar Function Generator Data Book contains equally essential information on a circuit family that includes our XR-2206 with its outstanding stability of 20ppm/°C. The Exar Operational Amplifier Data Book covers the full range of op-amps from the standard 4558 all the way through the quad programmable BIFETS.

Whether you have yet moved up to specifying Exar circuits or not, you will find these new Exar Data Books an invaluable reference source. To purchase any of these technical Data Books and receive a free copy of the Exar Product Guide, use the coupon.

Please send me copies of the Exar Data Books indicated at your list price of \$1.75 each. My check or money order is enclosed.



- ☐ Exar Timer Data Book - 48 pages
- ☐ Exar Phase-Locked Loop Data Book - 74 pages
- ☐ Exar Function Generator Data Book - 52 pages
- ☐ Exar Operational Amplifier Data Book - 60 pages
- ☐ Send all four data books at your special discount price of \$5.00.
- ☐ Send a free copy of your Product Guide.

Name _____ Title _____

Address _____ Phone _____

City _____ State _____ Zip _____

EXAR

EXAR INTEGRATED SYSTEMS, INC., P.O. Box 62229,
Sunnyvale, California 94088 • Phone (408) 732-7970

ANNOUNCING
... A New
CREI Program:
Minicomputer &
Microprocessor
Technology
Including A
Microprocessor
Laboratory

Now you can learn at home
the new technology that is
revolutionizing electronics

The microprocessor has ushered in the age of microtechnology and electronics will never again be the same. The microprocessor has made possible the placing of an entire computer on a silicon chip one quarter inch square. The microprocessor "miracle chip" is in the process of changing the world. Soon all technical personnel in electronics will have to understand and work with the microprocessor. It is invading virtually every area of electronics. And it is profoundly affecting your electronics career.

**Brand New
Program**

CREI has a brand new program to help you learn how to work effectively with this revolutionary electronics development. CREI's new program in Minicomputer and Microprocessor Technology is designed to prepare you for this field by giving you the education and practical experience you need.

The program provides solid preparation in electronics engineering technology with a specialization in minicomputers and microprocessors. In addition, it includes a microprocessor laboratory which features a fully programmable microcomputer which utilizes the Motorola 6802 microprocessor chip. This is an extremely important element of your program.


**Programming
Essential**

As you may well know, you must learn how to *program* the microprocessor in order to design, service or troubleshoot microprocessor electronic systems. There is only one effective way to learn this all-important skill of programming, and that is by actually *doing it*. CREI's new program gives you this opportunity as you work with the exciting microprocessor laboratory.

**Programming
Is Easy**

With CREI's new program, learning the skill of programming is simple. Within a few hours you'll be programming the microprocessor and in a short time you'll learn how to program it in three languages: BASIC, assembly and machine languages. In addition, you will learn how to interface the microprocessor with other systems and to test and debug specialized programs.

BUILD THIS

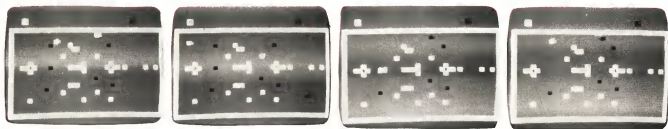

TANK

arcade quality TV game

Part 2. The object is to use your cannon to destroy your opponent first, but watch out for the land mines and anti-tank barriers. The circuit provides a composite video signal to your TV set and produces realistic sound

L. STEVEN CHEAIRS

LAST MONTH, WE PROVIDED THE COMPLETE schematic of the tank game and discussed in detail the circuit operation.

This month, the article concludes with the foil pattern, component placement diagram and construction details.

Building the game

Before beginning construction, you will need an etched and drilled PC board. You can use the foil pattern in Fig. 4 or purchase the board from the source listed in the parts list. Begin by installing the five jumpers on the drilled board (Fig. 5) and then solder all resistors, capacitors and IC sockets to the board. Next, solder in the diodes, transistors and the regulator IC.

Before proceeding, connect a 12-VAC transformer to the AC input; connect a DC voltmeter across the power-supply pins of the game IC; pin 1 is ground and pin 16 is $+V_{cc}$. Now, apply line power to the transformer—7 volts should be indicated on the meter. If 7 volts is not shown but some value close to it, then a new value for R1 or R2 can be chosen by trial-and-error. If the voltage is drastically different, then a circuit problem exists; use normal troubleshooting techniques to locate and repair the problem.

Next, install the CMOS IC's. Again apply power; using an oscilloscope, adjust

the amplitude of the clock at pin 19 of the LSI IC. Remove the power source and discharge the capacitor. Install the AY-3-8700-1 or AY-3-8710-1 IC; the circuit board is now complete. Wire the external components to the PC board (see Fig. 6) and install the unit into a case. If an RF modulator is used, it can be mounted in the case with the PC board or inside the TV set. One last note, the best results were obtained from the prototype with the TV set's contrast control turned up and the brightness control turned to medium-low.

Special considerations

There are several considerations that should be noted for the AY-3-8700-1. First, as the tanks rotate, the shape of their images will vary. Next, the border width will vary from integrated circuit to integrated circuit. Also, the mines could disappear upon interaction with the tanks. When a score is recorded the black tank rotates and the white does not. The 4-second delay makes this effect immaterial. If the tanks exit the screen area, sometimes they will disappear and never return.

For the AY-3-8710-1, the following considerations are important. Upon resetting of the game a random explosion may occur (it may be visible below the bottom

border). Also, during the game the gun of either tank may misfire; that is, shells may explode in a spot where the player is not aiming or the shell may not fire from the tank. These do not affect the normal events of the game.

It is possible for a tank to get trapped in a border. When this happens, the game is ended and the other tank is declared the winner. If the barrier interaction switch is

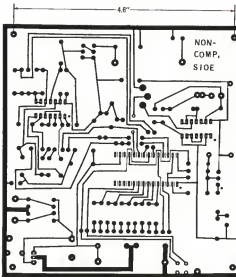


FIG. 4—FOIL PATTERN for the battle game PC board.

Preparation at Home

Wide Choice of Programs

Please note, however, that CREI's new program is only one of 16 state-of-the-art programs in advanced electronic technology offered by CREI. So even if you choose not to specialize in micro-processor technology, CREI has an advanced electronics program to meet your needs.

With CREI, you may choose from any of the following areas of specialization in advanced electronics:

- Microprocessor Technology
- Computer Engineering
- Communications Engineering
- Digital Communications
- Electronic Systems
- Automatic Controls
- Industrial Electronics
- Television Engineering
- Microwave Engineering
- Cable Television
- Radar and Sonar
- Nuclear Instrumentation
- Satellite Communications
- Aeronautical and Navigational
- Solid State Theory
- Nuclear Engineering

Unique Lab Program

An exclusive option available with CREI programs in electronic engineering technology is CREI's unique Electronic Design Laboratory program. It gives you actual experience in designing practical electronic circuits. It also helps you to understand the theories of advanced electronics and gives you extensive experience in such areas as tests and measurements, breadboarding, prototype construction, circuit operation and behavior, characteristics of electronics components and how to apply integrated circuits. Only CREI offers this unique Lab Program.

Practical Engineering

CREI programs give you a practical engineering knowledge of electronics. That is, each part of your training is planned for your "use on the job." By using your training, you reinforce the learning process. And by demonstrating your increased knowledge to your employer, you may qualify for faster career advancement.

Free Book

There isn't room here to give you all of the facts about career opportunities in advanced electronics and how CREI prepares you for them. So we invite you to send for our free catalog. This fully illustrated, 56 page book describes in detail the programs, equipment and services of CREI.

Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

Send for this FREE Book
describing your opportunities
and CREI college-level
programs in electronics

CREI Home Study Programs in
**ELECTRONIC
ENGINEERING TECHNOLOGY**

CREI Introduces
Program 680:
**MINICOMPUTER &
MICROPROCESSOR
TECHNOLOGY**
INCLUDING MICROPROCESSOR
LABORATORY PROGRAM

CAPITOL
RADIO
ENGINEERING
INSTITUTE
McGraw-Hill
Continuing
Education Center
Washington, D.C.
20016

Mail card or write describing qualifications to

CREI **CAPITOL
RADIO
ENGINEERING
INSTITUTE**

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Northwest
Washington, D.C. 20016

Accredited Member National Home Study Council

GI Bill

CREI programs are approved for training of veterans and servicemen under the G.I. Bill.



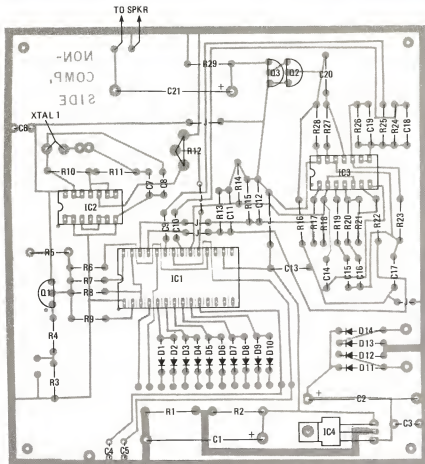


FIG. 5—COMPONENT LAYOUT showing positions of all on-board parts. Switches, speaker and power transformer are mounted in the case.

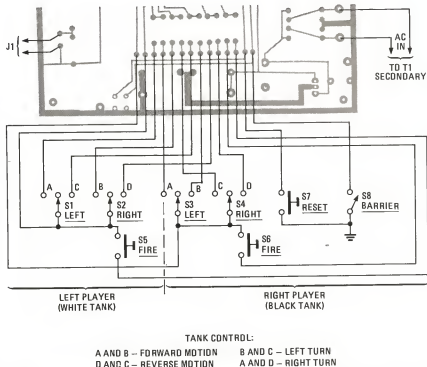


FIG. 6—HOW SWITCHES ARE CONNECTED to the game IC on the board. Lower section of the component side of board is shown for reference.

PARTS LIST

All resistors are 1/4 watt, 5%.

- R1—180 ohms
 - R2—510 ohms
 - R3—470 ohms
 - R4—1800 ohms
 - R5—1000 ohms
 - R6—270 ohms
 - R7, R16, R19, R20, R23, R28—10,000 ohms
 - R8—1600 ohms
 - R9—2400 ohms
 - R10—12 megohms
 - R11—220 ohms
 - R12—5000-ohm, PC-type potentiometer
 - R13—2.2 megohms
 - R14—2200 ohms
 - R15, R21, R26—20 megohms
 - R17, R22—3.9 megohms
 - R18—22,000 ohms
 - R24, R25—10 megohms
 - R27—30,000 ohms
 - R29—15 ohms
 - C1, C2—100 μ F, 50-volt electrolytic
 - C3—2.7- μ F tantalum
 - C4, C6, C13, C14—0.1- μ F disc
 - C7, C8—30-pF disc
 - C9, C10—0.01- μ F disc
 - C11, C12—0.22 μ F
 - C15, C16, C20—5 μ F
 - C17—0.47 μ F
 - C18—200 pF disc
 - C19—100-pF disc
 - C21—220- μ F, 15-volt electrolytic
 - D1—D10—1N4148 or similar
 - D11—D14—1N4005 or similar
 - Q1—Q3—2N3904 or similar
 - IC1—AY-38700-1 or AY-38710-1 LSI game
 - IC2, IC3—4001, CMOS quad NOR gates
 - IC4—78M05, 5-volt regulator
 - J1—miniature open-circuit jack
 - S1—S4—SPDT center-off, momentary-contact toggle switches
 - S5—S7—SPST normally open pushbutton switch
 - S8—SPST switch
 - S9—SPST toggle switch
 - T1—12VAC, 1A secondary transformer
 - XTAL—4.090900-MHz crystal
 - SPKR—8 ohms
 - MISC.—12 \times 7 \times 3-inch aluminum chassis, line cord, hook-up wire, four 1/2-inch stand-off bushings.
- The following parts are available from Questar Engineering Company, McDonald Street, Mesa, AZ 85202: PCB board, \$12.95; AY-38700-1 or AY-38710-1 (please specify), \$29.00; crystal, \$5.50; set of all switches, \$12.25. Kit of all parts, \$63.95.

selected, the tank cannot drive through barriers. If a tank gets trapped in a barrier, momentarily flip the barrier interaction switch to allow the tank to free itself. Also, sometimes the tanks may get locked together; the only way to separate them is to reset the game. In playing both the AY-38700-1 and AY-8710-1 games I very seldom have problems of the type outlined above. These special considerations are presented so that you know what to do in case a problem is encountered.

R-E

HOBBY CORNER

A look at some clever reader solutions to reader problems.

EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

THE TIME HAS COME TO TRY TO CATCH UP on some of the more interesting mail that readers have been sending. I answer letters directly as much as possible, especially if an SASE is enclosed, but there just isn't time to answer all of them. I'd like now just to share some reader ideas with you.

A reader in Puerto Rico makes the point in his letter that he can find published circuits to do everything he has needed so far. These circuits can all be found in manufacturers' data sheets, application notes and various magazines and books. He then says that he would feel pretty silly sending in a circuit obtained from another source, and I agree with him.

Well, it seems to me that although this reader must have a tremendous collection of well-filed and indexed publications there is plenty yet to be discovered. There are many new ways to do old things and new applications for existing components (IC's, etc.).

For example, the lowly 555 has been around for several years now and I would like to have just 1/1000th of a penny for every word that has been written about it. I doubt (although I'm not absolutely sure) that there remains any undiscovered way to make the 555 function as a timer. Quite probably, they all have been discovered and discussed.

Yet, in spite of all that has been written, I am sure that many other applications for the 555 remain. Perhaps some are being discovered right now. There are ways to use the 555 that have not yet been dreamed of.

I agree that we should keep up with what is going on by buying all the magazines and books we can find or afford! After all, there is no point in "re-inventing the wheel" every time we begin a construction project. *Someone* is always finding new and better ways of doing things and we should be aware of them.

Recently, I received a letter describing a fantastic reader-built project. There was not a single new device in the project, but the way some of them were used—WOW! I immediately sent the letter to the editor of *Radio-Electronics*, and if things go as planned, that article may

appear in *Radio-Electronics*.

So, keep on reading, learning, experimenting and building. There is plenty to be discovered. Even if we don't find anything new, though, trying is more fun than anything else I can think of!

Rocket-launching circuit

A while back (July 1978) we discussed several problems on which readers had asked for help. Well, at least one of those problems hit a nerve. Apparently there are a number of model rocketry buffs or rocketeers among us.

A reader asked for a rocket-launching circuit, and it has been interesting to observe the different approaches that have been developed. Once again this proves that there are many approaches to solving a problem.

One of the best launching circuits was sent in by Tim Coffman (Route 2, Box 448, Liberty, MO 64068). I have given his full address because he wrote that he would be glad to correspond with other readers who are interested in model rocketry.

Unfortunately, there isn't enough space to go into Tim's system in detail. In brief, then, he uses eight IC's and two 7-segment digits to count down to 0, fire the igniter and, finally, count up until rocket touch-down to give the flight time. Three of those IC's are used to detect the 0 count, reverse the counters and start the firing. The timer is the ever-useful 555 operating at 1 Hz.

This rocket circuit is complete with appropriate safety switches and LED status indicators. The count can be placed on HOLD at any time, and the firing is done using an SCR rather than a relay. Altogether, it is a very straightforward circuit.

I must admit I am not a rocketeer. I have had a healthy respect for rockets ever since I saw someone's hand badly damaged by carelessly handled fuel. If you are just starting this hobby, be very careful to observe strict safety rules and precautions.

More rockets

A further note about model rockets: I received a letter and catalog from CNA,

Box 1252, Lewiston, ME 04240. This company specializes in rocketry electronics with small and large launching systems and other devices. Company president Alfred Celetti recommends that readers interested in model rockets and electronics write the National Association of Rocketry, Box 275, New Providence, NJ 07974.

Super-simple oscillator

A Canadian reader, Guy Isabel, sent in two useful circuits. One is an interesting timer with no moving parts—not even a pushbutton switch. The other is a neat oscillator.

Guy's super-simple oscillator uses four of the six gates in a 7404 hexadecimale inverter plus one additional part (see Fig. 1). The output frequency is determined by the value of the capacitor (which should not be an electrolytic). As capacitor C is changed from 300 μ F to 300 pF, the frequency changes from 1 Hz to 1 MHz.

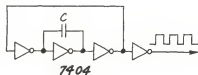


FIG. 1

This oscillator can be used to drive LED's, counters, transistor switches, relays and so on. It could be used as a signal source to test audio amplifiers and certain receivers. In many circuits, it could replace a 555. Used with a switch and several capacitors, it could provide selectable frequencies. And why not use a variable capacitor from an old broadcast radio to cover a range of frequencies?

In addition, Guy Isabel has offered to help those who need circuits for special applications. You can write him at 1725 East, Henri-Bourassa, Apt. 25, Montreal, P. Q. H2C 1J5, Canada.

Low-voltage detector

Hobby Corner received an interesting letter and circuit from Dave Corner of Chicago. Figure 2 is a diagram of Dave's low-voltage alarm circuit.

The values of R1, R2 and D1 are selected for the voltage applied. Using a 12-volt battery, R1 = 10K, R2 = 5.6K and D1 is a 5-volt Zener diode, or a string

of forward-biased silicon rectifiers equaling about 5 volts. Transistor Q1 is a general-purpose UJT (Unijunction Transistor), and Q2 is any small-signal or switching NPN transistor.

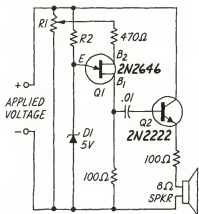


FIG. 2

When this detector is connected across the battery terminals, it draws little current and does not interfere with other devices powered by the battery. If the voltage drops below the trip voltage you have selected with the R1 setting, the speaker beeps a warning. The frequency of the beeps is determined by the amount of undervoltage.

If other voltages are being monitored, select R1 so that it draws only 1 mA or 2 mA (remember $E = IR$). Zener diode D1 is about one-half of the desired trip voltage, and R2 is selected to bias it at about 1 mA.

Thanks, Dave, for sharing this useful circuit with us.

Solder cream

Multicore Solders has a new line of solder cream that comes in tubes like toothpaste. This product doesn't even look like solder, but it is and does a beautiful job.

The type of solder useful for your projects is labeled "Ersin . . ." for electrical soldering. "All you do is squeeze a dab onto a joint and apply heat. For small joints that can't conduct the heat away so fast, the heat source can be a candle, match or cigarette lighter. On larger joints, you should use an iron or torch.

The rosin flux is incorporated in the cream along with the invisible solder. As the cream is heated, it changes to solder and then solidifies to make a good electrical and mechanical joint.

This solder cream is especially handy for use in places that are hard to reach with wire solder. For example, you can coat the end of a wire with cream, insert it into a pin like a phono plug or a PL-259, and then just heat the outside of the pin. It really simplifies the process.

I don't think solder cream will ever replace regular solderwire, but it can perform some jobs more conveniently.

Multicore also manufactures two other

types of solder cream, one an all-purpose variety that can be used for many kinds of metals, including stainless steel and silver. It can be used in the place of the acid-flux solderwire that cannot be applied on electrical joints.

The third solder cream is a lead-free cream composed of tin and silver. This cream can be used on stainless steel, silver and other metals; it is also nontoxic.

Solder cream is handy to have around. If you can't obtain it from a local dealer, write to Multicore Solders, Westbury, NY 11590.

R-E

WE WANT YOUR PROJECT

As you have seen, **Radio-Electronics** regularly publishes construction articles covering all aspects of electronics. If you've just completed an interesting project, tell us about it. If we like it, we'll ask you to become one of our authors and prepare your project as an article. Even if you have never written for a magazine before, this is an opportunity to get your article published and to be paid for your efforts.

Send your proposals to Larry Steckler, Editor, **Radio-Electronics**, 200 Park Ave. South, New York, NY 10003.

THE BIG PLUS + Graphic Equalizer



LOADED with Quality Features!

- Stereo . . . Eleven Bands Per Channel
- Extremely Low Noise & Distortion
- LED Peak Indicators
- Center Detent ("flat") sliders
- Built-in "record" Switching
- Line and Microphone Level Inputs/Outputs
- Fully Guaranteed
- Horizontal or Vertical Cabinets
- Kit or Fully Assembled
- Plus Much, Much More!

AARON-GAVIN INSTRUMENTS, INC.

17231 Corla Avenue

Tustin, California 92680

Send me:

assembled equalizers at \$189.95, p.p.d.

un-assembled equalizer kits at \$99.95, p.p.d.

horizontal (flat) vertical (up-right)

Visa & Master Charge orders accepted

Card No. Bank

Exp. Date No.

Name

City State Zip

California residents include 6% sales tax.


Dealer inquiries invited.

CIRCLE 78 ON FREE INFORMATION CARD

QUICK CHARGE IRON-QUICK CHANGE TIPS

ISO-TIP Quick Charge Cordless Soldering Iron recharges in 3-4½ hours. Uses any of Wahl's 16 snap-in tips.

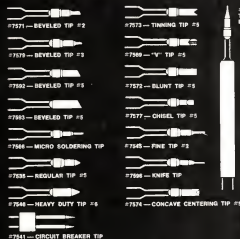Low voltage, battery powered, ground free isolated tip design.



WAHL CLIPPER CORPORATION
ORIGINATORS OF PRACTICAL CORDLESS SOLDERING.
Sterling, Illinois 61081 (815) 625-6525
"Manufacturing Excellence Since 1919"

CIRCLE 35 ON FREE INFORMATION CARD

computer corner

8085 A look at the software required to control an eight channel analog signal monitor.

C. TITUS, P. RONY, D. LARSEN, and J. TITUS*

IN A PREVIOUS COLUMN, WE DESCRIBED the needs of the 8085 control system and the use of the I/O ports and programmable timer to form an eight channel analog monitor. The necessary initialization of the I/O ports was also discussed. Now we will discuss the software that is

necessary for proper operation of the system. It is assumed that the control process is very simple, perhaps just sensing only upper and lower limits of the analog signals.

The programmable timer within the 8155 generates an interrupt every 10 ms.

or continue timing for another 1-second interval. A read/write memory location, SEC, is set aside that will be used to count the 100, 10-ms interrupts. Another location will be required to contain the number of seconds that must be delayed between sampling. Since the thumb-wheel-switch data will be entered in binary-coded decimal (BCD) format, you have to decide whether it will be processed in binary or BCD format. We have chosen to process it in BCD format to eliminate a BCD-to-binary conversion process.

A typical timer control subroutine is shown in Fig. 1. Note that there are steps in this subroutine that clear the RST 7.5 flag and then re-evaluate the RST 7.5 interrupt mask. The information stored in location SEC and BCDTIM has also been used.


```

RST75,  PUSHPSW      /SAVE REG A & FLAGS
        MVI         /CLEAR INTERRUPT FLAG
        020
        SIM
        MVI         /RE-ENABLE INTERRUPTS
        013
        SIM
        LDA         /GET # OF LOOPS REMAINING
        SEC
        0
        DCRA        /DECREMENT IT BY ONE
        STA         /SAVE IT
        SEC
        0
        JNZ         /IF NOT ZERO, DO ANOTHER LOOP
        NOTYET      /THROUGH THE INTERRUPT
        0
        MVI         /YES, IT'S ZERO, SO RESET THE SECOND
        144
        STA         /COUNTER TO 100 (10 MSEC LOOPS)
        SEC         /STORE IT
        0
        LDA         /GET THE TIME
        BCDTIM
        0
        STC         /SET THE CARRY FLAG
        CMC         /COMPLEMENT IT TO CLEAR IT
        ADI         /ADD 239 = DECIMAL 99
        143
        DAA         /DECIMAL ADJUST IT FOR A SUBTRACTION OF ONE
        STA         /OF ONE, AND THEN STORE IT
        BCDTIM
        0
        JNZ         /IF THE RESULT IS NOT ZERO, LOOP THROUGH
        NOTYET      /AGAIN
        0

/ADC SERVICE ROUTINE
IN       /INPUT THE BCD DATA FROM THE SWITCHES
        201
        STA         /UPDATE THE BCD TIME
        BCDTIM
        0
        NOP         /THE ADC SERVICE STEPS GO HERE
        NOP
        NOP
        NOP
        NOP
        /ETC.
        POPPSW      /RESTORE REG A & FLAGS
        RET         /RETURN TO MAIN PROGRAM
    
```

FIG. 1

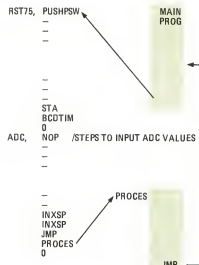Since the basic unit of time in this system is a 1-second interval, 100 1-second interrupts must be counted before any action can occur. When the 1-second point has been reached, the program must check to see if it must perform some other action,



data in the subroutine and then proceed to a data or control-processing section of the program that is *outside* of the interrupt-service subroutine. The control or processing of the program will be interrupted briefly every 10 ms, but it will have up to 1 second to process the old data. It has been assumed that the processing takes less than 1 second. The software example in Fig. 2 shows how the control processing software has been removed from the interrupt-service subroutine. There are other equally valid solutions to this problem. Remember, however, that when you do not intend to use a return address on the stack, you must increment the stack pointer twice to avoid loading the stack with useless information.

This application does not use the serial-in (SID) or serial-out (SOD) connections on the 8085. These connections could be used as a single line-control input and a single line-control output, respectively. They can also be used to serialize ASCII characters for output or to parallel the serial bit stream to reconstruct parallel data bytes. Thus, a software UART could be constructed very easily.

R-E

Have regular medical check-ups.

American Heart Association
We're Fighting For Your Life

ANNUAL INDEX JANUARY—DECEMBER 1978

To present the maximum number of articles to our readers, we have not published the Annual Index as part of this issue. A 4-page brochure containing this index is available for those who need one. To get your free copy, send a *stamped self-addressed envelope (legal size)* to:

Radio-Electronics
Annual Index
45 East 17th Street
New York, NY 10003

Any requests postmarked on or before February 28 are free. After that date there is a 25¢ fee. Questions and comments about anything other than the index that are included with your request cannot be handled. Send them separately to our Editorial Offices.

NOM CARD FOR 1802 continued from page 48

EF₂, EF₃, EF₄). The flip-flop is reset when the status/output register is read.

The only portion of the interface we have not discussed is the clock—a simple 400-kHz RC oscillator operating between +5 volts and -4 volts, and the hold/reset circuits. The reset circuit is a TTL-to-MOS voltage converter since the reset, hold and oscillator pins are non-TTL inputs. The reset must be held low for at least eight oscillator periods as part of its power-on sequence (8 oscillator periods

equals 20 μ s). Thus, when the system is powered-up as part of the initialization routine, the reset is set for a minimum of 20 μ s, during which time the input-ready flip-flop is clocked three times. The first two times it is set, write an 80_{HEX} to the input port to clear the flip-flop; this is necessary because the hold is set each time the output ready occurs. When the third signal occurs, the NOM interface is ready for its first instruction. If it is not needed at this time, store a 40_{HEX} in the input port. The hold circuit is formed by a TTL-to-MOS voltage converter driven by a 2-input OR gate.

continued next month

NLS
NEW

NLS LEADS AGAIN!!

MS-215 DUAL TRACE MINISCOPE



15MHz PORTABLE OSCILLOSCOPE

- 15 megahertz bandwidth.
- External and internal trigger.
- Time Base—0.1 microseconds to 0.5 Sec/div—21 settings.
- Battery or line operation.
- Automatic and line sync modes
- Power consumption less than 15 W.
- Vertical Gain—0.01 to 50 volts/div—12 settings.
- Weight is only 3 pounds.

RECHARGEABLE DUAL TRACE

PORTABLE
2.7"H x 6.4"W x 7.5"D

AVAILABLE NOW

\$435

With Rechargeable
Batteries & Charger Unit



**FREE
CASE**

DELUXE CARRYING CASE
A \$45 value, you get this deluxe carrying case free with the purchase of the MS215.

OFFER EXPIRES FEB. 28, 1979



212-587-2224

THE TEST EQUIPMENT SPECIALISTS

**TOLL FREE HOT LINE
800-223-0474**
54 West 45 Street, New York, N.Y. 10006

**ADVANCE
ELECTRONICS**

service clinic

Trouble with the color and how to localize the problem.

JACK DARR, SERVICE EDITOR

THERE ARE REALLY ONLY THREE COLOR problems and they should be easy to analyze. These are: no color at all, the wrong color and the loss of color sync. These problems originate in three separate circuits—the bandpass amplifier, the 3.58-MHz reference oscillator and the color AFPC (Automatic Frequency and Phase Control) circuit. If you check a set and a perfect black-and-white picture appears, this clears everything else in the set!

A complete loss of color can be due to several causes. First, a loss of the color signal itself can be due to a dead 3.58-MHz oscillator, or to faults in the color-killer circuit. To find out which circuit is at fault, feed a color-bar signal into the set and scope the bandpass-amplifier output signal. This signal is normally present at the color control, but it will always appear at the input to the demodulators. If you see a normal "comb" pattern at the right amplitude, the bandpass-amplifier stage is working all right, as well as the killer circuit.

Check for the oscillator signal with a scope. This signal must be at the right amplitude. If the oscillator isn't working, there will be no color.

If you do not see the comb pattern at the bandpass-amplifier output, check all DC voltages, tubes/transistors and pay special attention to the bias on the second bandpass amplifier. This is where the killer bias is used. The DC voltage shown on the service schematic are for no-signal conditions, meaning no color.

The grid will be at a high negative voltage (for a tube circuit; cutoff polarity for a transistor). This voltage should drop to a much lower value when a color signal is fed in. Remember, this is just a plain IF amplifier circuit! If necessary, you can override the killer bias on the grid to check whether the color signal goes through. If so, check out the killer-bias circuitry. This may mean bad diodes, tubes, transistors, or just control misadjustment.

With reference to color alignment, the key word is *don't!* If you must perform alignment, do so only as a last resort and only after finding definite clues that it is needed. Use a sweep curve on your scope to check for misalignment. This will give

you a definite clue. However, you should remember that, unless it is very bad, misalignment does *not* cause a complete loss of color, nor will it ever cause a sudden dropout of color. In most cases, alignment is only needed because someone has tampered with the set. Check the scope pattern. If the comb is flat on top and the bars are clean and sharp, it is probably not necessary to align. (Hint—with older scopes, for a clearer pattern use a crystal-detector probe to trace the signals through the bandpass-amplifier stages.) With wideband scopes, use a low-capacitance probe.

If the color oscillator doesn't function at all, this causes a complete loss of color. Some Service Clinic readers write: "My color bars are bluish and greenish, but I can't get any reds!" In quite a few sets, this is because of a dead oscillator. The weak tints observed are because enough of the signal burst leaks through to make the demodulators try to work. The color burst phase is between blue and green. (By the way, this usually means that the demodulators are working!)

The 3.58-MHz signal is critical. A phase shift of only one-sixteenth of one-cycle causes blue to change to green, etc.! A working oscillator/AFPC circuit holds the frequency so steadily that this shift seldom occurs. For a network program, a frequency counter on this oscillator should read 3,579,545 Hz. (This frequency is generated by networks using atomic clocks, rubidium and caesium.)

A defective crystal changes the frequency. So far, I have not yet discovered a set that has a dead oscillator due to a bad crystal. If the crystal is just a little off-frequency, the oscillator tends to pull against the AFPC circuit control signal. This makes the color-sync extremely sensitive and prone to fall out with interruptions.

There are two types of oscillator circuits. One is a Pierce oscillator circuit. The crystal controls the frequency, which, in turn, is controlled by the signal burst through the AFPC circuit. Don't be afraid of the AFPC circuit—it basically resembles any horizontal AFC circuit! The oscillator frequency is controlled by a DC voltage developed across a diode pair. To adjust this, kill the AFPC circuit

so that the oscillator works independently. Now, adjust the reactance coil, etc., until the colors lock in momentarily. Taking the shunt off the AFPC circuit should lock the color in firmly. If the color falls out of sync, the AFPC circuit isn't operating.

There is one obscure *external* cause for color-sync problems. This is the horizontal oscillator automatic frequency control. In many older sets, this control held the picture in sync over a considerable range. However, at the ends of the control range, the color changed hue and fell out. This was due to the change in *phase* of the pulse from the flyback used to gate-out the burst signal. Changing the phase of this pulse far enough results in no signal burst or a very weak burst. Make sure that the horizontal-hold control is centered in its range.

The other type of color oscillator circuit is actually a burst amplifier. This circuit picks off the burst signal and feeds it to a sharp filter, usually a crystal. This causes the crystal to ring; this ring lasts long enough for the next burst signal to arrive. It therefore develops a continuous output that is actually the network signal burst itself. If the gating pulse is out of phase, the burst will not be strong enough to make the circuit work.

In circuits with a reactance-tube AFPC control, this control is actually a voltage-controlled oscillator (VCO). The AFPC diodes develop a small DC-control voltage by comparing the signal burst to the oscillator frequency, similar to horizontal AFC. In many sets, there should be zero voltage on the grid of the reactance tube with the oscillator locked on. (In some, this voltage is offset. Make sure to check the schematic voltage values.) Typical voltage values might range from +5 to -5.

If you run into one with tricky color sync, check to make sure that this voltage "crosses zero" to about the same voltages. This is actually just like any FM discriminator, which it is. Its output signal is an S-curve. If the crystal is just slightly off, you'll probably discover that the grid voltage is either a positive or a negative voltage, but it will not cross zero. It will come down to zero perhaps, and then return in the same polarity. Try a new crystal to see if you can obtain a zero crossing and lock in at 0 volt.

All TV set service data includes com-

JUST \$495 GETS YOU THIS DUAL TRACE GOULD SCOPE PLUS TWO XIO PROBES.

You know that's a great price. Especially when you consider the outstanding performance you get with this Gould OS245A oscilloscope.

And you get clear, bright displays. 5mV/div. sensitivity and exceptionally versatile trigger performance. It's ideal for TV or general electronic service work; perfect for hobbyists and educational institutions. You can rely on Gould to live up to these specs:

- DC to 10 MHz; dual trace
- Trigger performance in excess of 15 MHz
- TV trigger facilitates solid synchronization with TV signals



- Portable; weighs just 11 lbs.
- Carries full two year warranty on all parts and labor excluding normal calibration, fuses and minor maintenance. Just one phone call gets you action.

Don't miss out on this bargain. Pick up the phone now and call us toll-free at 800-325-6400. (In Missouri call 800-342-6600). We'll rush you free literature and ordering information on the OS245A as well as other Gould oscilloscopes applicable to your needs. Gould Inc., Instrument Systems Division, 3631 Perkins Avenue, Cleveland, Ohio 44114.



CIRCLE 62 ON FREE INFORMATION CARD

SERVICE QUESTIONS

continued from page 82

open. Also, D101 was bad. I replaced it, but the new one lasts about 5 or 6 seconds and then shorts. Help!—D. W., Feeding Hills, MA.

The picture tube heater circuit in this set uses an instant-on transformer that places 5.0 volts on the tube heater. When you turn the switch on, the primary of this transformer is shorted out. In operation, the picture tube heater is fed from a winding on the flyback circuit. (This produces a 15,750-Hz pulse, at about 26 volts P-P, which is equal in heating effect to the normal 6 VAC 60-Hz pulse.)

If you used the substitute for D101 recommended in the parts list—RCA SK-3016—this is probably causing your trouble! The RCA SK-3016 is a "sine-wave diode," and the one you need must be a fast-recovery type. Try using SK-3175, SK-3515, etc. This applies to all sets using DC power supplies derived from flyback pulses.

R-E



HIGH BLOOD PRESSURE.
Treat it...and live.

The National High Blood Pressure Education Program,
U.S. Department of Health, Education, and Welfare.

WANT TO CUT OUT A NEW CAREER IN LAND MOBILE SERVICE?

WE CAN HELP YOU SWITCH

... by providing professional HOME STUDY training for you and your technicians. MTI has been providing specialized training in land mobile servicing for 18 years. We would like to help you also. For more information, cut out this coupon.

NO SALESMAN WILL CALL!

Name

Address

City

State/Zip

223




Mobile Training Institute
Box 735, Camp Hill, PA 17011

CIRCLE 40 ON FREE INFORMATION CARD

Personal Computers & Microprocessing

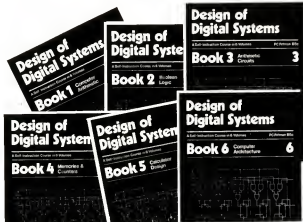Here are two inexpensive programmed learning courses designed to keep you up-to-date in digital electronics.



Design of Digital Systems - six volumes

The products of digital electronics technology will play an important role in your future. Calculators, digital watches and TV games are already commonplace. Now, microprocessors are generating a whole new range of products. Personal computers will be in widespread use very soon. Your TV, telephone and computer will combine to change your children's education, your job—your entire way of life.

WRITTEN BY EXPERTS

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects as well as your understanding of the rapidly changing technological world around you.

The courses are designed as much for the professional engineer as for the amateur enthusiast. You'll learn about microprocessing as well as personal computing—not to mention all the other aspects of digital electronics design.

ADVANCED COURSE DESIGN OF DIGITAL SYSTEMS

Design of Digital Systems is written for the engineer and serious hobbyist who wants to learn more about digital electronics. Its six large-format volumes—each 11" x 8 1/2"—are packed with information, diagrams and questions designed to lead you step by step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of microprocessors and computers.

CONTENTS

The contents of Design of Digital Systems include:

Book 1: Octal, hexadecimal and binary number systems; representation of negative numbers; complementary systems; binary multiplication and division.

Book 2: OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; DeMorgan's Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

Book 3: Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4: Flip-flops; shift registers; asynchronous counters; ring, Johnson and exclusive-OR feedback counter; random access memories (RAMs); read-only memories (ROMs).

Book 5: Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.

Book 6: Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; executive programs, operating systems, and time-sharing.

BASIC COURSE



Digital Computer Logic & Electronics

CONTENTS

Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though you should have an aptitude for logical thought. It consists of 4 volumes—each 11" x 8 1/2"—and serves as an introduction to the subject of digital electronics.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; DeMorgan's Laws; design of logic circuits using NOR gates; R-S and J-K flip-flops; binary counters, shift registers and half-adders.

NO RISK GUARANTEE

There's absolutely no risk to you. If you're not completely satisfied with your courses, simply return them to GFN within 30 days. We'll send you a prompt, full refund, **plus return postage.**

TAX DEDUCTIBLE

In most cases, the full cost of GFN's courses can be a tax deductible expense.

HOW TO ORDER

To order by credit card, call GFN's toll-free number — (800) 331-1000; or send your check or money order (payable to GFN Industries, Inc.) to the address below.

Prices include overseas surface mail postage. Air Mail: additional costs (10 volumes); Caribbean \$10; Europe \$15; Africa, South America \$20; Australia, Asia \$25; or write for exact quote.

Write for educational discounts, quantity discounts and dealer costs.

LOW PRICES - SAVE \$5

We ship promptly from stock. There are no extras—we pay all shipping costs; we even pay your sales tax where required. And if you order both courses, you save \$5. Order at no obligation today.

Design of Digital Systems \$19.95
- 6 volumes

Digital Computer Logic \$14.95
& Electronics - 4 volumes

Both courses - 10 volumes \$29.90

Also available at leading computer stores:

Computer Mart of New York, 118 Madison Ave., New York, NY.
Fire Computer Co., 1253 West 8th St., Erie, PA.
Interactive Computers, 78405 Elmwood, Houston, TX.
Interactive Computers, 16445 El Camino Real, Menlo Park, CA.
Interactive Computers, 217 W. San Francisco, Santa Fe, NM.
Readout Computer Stores, 6 Wimpole Ave., Buffalo, NY.
Imperial Computer Systems, Inc., 2109, 23rd Ave., Rockford, IL.
Home Computer Center, 6101 Yonge St., Willowdale, Ontario, Canada
and many others. Ask your dealer.

GFN

GFN Industries, Inc.
Suite 400-R
888 Seventh Ave.
New York
N.Y. 10019

Call TOLL-FREE (800) 331-1000
(orders only)

HOBBYISTS! ENGINEERS! TECHNICIANS! STUDENTS!

Write and run machine language programs at home, display video graphics on your TV set and design microprocessor circuits—the very first night—even if you've never used a computer before!

ELF II featuring RCA COSMAC MICROPROCESSOR/mini COMPUTER \$99.95

ELF II by

NETRONICS

as featured

in POPULAR

ELECTRONICS

Shown with

optional Memory Board,

GIANT BOARD™ a huge board.

Stop reading about computers and get your hands on one! With ELF II and our new *Short Course* by Tom Pittman, you can master computers in no time at all! ELF II is a computer that commands an RCA 1802 to execute and the *Short Course* quickly teaches you how to use each of the 1802's capabilities. ELF II's video output lets you display an alphanumeric readout or graphics on any TV screen or video monitor plus enjoy the latest video games, including an exciting new target/misile gun game that was specifically developed for ELF II.

But that's not all. Once you've mastered computer fundamentals, ELF II can give you POWER with add-ons that are among the most advanced found anywhere. No wonder IEEE chapters plus hundreds of universities and major corporations have chosen the ELF II to introduce their students and personnel to microprocessor computing!

Learn The Skill That May Soon Be Far More Important Than Your College Degree!

The ability to use a computer may soon be more important to your earning power than a college degree. Without a knowledge of computers, you are always at the mercy of others when it comes to solving highly complex business, engineering, industrial and scientific problems. People who understand computers can command MONEY and to get in on the action, you must learn computers. Otherwise you'll be left behind.

ELF II Is The F-A-S-T Way To Learn Computer Fundamentals!

Regardless of how minimal your computer background is now, you can learn to program a computer in an hour's time! That's because Netronics has developed a special *Short Course on Microprocessor And Computer Programming* in technical language that leads you through every one of the RCA COSMAC 1802's capabilities so you'll understand everything ELF II can do... and how to get ELF II to do it! A 1802 command manual an 1802 can execute and every one of your, step-by-step. The text, written for Netronics by Tom Pittman, is a tremendous advance over every other programming book in print.

Keyed specifically to the ELF II, it's loaded with "hands on" illustrations. When you're finished, ELF II and the 1802 will no longer hold you any mysteries to you.

In fact, not only will you be able to use a personal computer creatively, you'll also be able to read magazines such as *BYTE*, *TELETYPE AGE*, *POPULAR ELECTRONICS* and *PERSONAL COMPUTING* and understand the articles.

If you work with large computers, ELF II and our *short Course* will help you to understand what makes them tick.

A Dynamite Package For Just \$99.95!

With ELF II, you learn to use machine language—the fundamental language of all computers. Higher level languages such

as FORTRAN and BASIC must be translated into machine language to use them. A computer can understand them. With ELF II you build a solid foundation in computers so you'll really know what you're doing, no matter how complicated things get.

Video output also makes ELF II unique among computers selling for such a low price. Attach your TV set, ELF II becomes a fabulous home entertainment center. It's capable of providing endless hours of fun for both adults and children of all ages! ELF II can create graphics, alphanumeric displays and fantastic video games.

No additional hardware is required to connect ELF II to your TV's video input. If you prefer to connect ELF II to your antenna terminals instead, simply use a low cost RF modulator (to order only, see coupon below).

ELF II's 5-card expansion bus (connectors not included) allows you to expand ELF II as your needs for power grow. If you're an engineer or hobbyist, you can also use ELF II as a counter, alarm, lock, thermostat, timer or telephone dialer, or for countless other applications.

ELF II Explodes into A Giant!

Thanks to ongoing work by RCA and Netronics, ELF II add-ons are among the most advanced anywhere. Plug in the GIANT BOARD™ and you can record and play back programs, edit and debug programs, communicate with remote devices and much more. Happen to be the outstanding way to get ELF II to solve special problems such as operating a more complex alarm system or controlling a printing press. Add a video screen at any point in your program for more information and solve more sophisticated problems.

Expanded, ELF II is perfect for engineering, business, industrial and personal finance applications. No other small computer anywhere near ELF II's low price is backed by such an extensive research and development program.

The ELF-BUG™ Monitor is an extremely recent breakthrough that lets you debug programs with lightning speed because the key to debugging is to know what's inside the registers of the microprocessor and, instead of single stepping through your program, the ELF-BUG™ Monitor, utilizing break points, lets you display the entire contents of the registers of your TV screen at any point in your program and scroll immediately what's going on and can make any necessary changes. Programming is further simplified by displaying 24 bytes of RAM in full address, register cursor and auto scrolling. A must for serious programmers.

Netronics will soon be introducing the ELF II Color Graphics—more breakthroughs that ELF II owners will be the first to enjoy!

Now BASIC Makes Programming ELF II Even Easier! Like all makes, ELF II understands only "machine language" the language computers use to talk to each other. But, to make it easier for you, we've developed an ELF II BASIC. It talks to ELF II in machine language for you so that you can program ELF II with simple words that can be typed out on a keyboard such as PRINT, RUN and LOAD.

"Ask Now What Your Computer Can Do... But What Can It Do For YOU!"

Don't be trapped into buying a dinosaur simply because you can afford it and its big ELF II is more useful and more fun than any other computer that costs less than \$1000.

With ELF II, you learn to write and run your own programs. You're never reduced to being a mere keypunch operator, working blindly with someone else's predeveloped software.

No matter what your specialty is, owning a computer which you really know how to use is sure to make you a leader. ELF II is the fastest way there is to get into computers. Order from the coupon below!

—SEND TODAY!

- ☐ Deluxe metal cabinet for ASCII keyboard, \$19.95 plus \$2.50 p&h.
- ☐ ELF II TINY BASIC on cassette tape. Commands include SAVE, LOAD, RUN, PRINT, LIST, IF, THEN, INPUT, PRINT, GO TO, GO SUB, RETURN, END, REM, CLEAR, LIST, RUN, PLOT, PEEK, POKE. Comes fully documented and includes alphanumeric generator required to display alphanumeric characters directly on your TV screen without additional hardware. Also plays tick-tack-toe plus a drawing game that uses ELF II's keyboard as a joystick, 4k memory required. \$14.95 plus \$2.50 p&h.
- ☐ Tom Pittman's *Short Course on Tiny BASIC for ELF II*, \$5.95 paid.
- ☐ Expansion Power Supply (required when adding 4k RAM), \$34.95 plus \$2.50 p&h.
- ☐ ELF-BUG™ Deluxe System Monitor on cassette tape. Allows displaying the contents of all registers on your TV at any point in your program. Also displays 24 bytes of memory with full addresses, blinking cursor and auto scrolling. A must for the serious programmer! \$14.95 plus \$2.50 p&h.

Coming Soon: A-D, D-A Converter, Logic Pkts., Controller Board, City Graphics & Music System... and more!

Call or write for wired prices!

Netronics RAD Ltd., Dept. RE-12, 333 Litchfield Road, Dept. RE-12, New Milford, CT 06776. (203) 354-9375.

Yes! I want to run programs at home and have enclosed: ☐ \$99.95 plus \$3 postage & handling for RCA COSMAC ELF II kit, ☐ \$4.95 for power supply (required), ☐ \$5 for RCA 1802 User's Manual, ☐ \$5 for *Short Course on Microprocessor & Computer Programming*, ☐ I want mine wired and tested with power supply, RCA 1802 User's Manual and *Short Course* included for just \$149.95 plus \$3 p&h.

I am also enclosing payment (including postage & handling) for the items checked in left.

Total Enclosed (Conn. res. add. tax) \$_____ ☐ Check here if you are enclosing Money Order or Cashier's Check to expedite shipment.

USE YOUR C/VISA ☐ Master Charge ☐ Interbank ☐

Account # _____

Signature _____ Exp. Date _____

PHONE ORDERS ACCEPTED (203) 354-9375

Print Name _____

Address _____

City _____ State _____ Zip _____

DEALER INQUIRIES INVITED

SERVICE QUESTIONS

continued from page 81

21HB5 horizontal-output grid. When I did this, the bias on the 21HB5 was only -20 volts or so! (I found that I could clamp the pin 1 voltage to -11 and the picture and sound were good.) Why was the voltage so low? Was there leakage in the capacitor? When I checked, capacitor C65 was leaky. I replaced it and bingo! Button this one up.

The second chassis went white in a few minutes and then lost the horizontal drive completely. I followed same circuit; same problem, only heat-sensitive. I replaced C65; no luck. I replaced C66; no luck. Although the 21HB5 tube had been checked and showed good, I didn't change it because I didn't have a new one at the time. So I replaced the 21HB5. Hallelujah! Now the grid bias holds steady at -39 volts, which it should. It wouldn't do this before. So much for AGC problems (which aren't)!

(Congratulations on the persistence and perspicacity, Dave! We have run into quite a few oddball problems like this in horizontal-output tubes in the past few years. In general, it's a good idea to try a new tube and see if this clears the problem. The cause seems to be excessive grid emission (although this is only my opinion). In this case, the analysis became complex until we traced down the source of the negative voltage used to bias the AGC tube. This is a mildly unusual circuit, although quite workable if everything is in good shape.)

FUSE BLOWS VERY FAST

The main power-supply fuse blows very quickly in this Truetime model GEC-4316B. I've checked everything without result! I replaced a few parts, including the horizontal output transistor; no luck. It looks simple but isn't!—D. M., Brunswick, GA.

Here's my favorite remedy: Hook the set up to a variable voltage transformer (variac). Connect an AC ammeter across the empty fuse holder. (If you don't own an AC ammeter, hook up a 0.5-amp pilot light across the fuse holder.) Turn the line voltage up very slowly until you notice just a small current flow, or until the bulb lights up a little.

Check the DC power-supply voltages at a point where there should be voltage but it's missing. This solid-state power supply starts to conduct at a very low voltage, which allows you to get data without excessive smoke!

HEATER CIRCUIT OUT

Have I got problems in this Philco model 4C490! The high voltage is 28 kV, there's good sound, the dial lights work, but there's no raster because the picture tube heater is dead! The heater is not

continued on page 84

plete instructions for making color-setup tests, alignment tests and so on. Follow these instructions to the letter. Watch out for deviations; some instructions are different. The tests are usually quite simple; in most, the only instrument you need is a DC voltmeter. Watch the screen to observe what's happening. Color troubles can be easy to troubleshoot if they are approached methodically and logically, one step at a time.

R-E

service questions

VERTICAL PROBLEM

David Day, of Flori-Day Electronics, Apalachicola, FL, sends these tips along. (He had two Zenith model 14B38Z chassis, both with automatic-gain control (AGC) problems. I suggested some possible cures, including replacing the VDR in the AGC circuit.)

"Here's some feedback for you! I changed the VDR's on both chassis. This didn't help, so I started on the first chassis. I checked all DC voltages around the AGC tube, and found that the voltage on pin 5 of the 8BA11 was only -4 instead of -11. You also suggested tracing the circuit and following it back to the

continued on page 82

For
faster
service

USE
ZIP
CODE

on
all
mail

Accuracy like a VTVM... Convenience like a VOM...

NEW BATTERY-OPERATED FET
SOLID-STATE VOLT-OHMMETER #116

Easy-to-build KIT

\$44.⁷⁸ =116K

Factory-Wired & Tested

\$60.⁰⁵ =116W

Now you can get all the benefits of a VTVM (laboratory accuracy, stability and wide range) but with its drawbacks gone: no plugging into an AC outlet, no waiting for warm-up, no bulkiness. New Field Effect Transistor (FET) design makes possible low loading. Instant-on battery-operation and small size. Excellent for both bench and field work.

Compare these valuable features:

- High impedance low loading: 11 megohms input on DC, 1 megohm on AC • 500-times more sensitive than a standard 20,000 ohms-per-volt VOM • Wide-range versatility: 4 P-P AC voltage ranges: 0-3.3, 33, 330, 1200V; 4 RMS AC voltage ranges: >1-2, 12, 120, 1200V; 4 DC voltage ranges: >1-2, 12, 120, 1200V; 4 Resistance ranges: >1K, 0-100K, 0-10 meg, 0-1000 meg; 40dB ranges: -24 to +50dB.
- Sensible easy-to-read 4½" 200 micro-amp meter. Zero center position available. Comprises FET transistor, 4 silicon transistors, 2 diodes. Meter and transistors protected against burnout. Etched panel for durability. High-impact bakelite case with handle usable as instrument stand. Kit has simplified step-by-step assembly instructions. Both kit and factory-wired versions shipped complete with batteries and test leads. 5¼" H x 6¼" W x 2¼" D. 3 lbs.



Send FREE catalog of complete EMC line and name of nearest distributor. RE-12

Name _____
Address _____
City _____
State _____ Zip _____

EMC

ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N.Y. 10012



A Platt tool case won't fall apart at the seams because there are no seams.

Unlike other tool cases, the pockets on a Platt Pallet are molded without any seams, stitches or rivets to form a one-piece unit. It's practically indestructible.

The case itself has that same rugged construction. It comes in either tough, lightweight ABS Thermoplastic, rich looking expanded vinyl or a combination of both.

Platt also has rugged hardware. Like an aluminum rim for extra strength. Steel core handles. And tough brass locks.

Inside there are compartments for larger tools, parts boxes and testing equipment. And multiple lid pockets for paper and order books.

Besides having a tough case Platt has a tough 5-year guarantee on both the case and pallet.


* Pat. No. 3,880,285

Cases for business and industry.

platt

2301 S. Prairie Ave., Chicago, Ill. 60616 (312) 225-6670

CIRCLE 71 ON FREE INFORMATION CARD

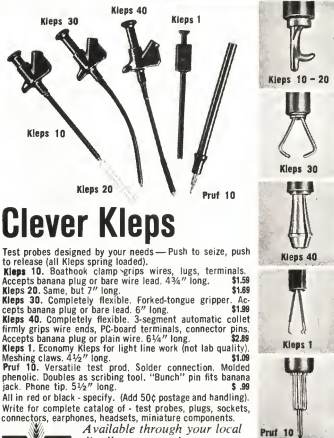

Clever Kleps

Test probes designed by your needs—Push to seize, push to release (all Kleps spring loaded).

Kleps 10. Boathook clamp grips wires, lugs, terminals.

Accepts banana plug or bare wire lead. 4¾" long. \$1.59

Kleps 20. Same, but 7" long. \$1.59

Kleps 30. Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. \$1.99

Kleps 40. Completely flexible. 3-segment automatic collar firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6¼" long. \$2.29

Kleps 1. Economy Kleps for light line work (not lab quality). Meshing claws. 4½" long. \$1.09

Prof 10. Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½" long. \$.99

All in red or black - specify. (Add 50¢ postage and handling).

Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

RYE INDUSTRIES INC.

130 Spencer Place, Mamaroneck, N.Y. 10543

In Canada: Rye Industries (Canada) Ltd.

CIRCLE 27 ON FREE INFORMATION CARD

THE
ELECTRICAL
TERMINAL
&
CONNECTOR
SHOP™

FREE

A \$2.50-value, well-size (17 1/2" x 24") Specifications Chart Shows how to select the right terminal or connector... how to identify wire and stud sizes... explains coding... and much, much more. Yours absolutely FREE!!

Just about every bit of electrical hardware you'll ever need... over 1,000 pieces (that's 7 gross! over 84 dozen!) all organized & labeled in a heavy-duty, bin-cabinet!

You'll wonder how you ever did without it... truly one of the most important "tools" you could own!

WORKSHOP'S
ALL FOR JUST

\$29.95

plus \$3.90 shipping and handling

The hardware alone would cost around \$100 at retail prices! Price it out anywhere!!



LOOK AT ALL YOU GET! Every type, size and style of terminal and connector you'll probably ever need! Full size ranges!

- No more "making do" with just anything you have on hand!
- No more "drugstore quality" terminals and connectors!
- No more high prices!
- No more less-than-professional repair jobs!
- No more frustrating searches for the right piece of electrical hardware!
- No more time-consuming soldering!
- No more Saturday-morning trips to the hardware or electrical supply store!

BONUS BUY:

A Stanley, industrial-quality "Jobmaster" crimper at our wholesale cost!

REGULAR \$5.99 JUST \$2.99

Limit: One crimper per shop. Crimpers not sold separately.

All high quality, 99% conductivity, plated copper terminals and connectors. Meet or exceed UL, CSA, and (where applicable) OEM standards. Not inexpensive "stamped-out-tin" hardware. No "seconds" or "rejects." All high-quality!

Truly \$100 worth of hardware alone! Check out prices yourself... you'll be amazed!

Unconditional 30-Day Guarantee: If you're dissatisfied in any way or for any reason, just return your Shop(s) within 30 days for an immediate, full refund. No questions asked!

Exactly what you receive. One 25-tray, polystyrene bin-cabinet (tray dividers form 45 bins), 1,012 terminals, connectors, and electrical accessories. 25 pre-printed, color-coded I.D. labels. One FREE Specifications Chart.

© 1978 D.R.I. Industries, Inc. Eden Prairie, MN *WORKSHOP'S and the "Electrical Terminal & Connector Shop" are trademarks of D.R.I. Industries, Inc.

D.R.I. Industries, Inc., 6864 Washington Ave. So., Eden Prairie, MN 55344

To Order—24-hour Phone Service: Send check, money order, or company purchase order for full amount. Or charge to any one of 5 major credit cards (see Order Coupon). Credit card buyers can also call our 24-hour, toll-free number: 800-247-2160 (in Iowa 1-800-362-2860).

UNCONDITIONAL 30-DAY GUARANTEE

Mail to and make remittance payable to: 12243
D.R.I. Industries, Inc., Dept. RE-128
6864 Washington Avenue South, Eden Prairie, MN 55344

Indicate Order: How many? _____
Electrical Terminal & Connector Shop(s) @ \$29.95 plus \$3.90 shipping and handling each.
Stanley Crimper(s) @ \$2.99 plus 75¢ shipping and handling each. (Limit: one per Shop purchased.)
How many? _____

Check (✓) Method of Payment: ☐ Check, money order, or company purchase order enclosed (MN residents add 4% sales tax).
☐ Charge it to: ☐ VISA/BankAmericard ☐ Master Charge ☐ American Express ☐ Diners Club ☐ Carte Blanche



CARD EXP. DATE _____

CARD NO. _____

SIGNATURE _____

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____



Not Available in Retail Stores!

DECEMBER 1978

The Big, NEW HEATHKIT® Christmas Catalog is just off the press!

Read about all the exciting new products you can give, or get, for real kitbuilding fun and satisfaction! We're the world's biggest and best source of quality money-saving electronic kits.

New

Computerized Weather Monitor

If you need weather information for ANY purpose, the ID-4001 is the way to get it! This microcomputer-based weather instrument digitally displays—time of day in 12 or 24-hour format; wind direction and magnitude; indoor and outdoor temperature; barometric pressure; and even wind chill factor! What's more, the computer's memory stores the highest and lowest data for each function so you can recall it for easy and accurate record keeping. Chart recorder and computer outputs provide even more versatility!

Includes remote transmitter with windcups and weathervane that have been wind-tunnel tested and an outdoor temperature sensor using the latest infra-red technology.



New

Hand-Held 2-Meter Transceiver

Superb features, specifications and a great low price make the VF-2031 a terrific buy in a hand-held two-meter transceiver. Features 8-channel simplex with ± 600 kHz offset using one crystal per channel, minimum 2 watts out, and 0.5 μ V sensitivity for 20 dB quieting. Includes built-in antenna, nickel-cadmium batteries and battery charger. An optional tone encoder and other accessories are also available. Units will be available in January, subject to FCC approval.



New

WH14 Line Printer for "Hard Copy" Computer Readout

Low-cost microprocessor-controlled printer is designed to give you a convenient "hard copy" printout of your computer programming. It eliminates losing and recalling program lines as they have scrolled off a CRT, it also provides handy printed lists of addresses, lists or other program data for editing and manipulation. Prints the standard 96-character ASCII set (upper and lower case) on a 5x7 dot matrix paper head. Designed for use with Heathkit computers and others as well. Available fully assembled and tested only.



New

Digital Readout Car Clock with Trip Timer

Versatile clock/timer for any vehicle shows time in hours and minutes, has 24-hour timer that reads to nearest second. Bright, easy-to-read display, low-power circuit doesn't drain battery.



New

Battery-Operated Portable Timing Light

Operates on its own rechargeable batteries for safety, convenience and complete portability. Ideal for use on boats or other vehicles where battery may be inaccessible. Also features dual-range tachometer, rugged pistol grip, extra-bright xenon tube for easy-to-see timing flashes.

New

Low-Cost Dual-Trace Oscilloscope

Low-priced dual-trace scope ideal for audio and TV servicing. Features outstanding sensitivity, extra-bright traces, selectable trigger, 7-position variable time base, DC to 5 MHz bandwidth.



HEATHKIT ELECTRONIC CENTERS* PROVIDE SALES AND SERVICE



*Units of Schlumberger Products Corporation.

Retail prices may be slightly higher.

ARIZONA — Phoenix, 85017, 2727 W. Indian School Rd. 602-279-6247.

CALIFORNIA — Anaheim, 92805, 330 E. Ball Rd. 714-776-9420; El Cerrito, 94530, 6900 Potrero Ave. 415-236-8870; Los Angeles, 90007, 2309 S. Flower St. 213-749-0261; Pomona, 91767, 1555 N. Orange Grove Ave. 714-823-3543; Redwood City, 94063, 2001 Middlefield Rd. 415-365-8155; Sacramento, 95825, 1860 Fulton Ave. 916-486-1575; San Diego, (La Mesa, 92041), 8363 Center Dr. 714-461-0110; San Jose (Campbell, 95008), 2350 S. Bascom Ave. 408-377-8920; Woodland Hills, 91364, 22504 Ventura Blvd. 213-883-0531.

COLORADO — Denver, 80212, 5940 W. 38th Ave. 303-422-3408.

CONNECTICUT — Hartford (Avon, 06001), 395 W. Main St. (Rte. 44) 203-678-0323.

FLORIDA — Miami (Hialeah, 33012), 4705 W. 16th Ave. 305-823-8280; Tampa, 33614, 4019 West Hillsborough Ave. 813-886-2541.

GEORGIA — Atlanta, 30342, 5285 Roswell Rd. 404-252-4341.

ILLINOIS — Chicago, 60645, 3462-86 W. Devon Ave. 312-853-3920; Chicago (Downers Grove, 60515), 224 Ogden Ave. 312-852-1304.

INDIANA — Indianapolis, 46220, 2112 E. 62nd St. 317-257-4321.

KENTUCKY — Louisville, 40243, 12401 Shelbyville Rd. 502-245-7811.

LOUISIANA — New Orleans (Kenner, 70062), 1900 Veterans Memorial Hwy. 504-722-6321.

MARYLAND — Baltimore, 21234, 13, E. Joppa Rd. 301-681-4446; Rockville, 20852, 5542 Nicholson Lane. 301-681-5420.

MASSACHUSETTS — Boston (Peabody, 01960), 242 And St. 617-631-8330; Boston (Wellesley, 02151), 165 Worcester Ave. (Rt. 9 just west of Rt. 128) 617-237-1510.

MICHIGAN — Detroit, 48219, 18645 W. Eight Mile Rd. 313-535-6490; E. Detroit, 48021, 18149 E. Eight Mile Rd. 313-772-0416.

MINNESOTA — Minneapolis (Hopkins, 55343), 101 Shad Oak Rd. 612-638-6371; St. Paul, 55106, 1645 White Bear Ave. 612-778-1211.

MISSOURI — St. Louis (Bridgeton) 63044, 3794 McKelvey Rd. 314-291-1650.

NEBRASKA — Omaha, 68134, 9207 Maple St. 402-391-2000.

NEW JERSEY — Fair Lawn, 07410, 35-07 Broadway (Rte. 4) 201-791-6935; Ocean, 07712, 1013 State Hwy. 35. 201-775-1231.

NEW YORK — Buffalo (Amherst, 14226), 3476 Sheridan

NO EXPERIENCE NECESSARY
Thousands of people with no electronics experience whatsoever — people who have never handled a soldering iron before — have proved that you can build any Heathkit product you want — and enjoy every moment of it! Simple step-by-step manuals make it easy as 1-2-3.



New Portable Room-Size Electronic Air Cleaner

An important addition to any household — it removes dust, and pollutants from any room in the house while cleaning and refreshing the air — and all for just pennies a day. It's especially important for sealed and tightly sealed houses where air can get "stale" after parties, smoking, etc. Features 3-way cleaning action to remove both large and small particles and household odors. Variable speed control that lets you "pick-clean" a room, then lower the speed to maintain a fresh air level. Available in some Southern-Pecan vinyl finish. Blends nicely with any decor. Easy NO SOLDER kit assembly too.

Learn about these and nearly 400 other fascinating and practical electronic kits you can build yourself for less, for satisfaction and for savings. Use this coupon for your catalog today!

PAST-TO-COAST

716-244-5470; White Plains (North White Plains, N.Y.), 7 Reservoir Rd. 914-761-7690.
— Cincinnati (Woodlawn, 45215), 10133 Springfield, 513-771-5850; Cleveland, 44129, 5444 Pearl Rd. 292-7553; Columbus, 43229, 2500 Morse Rd. 614-7200; Toledo, 43615, 48 S. Byrne Rd. 419-537-1887.
— ALABAMA — Oklahoma City, 73112, 2727 Northwest Freeway, 405-948-7093.
— PENNSYLVANIA — Philadelphia, 19149, 6318 Roosevelt, 215-268-0180; Frazer (Chester Co.) 19355, 630 E. Chester Pike (Rt. 30) 215-947-5555; Pitsburgh, 15235, 2 W. Penn Hwy. 412-824-3564.
— RHODE ISLAND — Providence (Warwick, 02886), Greenwich Ave. 401-738-5150.
— AS — Dallas, 75201, 2715 Ross Ave. 214-826-4053; Houston, 77027, 3705 Westheimer, 713-623-2090; Antonio, 78216, 7111 Blanco Road. 512-341-8876.
— OH — Salt Lake City (Midvale, 84047), 58 East 7200th, Opening Mid-November.
— VIRGINIA — Alexandria, 22303, 6201 Richmond Hwy. 703-5515; Norfolk (Virginia Beach, 23455), 1055 Independence Blvd. 804-460-0997.
— WASHINGTON — Seattle, 98109, 505 8th Ave., N. 682-2172.
— CONN — Milwaukie, 53216, 5215 W. Fond du Lac, 873-8250.



This FREE Catalog coupon can also be redeemed at any of the Heathkit Electronic Centers* nationwide. (See list at left.)

HEATH Schlumberger		Heath Company, Dept. 020-480 Benton Harbor, Michigan 49022	
Please send me my FREE Heathkit Catalog. I am not on your mailing list.			
Name _____			
Address _____			
City _____		State _____	
GX-359 _____		Zip _____	

CIRCLE 100 ON FREE INFORMATION CARD

ADVANCED Electronic Music

Products.... effects devices to computer controlled modular synthesizers. Select from experimenter's kits, step-by-step product kits or fully assembled professional equipment.



FREE color catalog
FMA ELECTRONICS, INC.
1020 W. Wilshire Blvd., Oklahoma City, OK 73116

SEND FREE CATALOG TO:

name _____

address _____

city _____ state _____ zip _____

FMA ELECTRONICS, DEPT. R

1020 W. WILSHIRE BLVD., OKLAHOMA CITY, OK 73116

CIRCLE 32 ON FREE INFORMATION CARD

Put Professional Knowledge and a COLLEGE DEGREE in your Electronics Career through

HOME STUDY



Earn Your DEGREE

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home-study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of directed but self-paced home study.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then to the B.S.E.E. degree. Our free bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. Write for Bulletin R-79,

Grantham College of Engineering

2000 Stoner Avenue

P. O. Box 25992

Los Angeles, CA 90025

Worldwide Career Training thru Home Study

CIRCLE 12 ON FREE INFORMATION CARD

Designing Digital Circuits

Continued from page 66

entry in the group below it, seeing if the differences in parentheses are the same (though they may be in any order), and seeing if the difference of the first numbers is a power of two. Indicate the end of the check of each group by a horizontal line in the next column, to show a new group there.

We now have a list of cubes that cover the 1-output boxes, similar to the cover created in the Karnaugh map. However, using the Karnaugh map, one can visually inspect to obtain the largest cubes to cover each 1-labeled box. This is not the case using the Q-M method, so a "cover map" must be drawn. On this map, we draw vertically the decimal equivalents of the cubes that are left unchecked in Fig. 12, and draw horizontally the decimal equivalent of each input that is to produce a 1 (but not a don't-care) output (see Fig. 13). A check is now placed in each box of

	4	8	9	12	13	14
4,12	✓			✓		
12,14				✓		✓
8,9,12,13		✓	✓	✓	✓	

FIG. 13—COVER MAP is obtained by listing the decimal equivalents of the unchecked cubes from Fig. 12.

the table under the column that is covered by a given row, i.e., the row labeled 4,12 has a check in columns 4 and 12.

Now we look at each column to see which rows are needed. We see that the column labeled 4 has only one check, in row 4,12. Thus row 4,12 (i.e., the term corresponding to 1-cube 4,12, as in the Karnaugh map) is essential to obtain an output of 1 when 4 is input, so we place a check by row 4,12. We then place a check above the columns numbered 4 and 12 to indicate that these have been covered. Column 8 has only one check, indicating row 8,9,12,13 is essential. A check is placed by this row and above columns 8, 9, 12 and 13. The only uncovered column is 14, which can only be covered by row 12,14. That row and column 14 are checked. The map now appears as shown in Fig. 14.

	4	8	9	12	13	14
4,12	✓			✓		
12,14				✓		✓
8,9,12,13		✓	✓	✓	✓	

FIG. 14—ESSENTIAL ROWS are determined and then confirmed by placing a check next to them.

All columns with only one check in them should be handled first in this manner. For the remaining unchecked columns with more than one table entry

check, choose the largest possible cubes to cover the most unchecked columns. In this manner, the function will be completely reduced. In any case, all columns must have a check above them when done, so that all output situations are covered. Any rows that do not have a check beside them are eliminated.

The remaining rows (those with a check to the left of them) then correspond to the inputs to each of the gates. To determine the inputs, the decimal numbers in the labels of each row are written in binary, and the input bits that do not change between the numbers are the inputs to the gate. For example, Fig. 15 illustrates that for row 8,9,12,13, bit a_1

	a_1	a_2	b_1	b_2
8	1	0	0	0
9	1	0	0	1
12	1	1	0	0
13	1	1	0	1

FIG. 15—TRUTH TABLE of final function is shown.

must always be on, and bit b_1 must always be off, while a_2 and b_2 may be either 0 or 1, to generate a 1-output for this term of the expression. Thus, the output is 1 if $a_1 b_1 = 1$. Similarly, row 4,12 indicates a 1-output if $a_2 b_2 = 1$, and row 12,14 indicates a 1 output if $a_2 b_2 = 1$. Our final function is thus:

$$f = a_1 b_1 + a_2 b_2 + a_2 b_2$$

This function is implemented as shown in Fig. 16.

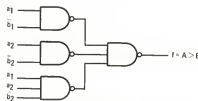


FIG. 16—LOGIC CIRCUIT implementation of truth table shown in Fig. 15.

Next month we will discuss multiple-output functions and sequential circuits along with cover maps and truth and state tables used in digital circuit design. **R-E**



"Don't let on you know—but actually it's just a simple project requiring the plugging of a few units into a prewired PC board."

patches, etc., because they deteriorate the quality of the audio signal. M & K claims its cable has an inductance that is 12 times lower than No. 12 zip cord and comparable resistance.

The Fulton cable uses silver-plated wire; the tips are finished off in spade lugs; 30-foot sections of No. 16 wire cost \$1.34-per-foot; and No. 12 cable costs \$2.60-per-foot.



FIG. 6—POLK AUDIO SPEAKER CABLE consists of 144 strands of low-resistance wire braided into two sets of conductors at right angles to each other.



FIG. 7—AUDIO SOURCE's High Definition cable, with 10-ohm impedance, has 10 pairs of braided wire, connected in parallel and with special tips.


The Polk cable comes in a round version (see Fig. 6) at \$1.34-per-foot; in four different lengths, up to 50 feet; and is claimed to have a characteristic 9-ohm impedance. The Polk cable consists of 144 strands of separately insulated, low-resistance wire braided into two sets of conductors that constantly lie at right angles to each other to avoid inductance.

All the braided cables are arranged this way because it is claimed that this eliminates interference between the adjoining magnetic fields, thus minimizing self-inductance. In addition, the two polarities are brought as close as possible to each other to insure minimal and correct characteristic impedance.

The Mogami cable's stacked arrangement has an inner core of nonconductive material for spacing and extra strength; a final conductor layer has 60 strands of wire about equal to No. 11; a layer of insulation made of tough synthetic material; and another conductor layer wound

continued on page 102

How do you really use a multimeter?

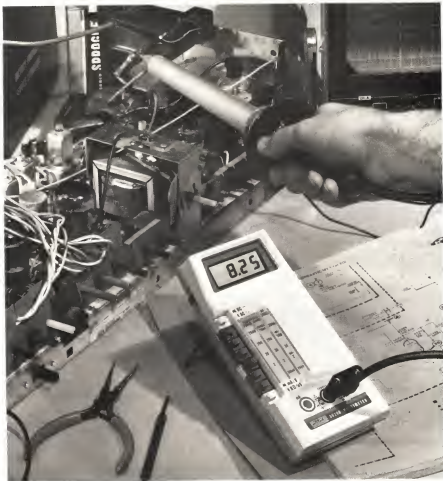

Usually at your bench, in the shop, shared with others. And, if it's a Fluke multimeter, you use it with confidence.

Now you can carry that same bench precision on the job. Introducing the new Fluke 820A DMM for only \$169.

This rugged beauty packs more field-valuable features than any other DMM available, at any price. And that means field versatility when you need it most.

The 820A has six resistance ranges, including a 20 megohm range for those special high-resistance TV components. Plus, you can measure focus dividers, pcb and capacitor leakage clear up to 10,000 megohms with the new conductance function. And conductance allows you to measure transistor beta—unique

with the 820A.

Ever damaged your meter in the fly-back circuit? Rest easy. The 820A is MOV-protected to 6000V against hidden spikes and transients.

Your 820A comes with a full-year warranty, with worldwide service back-up. Regardless of what happens to it, we'll fix it inexpensively and quickly, making the 820A a truly cost-effective investment.

Call (800) 426-0361*, toll free. We'll tell you the location of the closest Fluke office or distributor for the best value in DMMs around.

Price U.S. only.

*Alaska, Hawaii and Washington residents—please call (206) 774-2481.

The DMM for Home Electronics Experts.

2507-7207



CIRCLE 79 ON FREE INFORMATION CARD

THE COUNTERS YOU REALLY WANT

MODEL 380



MODEL 385

AT AFFORDABLE PRICES.

A Model for every need.

- MODEL 380.**
1 Hz to 80 MHz, 10 ppm \$209
- MODEL 380X.**
1 Hz to 80 MHz, 1ppm \$269
- MODEL 385.**
1 Hz to 512 MHz, 10ppm \$419
- MODEL 385X.**
1 Hz to 512 MHz, 1ppm \$499

Perfect for communications, CB, audio, TV and digital work, servicing and laboratory applications.

All 4 field-proven models feature full 7-digit display with automatic decimal and full autoranging. Our exclusive SPEED READ mode provides fast update (5/sec) time for easy tuning and adjusting.

Handsome, rugged metal case with brushed aluminum panel including all-angle tilt stand. (Low cost rack mounting kits for standard 19" rack also available.) All models come packaged in a plastic carrying case that protects the unit in shipment and in use.

Why settle for less than the best. See these hard-working counters at your distributor now.

If you're outside of Ohio, call us toll free at 800-321-4664 for the name of your nearest Hickok distributor.

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

CIRCLE 55 ON FREE INFORMATION CARD

new products

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside back cover.


DIP SOCKET low-profile unassembled Molex sockets available in 14-pin and 16-pin versions. IC DIP sockets come in display card package containing four terminal carrier strips and four IC nests. When assembled, components form two complete DIP sockets whose terminals are made of 70/30 spring-tempered tin-plated brass. Assembly instructions are given on the back of the



card. Socket assemblies are available from Waldom distributors. Prices: parts for two 14-pin sockets, 95¢; two 16-pin sockets, \$1.—Waldom Electronics, Inc., 4301 W. 69th St., Chicago, IL 60629.

CIRCLE 114 ON FREE INFORMATION CARD

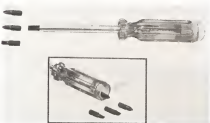MAGNETIC SCREWDRIVER, model 70035, has magnet built into the shank to hold interchangeable bits plus the screw. Confor dome handle has a removable dome cap that keeps three extra bits



stored inside handle while fourth bit is being used. Comes with 3/16-in. and 1/8-in. slotted, No. 1 and No. 2 Phillips bits.—Vaco Products, 1510 Skokie Blvd., Northbrook, IL 60062.

CIRCLE 115 ON FREE INFORMATION CARD

WIRELESS REMOTE CONTROL, model GP-500, attaches to the antenna terminals of any black-and-white or color TV set. The unit's 10-channel capacity is tunable to either VHF or UHF, and each channel can be preset. A built-in RF preamplifier has a power gain of 30 dB (typical). Other specifications include: Maximum noise—90 dB (VHF) and 12 dB (UHF); IF rejection—40-dB minimum (VHF) and 60-dB minimum (UHF); minimum

image rejection—50 dB (VHF) and 40 dB (UHF); input impedance—75 ohms; tuner frequency bands—55.25 to 83.25 MHz, 175.25 to 211.25



MHz (VHF); 471.25 to 888.25 MHz (UHF). The model GP-500 components are encased in two-tone high-impact plastic; the receiver measures 6 × 10 1/4 × 3 1/4 inches; the transmitter measures 2 1/2 × 5 1/4 × 1 inch. Suggested list price: \$99.95.—GP Electronics, Ltd., Subsidiary of Gold Peak Industries, Ltd., Box 261, Middletown, NJ 07748.

CIRCLE 116 ON FREE INFORMATION CARD

SOLDER STRIP PACKAGE, Emergency Solder, is designed for on-the-spot repairs and requires only a match to melt the solder. Multiple cores of noncorrosive, nonconductive flux are contained in the strips. Emergency Solder can be used on any solderable metal (not suitable for aluminum). Package includes 36 inches of solder strip, and complete directions.—Multicore Solders, Westbury, NY 11590.

CIRCLE 117 ON FREE INFORMATION CARD

DUAL-TRACE 30-MHz OSCILLOSCOPE, model LBO-520, offers built-in 120-ns delay line. Among the unit's other features are a 5 mV-per-division vertical sensitivity; display modes include Channel 1, Channel 2, alternate, subtract, add and X-Y modes; continuously variable sweep speeds from 0.2 µs-per-centimeter to 0.5 second-per-centi-




meter; ×10 magnification. In addition, the model LBO-520 provides trace rotations; + and - polarity; an uncalibrated warning indicator lamp; and lever-type input switches. Priced at under \$1000, the instrument comes with contoured

handle that doubles as locking bale; probes and accessories are included.—**Leader Instruments Corp.**, 151 Dupont St., Plainville, NY 11803.

CIRCLE 128 ON FREE INFORMATION CARD

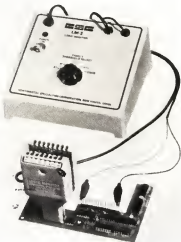LOGIC MONITOR, model LM-2, is a self-powered unit that clips right onto IC under test; a series of 16 LED's at top of the clip follow IC pin pattern. A rotary switch selects the proper logic threshold



for monitoring RTL/DTL, TTL/HTL and CMOS circuits. A separate cable for CMOS circuits uses the circuit voltage to determine the logic level and operates up to a 30-kHz input frequency at 50% of duty cycle. The model LM-2, with self-contained 117 VAC 50- to 60-Hz power supply, is priced at \$129.95. A 220 VAC 50- to 60-Hz model is also available.—**Continental Specialties Corp.**, 70 Fulton Terrace, New Haven, CT 06509.

CIRCLE 129 ON FREE INFORMATION CARD

SCREWDRIVER SET, model 31802. Five-piece mechanic's screwdriver set comes packaged in heavy vinyl pouch. It contains one $\frac{1}{4}$ x 4-inch blade ($\frac{1}{4}$ x 2 $\frac{1}{2}$ -inch handle); $\frac{3}{16}$ x 4-inch blade (1 x $\frac{3}{4}$ -inch handle); $\frac{1}{8}$ x 4-inch blade (1 $\frac{1}{4}$ x $\frac{3}{4}$ -inch handle); $\frac{1}{8}$ x 3-inch blade with No. 1 tip



(1 x $\frac{3}{4}$ -inch handle); and $\frac{1}{8}$ x 4-inch blade with No. 2 tip (1 $\frac{1}{4}$ x $\frac{3}{4}$ -inch handle). Screwdrivers are made of chrome vanadium steel, with cross-ground tips and easy-grip handles. Suggested resale price, \$7.63.—**Hunter Tools**, 9674 Telstar Ave., El Monte, CA 91731.

R-E

CIRCLE 130 ON FREE INFORMATION CARD

Great Advice:



Give a Great Vise!

PanaVise... a great gift idea. Everyone loves a PanaVise. It tilts, turns and rotates every which way to quickly and securely position electronic parts and PC boards exactly where wanted.

Sturdy all metal construction. Model 396 PanaVise shown. Available at your electronic distributors, boxed ready to go, along with a variety of other PanaVise interchangeable bases, holders and accessories.

PANA VISE Write for FREE brochure and distributor list.
Dept. CE5, 2850 29th Street, Long Beach, CA 90806

CIRCLE 52 ON FREE INFORMATION CARD

SUBSCRIBE AND SAVE!



Get every excitement-packed issue of Radio-Electronics delivered to your door. And save money, too—up to \$9 off newsstand prices! Use the handy coupon and subscribe today!

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80323 (please print)

Name		
Address		
City	State	Zip Code

Indicate the offer you prefer:
☐ 1 Year—12 issues ONLY \$9.98 (You save \$2.02 off newsstand price.)
☐ 2 Years—24 issues ONLY \$19.00 (Save More! \$5.00 off newsstand price.)
☐ 3 Years—36 issues ONLY \$27.00 (Save Even More! Save \$9.00 off newsstand price.)
☐ Payment enclosed ☐ Bill me
☐ Check here if this is a new subscription.
☐ Check here if you are extending or renewing your subscription.
 Extra Shipping: Canada \$3.00 per year, all other countries \$5.00 per year.

Microprocessor Accessories.



Get the complete Bugworks® catalog and see E&L's complete line of micro-accessories and aids for versatile, professional

circuit design. All compatible with both E&L Microprocessor systems and many others: from Hex Keyboards for E&L's Mini Micro-Designer® (MMD-1) and MMD-1 Student Stations, to breadboarding cards and aids for the Altair/Imai and DEC systems. E&L has the products, instruments and educational materials to help you master the world of electronics. See them in your free copy of the complete Bugworks catalog.



E&L INSTRUMENTS, INC.
61 First Street, Derby, Conn. 06418
(203) 756-8774, Telex No. 96 3536



CIRCLE 10 ON FREE INFORMATION CARD

3 Automotive instruments in 1

Today's most exciting automotive accessory, AUTOCOMP, is actually three complete instruments in one — each operated by electronic microprocessor control. AUTOCOMP mounts easily in or on your dash and provides large LED readouts of these functions by pushbutton control. With this valuable data at your fingertips, you can significantly reduce fuel bills by monitoring and improving your driving habits.

DIGITAL CLOCK

AUTOCOMP is a digital clock. Press the TIME button and the LED display reads the correct time (in hours and minutes). The clock may instead be used to display ELAPSED TIME.

MPG METER

AUTOCOMP is also a true MPG meter, utilizing a patented flow sensor and a speed sensor to compute instantaneous miles-per-gallon or average miles-per-gallon as you drive. Press the INST MPG button and read how many miles per gallon your vehicle is attaining at each moment. Press the AVE MPG button, and read the average miles per gallon the vehicle has attained since the last reset (up to 200 MPG).

TRIP COMPUTER

AUTOCOMP is a complete trip computer. Press the FUEL button and read the amount of fuel the vehicle has used since last reset (up to 1000 gallons). Press the DIST button and read the distance the vehicle has traveled since last reset (up to 1000 miles).

AUTOCOMP can be installed on most American and Japanese (special adapter is required at \$9.95) make autos and vans except those with fuel injection. It is supplied with all necessary components and hardware and illustrated instructions that make it easy to install. AUTOCOMP is covered by a 1 year Manufacturer's Limited Warranty.



\$99.95 FOR ORDERS ONLY
CALL TOLL FREE ANYTIME!
1-800-423-2355 Ext. 601
In California 1-800-232-2175 Ext. 601
For more information call 805-965-1015

SPACEKOM-AUTOCOMP
212 E. Gutierrez Street
Santa Barbara, CA 93101

Please send me AUTOCOMP(s) at \$99.95 each.
(California residents must add 6% sales tax.)

Car on which AUTOCOMP will be installed

Make _____ Model _____ Year _____

Factory Cruise Control? ☐ Yes ☐ No

Total enclosed (Cal. res. add tax) \$ _____

USE YOUR CHARGE CARD! (Postage and handling will be added.)

☐ BankAmericard (VISA)

☐ Master Charge (Interbank # _____)

Charge # _____ Exp. Date _____

Signature _____

PRINT NAME _____

ADDRESS _____

CITY _____


STATE _____ ZIP _____

CIRCLE 67 ON FREE INFORMATION CARD

computer products

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside back cover.

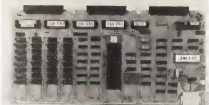Z80 COMPUTER BOARD, 90F/MPH, is a Z80-based, single-board device with resident floppy-disc controller that supports up to four 5 1/4-inch or 8-inch single-density floppy-disc drives. The basic board contains 4K bytes dynamic RAM (expandable to 64K bytes); six 2708/2716 EPROM sockets; 1K byte resident PROM monitor




with static RAM scratch pad; PROM programmer; counter/timer; hardware UART with RS232C/TTY serial I/O; plus a programmable 8-bit parallel I/O port with two expansion sockets for additional PIO IC's. Prices: single unit, \$995; OEM discounts available.—Quay Corp., Box 386, Freehold, NJ 07728.

CIRCLE 121 ON FREE INFORMATION CARD

COMPUTER PRINTOUT PICTURES are now available in a 23-picture set printed on 58 14 x 11-inch sheets. The set includes four pictures of Snoopy, five Christmas scenes, Abe Lincoln and others. Price: \$7.75.—Data Analysis Systems, Dept. F, Box 162, Franktown, CO 80116.

CIRCLE 122 ON FREE INFORMATION CARD

PROTOTYPE BOARD is a two-sided wire-wrap board that comes in kit form, complete with layout, instructions, 4 matching heat sinks plus hardware mounting, and 2 yards of AWG No. 18 wire. One side of the 10 x 5.5-inch board is 18 SS-100-bus compatible with 100 contacts spaced at 0.125-inch intervals. The board's other side has 50 contacts spaced at 0.156-inch intervals for the SS-50 bus but is only electrically compatible with the SS-50 bus. An SS-50 bus extender board is also available with a 22-slot maximum

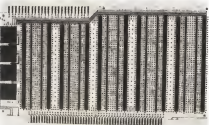

capability (no edge connectors are provided). The board accepts from 14- to 40-lead DIP packages, and additional space is provided for up to 26 or more resistors or transistors. The board also has provision for three-way keyed mounting, 2 card ejectors, filter capacitors for the voltage regula-

tors and transient suppressor capacitors et al. approximately 6-inch spacing. Prices: kit, \$29.95; SS-50 bus extender board, \$49.95; edge connectors available separately.—AUM-Ideas, Box 2582, Richardson, TX 75080.

CIRCLE 123 ON FREE INFORMATION CARD


COMPUTER SYSTEM, PeCos I, is a complete personal computing system that does not require hookup to any RF adapters, TV sets, audio cassettes, etc. It provides 24K ROM and 16K RAM; a 60-key keyboard with upper and lower case; a 9-inch CRT displaying 16 lines of 40 characters each with automatic scrolling and speed control; built-in dual cassette decks, each with 80K byte storage capability; 6502 microprocessor; power supply; and RS 232 port for connecting a printer. Software is implemented in PeCos, an English-like language derived from Rand JOSS; and includes full 9-digit floating point



arithmetic computation. The unit measures 18 1/2 x 19 1/2 x 8 1/2 inches. Suggested retail price: \$1695.—APF Electronics, Inc., 444 Madison Ave., New York, NY 10022.

CIRCLE 124 ON FREE INFORMATION CARD

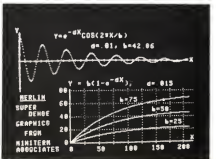GRAPHIC/TEXT VIDEO DISPLAY INTERFACE, Merlin, comes assembled and tested, or as a kit. It can be used to interface to any S-100 bus computer and provides 4K bytes of ROM, keyboard input port, plus text and graphic displays. The text display consists of 20 lines, 40 characters-per-line, suitable for BASIC and assembly programs. The medium-resolution bit-mapped



graphic display is 160H by 100V with expansion to 320H by 200V using super-dense graphic option.

The keyboard contains the following modes: edit function, scrolling, monitor, 25 cursor/edit functions, graphic subroutines and graphic drawing. The display address and display mode (text, graphic or "split screen") are software-programmable. Prices: assembled (with 4K ROM control and super-dense graphic option) \$499.95; kit (without ROM software) \$299.95.—MiniTerm Associates, Inc., Dundee Park, Andover, MA 01810.

CIRCLE 125 ON FREE INFORMATION CARD

PROGRAMMABLE TERMINAL SYSTEM, EXOR 68, is multifunctional—consists of basic display unit with 12-inch CRT, six keyboard options and a group of micromodule subassembly boards. The CRT display unit consists of video monitor that can display 128 ASCII characters in 24 lines (up to 1920 characters); switches select word length, baud rate, communications mode and modem



control. Other features include inverted cursor, scrolling and page/edit/protect display modes; remote or keyboard data entry capability; and optional motherboards. Basic display unit is available separately for end applications without keyboards. Keyboard options include Standard TTY/control key format plus 5 other variations. End-use micromodule options range from partial computers (memory, interface, etc.) to complete single-board assemblies; all are compatible with EXOR 68 system. Basic display unit with extended communications and display features plus keyboard end cable assembly sells for \$2600 (approx.) in single quantities.—Motorola Microsystems, 3102 N. 56th St., Phoenix, AZ 85018.

CIRCLE 126 ON FREE INFORMATION CARD

COMPUTER TERMINAL, model OE1000, comes as a kit or assembled, and interfaces to any computer having a 300-baud serial data output port. It offers the full duplex mode with either a 20-mA current loop or an RS 232C voltage swing. Displays 96 ASCII characters and 32 special characters in a 16-line by 64-character format,



with either upper and lower case or TTY modes. Other features are full cursor control, automatic scroll, erase to end of line, erase to end of screen and clear screen. Prices: kit, \$275; assembled, \$350.—Oto Electronics, Box 3068, Princeton, NJ 08540.

R-E

CIRCLE 127 ON FREE INFORMATION CARD

FORDHAM BEST BUYS

HICKOK OSCILLOSCOPES

High Performance • American Made • Discount Prices!

30 MHz, Dual trace

11.7 MS risetime • Fixed delay for leading edge viewing of fast rise time signals • Stable pushbutton triggering to 50 MHz • High and Low pass filters • Bright, ultra sharp trace POA CRT • Deluxe probe kits included • Full time 4X expansion and multitrace horizontal position control • Ideal for logic and pulse circuits, microprocessor applications.

SPECIFICATIONS:

VERTICAL


Range: 10mV/cm in 11 calibrated steps plus variable control.
Accuracy: $\pm 4\%$.
Frequency Response: DC to 30 MHz.
Risetime: 11.7ns.
Overshoot: 4% or less.
Vertical Modes: Channel A only; Channel B only; Alternate A & B, Chopped A & B, Add (A + B).

TIME BASE

Sweep Rates: 2 SEC/OIV to 0.05 SEC/OIV in 24 calibrated steps plus variable control.
Accuracy: $\pm 4\%$. Except 7% slowest 3 speeds.

TRIGGERING

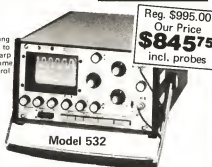Modes: AC-HF, AC-LF
Sources: Line, Internal, External.
Slope: Positive and negative; continuously Variable level.
Sensitivity: Internal, 1/2 division to 30 MHz



GENERAL

CRT: 4-inch flat faced round with viewing area of 6 x 10 divisions. P31 phosphor with 3.8 kV accelerating voltage.
Power Requirements: 105-125V, 50-400 Hz, 35 watts.

DIMENSIONS AND WEIGHT

6 7/8" h x 11 1/4" w x 17 3/4" d, 27 pounds.

ACCESSORIES

Rack mounting kit RM-4 (P/N 100-138) also available.

SPECIFICATIONS:

VERTICAL

Range: 10mV/cm to 50V/cm in 12 calibrated steps. Variable control from 5mV/cm to 50V/cm.
Accuracy: $\pm 3\%$.
Frequency Response: DC to 15 MHz.
Risetime: 24ns.

TIME BASE

Sweep Rates: 0.2 SEC/cm to 0.5 μ SEC/cm (0.1 μ SEC/cm with X5 expand) in 18 calibrated steps. Variable control from 0.1 μ SEC/cm to 1 SEC/cm.
Accuracy: $\pm 5\%$.

TRIGGERING

Slope: $\pm 6^\circ$. Variable level control.
Sensitivity: 1 division (on CRT) to 27 MHz guaranteed.
TV Sync: Separation circuitry permits locking to TV video waveform. TV-H (Line) and TV-V (Frame) sync automatically selected by TIME/CM switch.

EXTERNAL HORIZONTAL (X-AXIS):

Variable from 0.5V/cm to 50V/cm with X5 expand.

Frequency Response: DC to 1 MHz.

GENERAL

CRT: 5-inch flat faced round with viewing area of 8 cm x 10 cm.
Z-Axis: (Intensity Modulation) Rear panel connector for display blanking by 5V signal (TTL compatible).
Power: 105-125V, 50-400 Hz, 35 watts.

DIMENSIONS

16 5/8" h x 7" w x 17 1/2" d.

ACCESSORIES

Rack mounting kit RM-3 (P/N 100-205) also available.



15 MHz, Dual trace

24ns rise time • 15 MHz response for all signal levels • 5 mV sensitivity • Footprint pushbutton triggering to 27 MHz • TV Sync separators built-in • Sweep speed • TIME/cm switch automatically selects line or frame sync as well as Chop or Alternate sweep in Dual mode • Perfect for VCR, TV, and audio service as well as digital and industrial work • CHA, CHB, Qual, Add, Subtract modes • TTL compatible intensity modulation (X-AXIS): Large 8cm x 10cm viewing area • Front-panel Vectorscope operation.

15 MHz, Triggered Sweep

• Same specs and performance as Model 517 except single trace • 15 MHz frequency response • 5mV sensitivity • TV Sync separators built-in • Bright 8cm x 10cm display • Front Panel vectorscope operation • Lightweight, portable • Designed for industrial and consumer service applications as well as educational and laboratory purposes.



Immediate Delivery...
To Place Your Order

Call TOLL FREE (800) 645-9518

N.Y. State call (516) 752-0050

FORDHAM
YOUR ONE STOP DISCOUNT CENTER

Send for new 1978 catalog of over 3,000 items. 164 pages of test equipment. CB, test, video, components and electronic supplies.

Mastercharge, BankAmericard, VISA and C.O.D. accepted
ADD \$3.00 TO COVER SHIPPING AND INSURANCE
RADIO SHACK CO.

FREE

CIRCLE 77 ON FREE INFORMATION CARD

MATHEMATICS ELECTRONICS ENGINEERING MATHEMATICS ADVANCED MATHEMATICS DIGITAL TECHNOLOGY

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

WE ARE THIS SURE:—you order your lessons on a money-back guarantee.

In plain language, *if you aren't satisfied you don't pay*, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

**The INDIANA
HOME STUDY INSTITUTE**
EASTERN DIVISION
P.O. BOX 1189
PANAMA CITY, FLA 32401

CIRCLE 14 ON FREE INFORMATION CARD

stereo products

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside back cover.

DIRECT-DRIVE TURNTABLE, model PS-Ti, is a semiautomatic unit that features a linear-torque, brushless, slotless DC servomotor with ring-shaped magnet and fixed coil. The speed-monitoring system consists of a magnetic coating on outer rim of the platter, which is tracked by a magnetic head to detect speed variations. Other



features include a J-shaped tonearm (statically balanced to provide 7–9-Hz resonance), counterweight with stylus pressure gauge, antiskating device, safety clutch, reject button and illuminated strobe. Suggested list price: \$130.—Sony Corp. of America, 9 W. 57th St., New York, NY 10019.

CIRCLE 113 ON FREE INFORMATION CARD

AM/FM STEREO RECEIVER, model CR-3020, incorporates preamp containing peak-reading meters, coil-head amplifier, signal meter, LED display and two headphone jacks (with separate



volume control). General specifications: continuous RMS power, 200 watts-per-channel (at 4 ohms, 0.05% THD); 20-Hz–20 kHz THD (phono 1 & 2 to record output), 0.003% at 5 volt output; input sensitivity (phono 1), 2 mV; frequency response (aux, tape 1 & 2 to speaker output) 5 Hz–100 kHz, $\pm 3 \pm 2$ dB; S/N ratio (phono 1 & 2) 96 dB (10-mV input).

FM section: usable sensitivity at 300 ohms, 11.2 dB; 50-dB quieting (mono) 15.3 dB, (stereo) 37.2 dB; IHF distortion (stereo), 0.1% (local), 0.6% (DX). AM section: 1000-kHz selectivity, 45 dB (± 10 kHz), 35 dB (± 9 kHz).

The model CR-3020 comes in an ebony cabinet, measures 24" X 7 1/4" X 19 1/2" inches and weighs 81 lb, 8 oz. Price: \$1400.—Yamaha International Corp., 6000 Orangethorpe Ave., Buena Park, CA 90622.

CIRCLE 112 ON FREE INFORMATION CARD

CEILING SPEAKERS, models DK5-F, RS69-F and RSQ8-F are made of acrylic plastic and feature cloth-roll suspension, 1 1/2-lb magnet construction and an aluminum voice coil. The speakers are easily mounted and come with complete mounting instructions. The model DK5-F (shown) is a 5-inch two-way speaker with a 360° swivel tube for directional sound and a decorative grille. Its specifications include a 48-Hz–20-kHz frequency response, 8-ohm impedance, 65-Hz resonant frequency and 25-watt power handling capability. The model RS69-F is a 6 X 8-inch two-



way recessed round speaker with a 35-Hz–19,500-Hz frequency response, 8-ohm impedance, 50-Hz resistant frequency and 40-watt power handling capability. The model RSQ8-F is an 8-inch two-way recessed square speaker with a white exterior and chrome grille. Its specifications are: a 28-Hz–21-kHz frequency response, 8-ohm impedance, 50-Hz resonant frequency and 45-watt power handling capability. List prices: model DK5-F, \$54.95; model RS69-F, \$64.95; model RSQ8-F, \$69.95.—Rohn Electronics, Ltd., 5 Pearsall Ave., Glen Cove, NY 11542.

CIRCLE 111 ON FREE INFORMATION CARD

AM/FM TAPE CAR STEREO, 8-track model 873 and cassette model 633, both deliver 20 watts-per-channel RMS; the tuner sections feature FET frontends and PLL circuitry in the multiplex



decoder, plus local/distance switch and FM muting. The model 873 player has indicator lights and a dial-in-door cartridge slot. The model 633 cassette player (shown) provides automatic reverse, pushbutton eject, locking rewind/fast forward switches, plus tape direction indicators.



NATCAM
catalog
Shipping center for small and precision tools

A fine selection of small tools, measuring instruments, hard-to-find items for shop, home and lab. Convenient one-stop shopping for technicians, engineers, craftsmen, hobbyists. Major credit cards accepted, satisfaction assured. Get your NATCAM catalog today.


National Camera, Inc.
2000 West Union Ave., Dept. GBF
Englewood CO 80110 USA

CIRCLE 19 ON FREE INFORMATION CARD

Both units contain bass/treble, balance/fader, and volume/loudness controls. Suggested retail prices: model 873, \$209.95; the model 633, \$244.95—J.L.L., Dept. P, 737 W. Artesia Blvd., Compton, CA 90220.

CIRCLE 106 ON FREE INFORMATION CARD

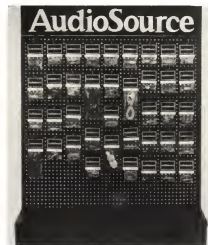HI-FI CABLES/CONNECTORS, full line of stereo cables and connectors for all systems. Product line includes 2-pin DIN speaker, line plugs and sockets; 3- and 5-pin DIN plugs and sockets; leads with either RCA or DIN plugs and sockets in



different lengths and configurations; leads with combined RCA/DIN plugs or sockets; a headphone extension cable; and an FM dipole antenna.—AudioSource, 1185 Chess Drive, Foster City, CA 94404.

CIRCLE 110 ON FREE INFORMATION CARD



NEW EICO 480 TRIGGERED SWEEP SCOPE

100% Solid State • Includes 10:1 Probe

More Professional scope performance for your money! DC to 10 MHz bandwidth, AC and DC coupling, 11 position calibrated attenuator, 10 mV/cm sensitivity, push-button operation. Outstanding features: Built-in TV Sync Separator; Digitally controlled trigger circuits; reference baseline display; calibrated 21 step sweep speed; Fully regulated power supply; Custom Bezel for standard camera mounting. **Assembled \$449.95**

FREE '78 EICO CATALOG

Check reader service card or send 50¢ for first class mail. See your local EICO Dealer or call (516) 681-9300, 9:00 a.m.-5:00 p.m. EST. Major credit cards accepted. **EICO-108 New South Rd. Hicksville, N.Y. 11911**

CIRCLE 8 ON FREE INFORMATION CARD



You can build a better organ than you can buy!

A magnificent Schober Electronic Organ

What a marvelous way to put your special talents to work! With our Schober Electronic Organ Kits and your skill, you can build yourself some very special satisfaction, and a lifetime of great music!

Schober Organs are literally far superior to comparably-priced "ready-made" units. You could actually pay twice as much and get no better organ...and miss the fun of assembling it yourself. A PC board at a time, component by component, you'll assemble your own "king of instruments." And when you're done, you'll wish there was more to do. And there is! For then, Schober will help you learn to play, even if you've never played a note before!

Schober Organ Kits range from \$650 to \$2650, and you can purchase in sections to spread costs out...or have two-year time payments. Combine the incomparable quality of Schober components with your talent...and produce a far better organ than you can buy!

Thousands of others have, ever since 1955.

You can have all the details, without cost or obligation. Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a record that lets you hear as well as see Schober quality.) Why not clip it right now, before you forget?

The Schober Organ Corp., Dept. RE-181
43 West 61st Street, New York, N.Y. 10023

- ☐ Please send me Schober Organ Catalog
☐ Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

CIRCLE 66 ON FREE INFORMATION CARD

BYTE®

**The leading magazine in the
personal computer field**

BYTE is the magazine for the creative home computer experimenter. BYTE tells you everything you want to know about personal computers, including how to construct and program your own system.

Home computers are now practical and affordable. Low cost peripherals have resulted in more hardware and software. More applications than you could imagine. BYTE brings it all to you. Every issue filled with stimulating, timely articles by professionals, computer scientists and serious amateurs.

BYTE, and BYTE logo are trademarks of BYTE Publications, Inc.



Fill in the coupon today. Read your first copy of BYTE; it's everything you expected, honor our invoice. If it isn't, just write "CANCEL" across the invoice and mail back. You won't be billed, and the copy is yours.

Allow 6 to 8 weeks for processing.
BYTE Subscription Dept 800-258-5485

BYTE Subscription Dept • P.O. Box 590 • Martinsville, NJ 08836

PLEASE ENTER MY SUBSCRIPTION FOR:

- ☐ One year \$15 (12 issues) ☐ Two years \$27 ☐ Three years \$39
☐ Check enclosed (entitles you to 13 issues for price of 12)*
☐ Bill Visa ☐ Bill Master Charge ☐ Bill me*

Card Number _____

Expiration Date _____

Signature _____

Name (please print) _____

Address _____

City _____

State/Country _____

Code _____

FOREIGN RATES (To expedite service, please remit in U.S. Funds)

- ☐ Canada or Mexico \$17.50 — One Year ☐ Two years \$32 ☐ Three years \$46.50
☐ Europe \$25 — One Year (Air delivered)
☐ All other countries except above \$25 — One Year (surface delivery)

*North America only

Air delivery available on request

7G88

CIRCLE 80 ON FREE INFORMATION CARD

BEST IN NEW ELECTRONICS BOOKS!

Digital Interfacing With An Analog World	406 p., 271 il.	\$8.95
How To Design/Build Your Own Custom TV Games	322 p., 150 il.	\$7.95
The Complete Handbook of Robotics	364 p., 137 il.	\$7.95
24 Tested, Ready-To-Run Game Programs in BASIC	266 p.	\$5.95
Beginner's Guide to Computers/Microprocessors	268 p.	\$8.95
Direct Current Motors—Characteristics & Applications		\$14.95
301 Dynamic Electronic Circuits	268 p., 363 il.	\$6.95
How To Design, Build, Test Complete Speaker Systems	336 p.	\$6.95
Antenna Construction Handbook for Ham, CB & SSB	238 p.	\$5.95
First Class Commercial FCC License Study Guide	378 p.	\$7.95
Radar Detector Handy Manual	88 p., 48 il.	\$2.25
Jap Radio, Record, Tape Player Schem./Soc. Manual	171 p.	\$7.95
CB's Handy Manual of Base Stations	66 p., 55 il.	\$2.50
The Handbook of Telephones & Accessories	432 p., 215 il.	\$9.95
Locust Electronic in Cars, Buses, Planes, Trucks & RV's	384 p.	\$7.95
The BASIC Cookbook	140 p., 49 il.	\$4.95
How to Repair Video Games	276 p., 182 il.	\$7.95
Beginner's Guide—Designing/Building Trans. Radios	140 p.	\$4.95
Towers International FET Selector	140 p.	\$4.95
How to Design/Build Electronic Instrumentation	420 p.	\$9.95
How to Repair Home & Slide Projectors	384 p., 270 il.	\$7.95
Understanding Sound, Video & Film Recording	140 p., 74 il.	\$5.95
Build-In Book of Solar Heating Projects	196 p., 111 il.	\$4.95
Hdbk. of Solar Flame Monitoring/Progn. Forecasting	196 p.	\$4.95
57 Practical Programs & Games in BASIC	210 p., 811 il.	\$7.95
CMS Aid Handbook	432 p., 224 il.	\$8.95
ENRIS Outbook	240 p., 270 il.	\$6.95
Master HP AMP Applications Handbook	476 p., 320 il.	\$9.95
Microprocessors: From Calculators to Computers	196 p., 67 il.	\$5.95
Complete Hdbk. of Public Address Sound Systems	272 p.	\$7.95
Master Transistor Radios	64 p., 172 il.	\$2.50
Motorcycle Over Service & Repair	420 p., 216 il.	\$9.95
Solid-State Motor Controls	322 p., 162 il.	\$4.95
Master Handbook of Ham Radio Circuits	392 p., 301 il.	\$8.95
Towers International Transistor Selector	200 p., 179 il.	\$6.95
Ham Radio Incentive Licensing Guide	154 p., 70 il.	\$4.95
Programming Microprocessors	288 p., 162 il.	\$7.95
The "Calculator" Book—Build Super Calculators	322 p.	\$7.95
Master Transistor IC Substitution Handbook	518 p., 165 il.	\$7.95
Home-Brew HF/VHF Antenna Handbook	210 p., 143 il.	\$5.95
CB's Handy Manual of SSB	80 p., 42 il.	\$2.25
Beginner's Guide—Making Electronic Gadgets	140 p., 113 il.	\$4.95
Modern Digital Communications	348 p., 122 il.	\$6.95
Microcomputer Prog. Center Handbook	378 p., 219 il.	\$8.95
Illus. Bkct. Broadcast/CATV/Telecommunications	420 p.	\$8.95
Linear IC Applications Handbook	280 p., 183 il.	\$6.95
Build-In Book of Radiotelectronic Projects	238 p., 175 il.	\$5.95
How to Use AF & RF Signal Generators	230 p., 162 il.	\$5.95
Model Railroad Electronics	348 p., 218 il.	\$5.95
The ABC Book of Hi-Fi Audio Projects	182 p., 131 il.	\$4.95
Complete Hdbk. of Electrical/House Wiring	476 p., 197 il.	\$6.95
88 Practical Amp Circuits You Can Build	140 p., 120 il.	\$4.95
How to Build/Maintain Treasure Locators	140 p., 68 il.	\$3.95

SEND NO MONEY! We'll invoice you on 10-DAY FREE TRIAL. Ship back for refund or order. No return postage. No money refunded.

TAB BOOKS DEPT. RE-128 BLUE RIDGE SUMMIT PA 17214

CIRCLE 28 ON FREE INFORMATION CARD

You Can Count On DAVIS!



NEW CTR-2A

500 MHz & 1 GHz CONTROLS

NOW WITH

PERIOD MEASUREMENT (Optional) AND BUILT-IN PREAMP

- 8 Digit .3" LED Display
- High Stability TCXO Time Base
- Built-in VHF-UHF Prescaler & Preamp
- Period 1 us to 1 sec. (optional)
- TCXO Std. ± 2 ppm
- Input Diode Protected
- 12V-DC Operation (optional)
- Oven Crystal ± .5 ppm (optional)
- Selectable Gate Times .1 sec. & 1 sec.

500 MHz kit CTR-2A-500K	\$249.95
500 MHz assembled CTR-2A-500A	\$349.95
1 GHz kit CTR-2A-1000K	\$399.95
1 GHz assembled CTR-2A-1000A	\$499.95

OPTIONS:

(02) Oven Crystal	\$49.95
(03) .43" LED	10.00
(04) 12 V-DC	10.00
(05) 10 sec. Time Base	10.00
(06) Period Option	15.00

DAVIS

DAVIS ELECTRONICS
636 Sheridan Drive
Tonawanda, NY 14150
716/874-8848



books

MICROCOMPUTER HANDBOOK, by Charles J. Sippl, Petroselli/Charter, Div. Mason/Charter Publishers, Inc., 641 Lexington Ave., New York, NY 10022. 454 pp. 6 1/2 x 9 1/2 in. Hardcover \$19.95.

This book is designed to serve the needs of designers, students, hobbyists and all those who require a thorough understanding of low-cost microminiaturized computer systems. Systems engineers and developers who must integrate these computers into existing systems will also find this book a useful guide.

Early chapters deal with and contrast standard computers and minicomputers. Other chapters describe the various types of microcomputers and their capabilities, software, programs and many applications. All terminology is carefully defined, and photos and diagrams clarify the text.

THE DESIGN OF OPERATIONAL AMPLIFIER CIRCUITS, WITH EXPERIMENTS, by Howard M. Berlin. E&L Instruments, Inc., 61 First St., Derby, CT 06418. 266 pp. 6 x 9 in. Softcover \$6.50.

The beginning experimenter and hobbyist will find this latest in the Bugbook series useful in a home study program dealing with the design and operation of different types of op-amp circuits. Each chapter contains its own set of experiments on a wide spectrum of circuits, from linear amplifiers to single-supply units. Chapter 1 introduces the reader to the basics; other chapters deal with the fundamental circuits using bipolar and Norton-type op-amps; and Chapter 10 discusses the instrumentation amplifier used in augmenting low-level signals.

WORKSHOP IN SOLID STATE, Second Edition, by Harold E. Ennes. Howard W. Sams & Co., Inc., 4300 W. 62nd St., Indianapolis, IN 46268. 384 pp. 5 1/2 x 8 1/2 in. Softcover \$7.95.

The student and technician with previous training in electronics will find this book helpful in making the transition from vacuum-tube circuitry to solid-state devices. The material was originally developed to aid in training broadcast technicians, but the basic principles apply to other branches of electronics as well.

The text covers the fundamentals of solid-state devices, circuits for both linear and pulse applications, logic-circuit principles and testing and servicing information. Test questions follow most chapters, with answers in an appendix in the back of the book.

HOME-BREW HF/VHF ANTENNA HANDBOOK, by William Hood. TAB Books, Blue Ridge Summit, PA 17214. 210 pp. 5 x 8 1/2 in. Softcover, \$5.95; hardcover, \$8.95.

This how-to guide on building antennas contains complete down-to-earth instructions on designing, constructing, installing, selecting, buying and customizing any HF/VHF antenna, from a basic dipole to stacked-beam arrays. The first two chapters deal with essential antenna principles, formulas, systems and configurations. Also included are in-depth examinations of wave propagation, radiation characteristics, transmission lines, baluns, etc., plus instructions and schematics for constructing dummy antennas, SWR meters, impedance bridges, L- and Pi-networks, and many more. Contains four appendices and an index.

R-E

FREE SWITZ CATALOG

Audio—Computers Instruments Kits & Assembled

COMPUTER PRODUCTS CATALOGUE



Southwest Technical Products Corporation
219 W. RHAPSODY
SAN ANTONIO, TEXAS 78216

CIRCLE 57 ON FREE INFORMATION CARD

Try this exciting new hobby!

Build your own electronic concert organ. It's easy. No technical knowledge required. Just follow the clearly-pictured instructions of the famous Wersi do-it-yourself system. Choose from seven different models. Send \$2.00 (refundable) with coupon for colorful 104 page catalog.

WERSI



Wersi Electronics, Inc.
Dept. 42,
1720 Hempstead Road
Lancaster, PA 17601

Enclosed is \$2.00 for my copy of your 104 page catalog.

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE 29 ON FREE INFORMATION CARD

next month

JANUARY 1979

- Build An Audio Test Station
- How To Troubleshoot Communication Receivers
- Build An Arcade Quality Motorcycle Game
- All About Optical Fiberquides
- Simplifying The Wire-Wrap Jungle

PLUS

Lab Tested Hi-Fi Test Reports

Build A Compact 600 MHz Freq Counter

CET Test

Computer Corner

HOBBY COMPUTER POWER SUPPLIES

Continued from page 59

Keep it cool

While giant strides have been made in the miniaturization of electronic components, nobody has yet miniaturized the *joule* (i.e., watt-second). Heat causes many electrical component failures, and it is likely that series-pass transistors and regulators will fail if allowed to get too hot. Additionally, most such devices have a temperature coefficient that defines an output voltage change in percent-per-degree centigrade ($\%/^{\circ}\text{C}$).

At current levels up to about 5 amperes, ordinary heat-sinking and convection cooling will usually suffice, but at higher current levels it becomes increasingly necessary to use a blower or fan in addition to the heat sink.

In one configuration of my Z-80 system, I used a heat-sinked HEP S7000 in the circuit of Fig. 3 to provide 5 volts at 10 amperes. The heat sink was one of the large finned International Rectifier models sold in hobbyist outlets. This transistor got so hot after 20 minutes of operation at near full load that a first degree burn would reward anyone foolish enough to touch it! But a 50-cfm "whisper" fan reduced the temperature to the "barely hot" level in only a few minutes!

In short, it is good practice to always use forced-air cooling on power regulators and series-pass transistors operated at more than a few amperes of constant load current. Keeping the case temperature low will not only improve longevity, but will also prevent output voltage drift due to thermal changes. The rules for keeping a regulator and rectifier cool are:

1. Mount the IC regulator, series-pass element and rectifiers on heat sinks, not just on the chassis.
2. Use silicone/heat-transfer grease between all devices and their respective heat sinks.
3. Blow 40 to 105 cubic-feet-per-minute (cfm) of air across the heat-sink fins. Such fans or blowers can usually be obtained at low-cost surplus or somewhat higher cost at retail. The investment is well worth it—remember that bit about the silicon-to-carbon converter!

R-E

INTERNATIONAL FM-2400CH

FREQUENCY METER FOR TESTING MOBILE TRANSMITTERS AND RECEIVERS

• Portable • Solid State • Rechargeable Batteries

The FM-2400CH provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz.

The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency stability: $\pm 0.0005\%$ from $+50^{\circ}$ to $+104^{\circ}\text{F}$.

Frequency stability with built-in thermometer and temperature corrected charts: $\pm 0.0025\%$ from $+25^{\circ}$ to $+125^{\circ}$ (.000125% special 450 MHz crystals available).

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

FM-2400CH (meter only) Cat. No. 035320	\$595.00
RF crystals (with temperature correction)	24.90 ea.
RF crystals (less temperature correction)	18.90 ea.
IF crystals	catalog price

Write for catalog



INTERNATIONAL CRYSTAL MFG. CO., INC.
10 North Lee / Oklahoma City, Okla. 73102

CIRCLE 73 ON FREE INFORMATION CARD

SPEAKER CABLES

continued from page 93

in the opposite direction. Both conductor layers are wound at a 45-degree angle, constantly crisscrossing each other.

The *High Definition* cable manufactured by Audio-Source (see Fig. 7) is the least expensive, costing 80 cents-per-foot, with a characteristic 10-ohm impedance; having 10 pairs of braided wire; and connected in parallel to reduce DC resistance and with specially finished tips.

It is impossible to predict accurately how certain speaker/wire/amplifier com-

binations will perform. Some amplifiers cannot handle capacitances greater than 6000 pF and shut down. Some amplifiers cannot *handle too little capacitance*, and shut down or produce a metallic or ringing sound. Dr. Maier, president of the Disc Washer Group, distributors of *Smog Lifters*, says: "Very fine amplifiers with highly balanced output stages, with complementary power supplies will sustain up to one microfarad just like certain amps will play 'into' and sound good on electrostatic speakers. Amps, which do not like electrostatic speakers, and which sound terrible on them, tend to be candidates for super cable problems."

Some high-powered amplifiers have had problems with too small a capacitance—1500 and 15,000 pF. Engineers say this can be avoided by inserting an inductor in the output circuit.

The *Smog Lifter* cables are claimed to have a lower capacitance (480 pF) than other super cables. Dr. Maier believes "the capacitance of the *Smog Lifters* allows most amps to be used, but we are including a disclaimer of consequential damage with our words of caution for the protection of everybody."

The problem is somewhat similar to using penicillin or any other drug—not all people respond the same way. There is a dynamic equation between speaker wire and amplifier. So here's a word of caution for any potential user: Not all people will hear the difference between a No. 16 wire and a No. 22 wire; nor may they hear the difference between the super cables and the best of conventional cord. You may discover that upgrading your cable doesn't actually make a difference. In my tests, which were not highly controlled blind listening tests, I discovered there was a difference—a cleaner percussive sounds and a tighter bass.

If you're looking for better sound from your audio system, try the super cables (or even just heavier wire) on a money-back basis; you may be pleasantly surprised with the results. **R-F**

R-F

[illegible]

When in our area, Northeastern Massachusetts or Southern New Hampshire, visit our new showroom, loaded with many desirable items that never get in the catalog or ads, due to a limited quantity.

Please enclose
sufficient postage.
Fees included.

FREE
CATALOG


Send for new catalog 10-120 pages of computer & electronic bargains... the best in the world!

TELEPHONE
AREA 388-4705

ELECTRONICS
P.O. BOX 2, DEPT. 128
7 OAKLAND ST.,
AMESBURY, MASS.
01913

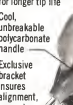9 reasons why the real pros prefer Endeco desoldering irons



- 
1. Operates at 120v, 40w. Idles at 20w for longer tip life
2. Flexible, burn resistant Neoprene cord set
3. Cool, unbreakable polycarbonate handle
4. Exclusive bracket insures alignment, prevents damage
5. Safety light in handle tells when it's on
6. Stainless steel construction
7. Temperature control. Low, high or off
8. Eight tip sizes. Comes with .063 I.D.
9. Converts to soldering iron with 1/4" shank type tip
- MODEL 510

Enterprise Development Corp.
5127 E. 65th St. • Indianapolis IN 46220
PHONE (317) 251-1231

CIRCLE 9 ON FREE INFORMATION CARD

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services) \$1.50 per word (no charge for zip code) . . . minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) 85¢ per word . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 5% discount for 6 issues, 10% for 12 issues within one year, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e., August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.

FOR SALE

FREE catalog (anglais). IC's, semi's. CORNET ELECTRONICS, 649A Notre Dame W., Montreal, Que., Canada, H3C-1H8. US inquiries.

RADIO & TV tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, Calif. 92105

BLITZ ZOINK ZATT: UNSCRAMBLE these fascinating police communications with our CODE-BREAKER and keep informed. Tunes all scramble frequencies, works with all scanners, and is factory built and guaranteed. \$34.95PP. UNSCRAMBLER KIT: Latest Technology, 2 1/2x2 1/4x1 1/4-inch, complete instructions, only \$19.95PP. Thousands of satisfied customers. Catalog 55¢. Order from CRYSTAL KITS, BOX 445, BENTONVILLE, ARK. 72712. CDD orders. 501-273-5340.



TUBES sale!!! Sylvania, G.E.—Brand-new receiving tubes, 70%-75% discount. Semiconductors—low, low prices. UJ, 18374 Oxnard St., Tarzana, CA 91356. Tel 213-996-4222

To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$1.50 per word (minimum 15 words) to:

Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003

ORDER FORM
PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$10.

() Plans/Kits () Business Opportunities () For Sale
() Education/Instruction () Wanted ()

Special Category: \$10

(PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.)

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

PRINTED CIRCUIT

Positive Acting Photo Resist; Carbide bits; Bubble etchers; Artwork; Epoxy Glass Boards.

Send stamp & address label for flyer
TRUMBULL
833 Balra Dr., El Cerrito, CA 94530

RECORDS-TAPES! Discounts to 73%; all labels; no purchase obligations; newsletter; discount returned certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB**, 650 Main St., Dept. 3-1278, New Rochelle, NY 10801

NEW, adjustable, three-output, regulated power supply, plus 900 parts worth over \$400.00 in complete cartrivision television recorder electronics assembly. Documentation included. Perfect for microprocessor and all electronic applications. \$16.95 plus \$4.50 S&H. Master Charge, VISA. Free brochure. **MADISON ELECTRONICS**, 369, Madison, AL 35758. Satisfaction guaranteed. 205-837-6658, Res.

Burglar • Fire • Smoke Alarm Catalog

* Billions of dollars lost annually due to lack of protective warning alarms.

FREE CATALOG Shows you how to protect your home, business and person. Wholesale prices. Do-it-yourself. Free engineering service.



Burdex Security Co.

Box 82802 RE-128 Lincoln, Ne. 68501

NAME brand test equipment. Up to 50% discount. Free catalog and price list. **SALEN ELECTRONICS**, P.O. Box 82, Skokie, IL 60076

LIGHT-triggered relay driver. 6VDC adjustable threshold. Completely assembled only \$3.00 302AT. Sonic switch turns on lamps, radio, tape, etc. Completely assembled, solid-state super buy only \$3.00 210AT. 3 transistor audio preamp for mike, phone, tape, etc. Hi-Q-input, 8-45 ohm output. 9VDC completely assembled, only \$4.00 AT032. **ABT SYSTEMS**, P.O.B. 173, Schererville, IN 46375

SPEAKER INFORMATION KIT

Get 70 pages of speaker facts, specs, construction tips plus info on our raw speakers, crossover and a line of 9 quality hi-fi speaker system kits. We'll send you our full-color catalog; plus **How to Hook Up Your System**, an exhaustive step-by-step treatise on hi-fi system installation; and our **Speaker Operating Manual**, check book of facts on how to get the most from any speaker system, for Free. Even if you don't buy from us we want you to have the facts. That's how we got to be the world's largest manufacturer of speaker kits.



Send to:
Speakerslab, Dept. RE-1
735 N. Northlake
Seattle, WA 98103

Test equipment catalog listing used Tektronix, HP and GR equipment at bargain prices. Price \$1.00 refundable with first order. **PTI**, Box 8699, White Bear Lake, MN 55110

CIRCUIT boards from camera-ready artwork. Quantity discounts. Free details. **CM CIRCUITS**, 22 Maple Avenue, Lackawanna, NY 14218

PICTURE TUBE MACHINE
We buy and sell NEW and USED CRT rebuilding machinery. COMPLETE TRAINING. Buy with CONFIDENCE from the ORIGINAL MFR.
For complete details send name, address, no to:
LAKESIDE INDUSTRIES
4071 N. Elston Avenue
Chicago, IL 60618
Phone: 312-543-6545

B & K test equipment. Free catalog. Free shipping. Dinosaur discounts. **SPACETRON-DM**, 948 Prospect, Elmhurst, IL 60126

FREE KIT Catalog

STOP! Take a minute & let us send our latest kit catalog. If you like, send us the name & address of a friend who may also be interested and we'll include to you our booklet "How to build electronic thermometer".

DAGE SCIENTIFIC INSTRUMENTS
BOX 1054R LIVERMORE, CA 94550

AMERICA'S LARGEST SUPPLIER

of ORIGINAL Japanese Semi-Conductors
for CB, TV and Stereo Repair

We carry only genuine replacement parts

TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9
2SA 102	.20	.27	.30	2SC 696	1.00	1.20	1.30	2SD 234	.60	.70	.80	TA 720SP	1.60	1.80	2.00
2SA 234	.45	.53	.59	2SC 710	.20	.27	.30	2SD 235	.60	.70	.80	TA 7310P	1.30	1.45	1.60
2SA 473	.45	.53	.59	2SC 711	.30	.37	.40	2SD 261	.35	.40	.45	TBA 8105H	1.90	2.10	2.40
2SA 484	1.50	1.75	1.95	2SC 730	3.00	3.20	3.40	2SD 287	2.50	2.70	2.90	TC 5080P	5.00	5.20	5.80
2SA 495	.30	.35	.40	2SC 732	.20	.27	.30	2SD 313	.60	.70	.80	TC 5081P	3.00	3.20	3.40
2SA 497	1.00	1.20	1.30	2SC 735	.20	.27	.30	2SD 315	.60	.70	.80	TC 5082P	3.40	3.55	3.90
2SA 509	.30	.35	.40	2SC 756	1.50	1.80	2.00	2SD 325	.60	.70	.80	UHC 002	4.20	4.40	4.90
2SA 561	.30	.35	.40	2SC 756A	1.50	1.80	2.00	2SD 427	1.80	2.00	2.25	UHC 004	4.20	4.40	4.90
2SA 562	.30	.35	.40	2SC 781	1.90	2.10	2.40	2SD 525	.90	1.10	1.20	UHC 005	4.20	4.40	4.90
2SA 564A	.20	.27	.30	2SC 784	.30	.35	.40	2SD 526	.60	.70	.80	UPC 20C	2.10	2.50	2.80
2SA 634	.40	.45	.50	2SC 799	2.00	2.20	2.50					UPC 563	1.90	2.10	2.40
2SA 643	.30	.40	.45	2SC 828	.20	.27	.30					UPC 575C2	1.30	1.45	1.60
2SA 673	.35	.40	.45	2SC 839	.30	.35	.40					UPC 576	1.90	2.10	2.40
2SA 678	.35	.40	.45	2SC 867	3.20	3.40	3.70					UPC 552HZ	.70	.80	.90
2SA 682	.80	.90	1.00	2SC 867A	3.20	3.40	3.70	2SK 198L	.45	.55	.60	UPC 1001	1.90	2.10	2.40
2SA 683	.30	.35	.40	2SC 897	2.00	2.20	2.50	2SK 23	.70	.80	.90	UPC 1008C	4.20	4.40	4.90
2SA 684	.35	.40	.45	2SC 930	.20	.27	.30	2SK 33	.60	.70	.80	UPC 1020H	1.90	2.10	2.40
2SA 695	.40	.45	.50	2SC 945	.20	.27	.30	2SK 55	.60	.70	.80	UPC 1025H	1.90	2.10	2.40
2SA 699A	.50	.64	.70	2SC 953	.50	.64	.70	2SK 22Y	1.40	1.60	1.80	UPC 1154	2.00	2.20	2.50
2SA 706	.85	1.00	1.10	2SC 959	1.10	1.20	1.30	2SK 39	.90	1.10	1.20	UPC 1155	2.00	2.20	2.50
2SA 719	.30	.35	.40	2SC 1000BL	.35	.40	.45	2SK 40	.90	1.10	1.20	UPC 1156	1.90	2.10	2.40
2SA 720	.30	.35	.40	2SC 1014	.50	.64	.70	2SK 41	1.30	1.45	1.60	UPC 1430S	3.20	3.40	3.90
2SA 733	.20	.27	.30	2SC 1018	.60	.70	.80	2SK 45	1.30	1.45	1.60	UPD 851	8.00	8.40	9.50
2SA 747	4.40	4.40	4.90	2SC 1030C	1.80	2.10	2.40	2SK 48	3.40	3.55	3.90	UPD 857	8.00	8.40	9.50
2SA 818	.70	.81	.90	2SC 1061	.70	.80	.90	2SK 49	1.30	1.45	1.60	PLL 01A	6.00	6.30	7.00
2SA 841	.20	.27	.30	2SC 1079	3.40	3.55	3.90					PLL 02A	5.00	5.30	5.90
				2SC 1096	.45	.55	.60					PLL 03A	7.60	8.00	8.80
				2SC 1098	.50	.64	.70								
				2SC 1111	2.10	2.50	2.80								
				2SC 1124	.80	.90	1.00								
				2SC 1172B	3.30	3.60	3.95	AN 214Q	1.30	1.70	1.90				
				2SC 1173	.50	.55	.60	AN 239	4.20	4.40	4.90				
				2SC 1226	.50	.55	.60	AN 247	1.50	2.70	3.00				
				2SC 1226A	.50	.55	.60	AN 274	2.50	1.75	1.95				
				2SC 1239	2.20	2.70	2.90	AN 313	3.00	3.20	3.40	IS 84	.45	.55	.60
				2SC 1306	1.30	1.45	1.60	AN 315	1.80	2.00	2.25	IS 332	.35	.40	.45
				2SC 1307	1.90	2.10	2.40	BA 511A	1.80	2.00	2.25	IS 953	.16	.18	.20
				2SC 1318	.35	.40	.45	BA 521	1.90	2.10	2.40	IS 1007	.35	.40	.45
				2SC 1363	.30	.35	.40	HA 1151	1.90	1.75	1.95	IS 1209	.35	.40	.45
				2SC 1384	.35	.40	.45	HA 1156	1.60	1.80	2.00	IS 1211	.35	.40	.45
				2SC 1419	.60	.70	.80	HA 1306W	2.00	2.20	2.50	IS 1555	.20	.22	.25
				2SC 1675	.20	.27	.30	HA 1322	2.50	2.70	3.00	IS 1588	.20	.22	.25
				2SC 1678	1.10	1.25	1.40	HA 1339	2.50	2.70	3.00	IS 1885	.16	.18	.20
				2SC 1728	.70	.80	.90	HA 1339A	2.50	2.70	3.00	IS 2076	.20	.22	.25
				2SC 1730	.45	.53	.59	HA 1366	2.50	2.70	2.90	IS 2093	.35	.40	.45
				2SC 1760	.70	.80	.90	HA 1366W	2.50	2.70	2.90	IS 2473	.16	.18	.20
				2SC 1816	1.50	1.75	1.95	LA 4031P	1.80	2.00	2.25	IN 34	.12	.13	.15
				2SC 1856	.50	.64	.70	LA 4032P	1.80	2.00	2.25	IN 60	.12	.13	.15
				2SC 1908	.30	.35	.40	LA 4400	1.90	2.10	2.40	100 1	.30	.35	.40
				2SC 1909	1.80	2.00	2.25	LA 4400Y	2.00	2.20	2.50	100 10	.45	.55	.60
				2SC 1945	4.50	5.00	5.60	LA 4420	2.00	2.20	2.50	V06B	.30	.35	.40
				2SC 1957	.60	.70	.80	M51513L	2.00	2.20	2.50				
				2SC 1970	2.10	2.50	2.80	STK 011	3.80	4.00	4.40				
				2SC 1978	5.40	6.00	6.60	STK 013	7.60	8.00	8.80	WZ 071	.20	.22	.25
				2SC 2028	.50	.64	.70	STK 015	4.20	4.40	4.90	WZ 090	.20	.22	.25
				2SC 2029	1.50	1.80	2.00	STK 435	4.50	5.00	5.60	WZ 120	.20	.22	.25
				2SC 2078	.50	.64	.70	TA 7045M	2.00	2.20	2.50	WZ 152	.20	.22	.25
				2SC 2091	.90	1.10	1.20	TA 7060P	.70	.80	.90				
				2SC 2092	1.80	2.00	2.25	TA 7061P	.90	1.10	1.20				
				2SC 2166	1.40	1.60	1.80	TA 7062P	1.10	1.25	1.40				
								TA 7068P	2.00	2.20	2.50				
								TA 7202P	2.50	2.70	2.90				
								TA 7203P	2.50	2.70	2.90				
								TA 7204P	2.00	2.20	2.50				

Minimum order \$5.00. Add \$1.00 postage and handling. Ask for our complete price list when ordering. Overseas buyers, Manufacturers, Distributors or Dealer orders welcome. All parts are guaranteed against factory defects for one year. C.O.D. orders are welcome. 48-hour delivery.

ORDER TOLL FREE

EAST
Nationwide 800-543-1607
Ohio 800-543-1630
Mon-Fri 10:00 to 7:00 - Saturday 10:00 to 5:00
P.O. Box 40325 • Cincinnati, Ohio 45240

WEST
Nationwide 800-543-1642
California (Call Collect) 213-533-1221
Mon-Fri 9:00 to 5:00 • Sat 9:00 to 3:00
P.O. Box 3375 • Torrance, California 90501

Telex: 21-4732


Fuji-Svea®



THE NEW HOBBY WORLD CATALOG

Your source for factory prime, professional quality equipment. Computers, add-on boards, IC's, sockets, resistors, supplies, tools, test equipment,

books, and more. Shop your buy list at Hobby World. You'll find what you want, and at a solid savings. For example, look at this month's specials:

THE NEW ELENCO 3 1/2 DIGIT SOLID STATE MULTIMETER

The ultimate in performance: measures resistance to .01 ohms, voltage to 100 micro-volts, current to one micro-amp. Assembled and tested, with 2-Year warranty. Lists at \$99.95, **HOBBY WORLD PRICE ONLY \$74.95!**

16K MEMORY ADD-ON FOR APPLE OR TRS-80

HOBBY WORLD PRICE IS ONLY \$98.00 (specify when ordering)

WAHL ISO-TIP CORDLESS SOLDERING IRON

Includes ni-cad batteries and wall plug transformer. Lists at \$19.95, **BUT HOBBY WORLD HAS IT FOR \$14.95!**

SEND ME A FREE CATALOG!

Name _____

Address _____

City _____

State _____

Hobby World
19355 Business Center Dr #6
Northridge CA 91324

TELEPHONE ORDERS
Inside Cal 213 886 9200
Outside Cal 800 423 5387

RE-DEC

CIRCLE 59 ON FREE INFORMATION CARD

New Tone Electronics

Quality components at fair prices

HIGH FIDELITY SPEAKERS

8-INCH COAXIAL

Combines a high quality 8" woofer and a tweeter into a pre-phased sound reproducer. Built-in cross-over network. Excellent choice for a low cost Hi-Fi system for autos, vans, or in your home. Frequency response is a smooth 80-15000 Hz. 8-ohm VC, 10 ohm ceramic ring magnet. 25W rating. **NT577 \$13.99 plus 40 cents postage**

10-INCH WOOFER

The speaker for your "big sound" system. Frequency response is 20-4000 Hz. 8-ohm aluminum VC; powerful 20 ohm ceramic ring magnet and a rubberized accordion-edge suspension for excellent compliance. Handles 50W max. Use with the NT576 for a super system. **NT576 \$17.99 plus 40 cents postage**

50W DOME TWEETER

Here is the super tweeter. A rugged 10 cm 14" dome tweeter which handles 50W max. Frequency response is 4000-20000 Hz. 8-ohm VC, 8-ohm ceramic magnet. Your system can have a brilliance you never imagined. **NT578 \$6.99**

Resistors Standard values, +5%, first quality. Packed 5 of one value.
1/4W 5 for \$1.25 1/2W 5 for \$1.30

Capacitor Special 3600 mF, 40Vdc Sprague "Powerlytic" \$1.89

Relay SPDT, 12Vdc: 5A contacts **NT565 \$1.79**

Sound Activated Switch Complete, ready to use. Built-in microphone's output triggers a Triac which acts as a switch. Measures only 1" x 3". Requires 3-8Vdc. **NT527 \$1.29**

And, the largest inventory of domestic and Japanese transistors and ICs in the United States.

ALL PARTS GUARANTEED
WRITE FOR FREE CATALOG

Minimum Order \$5. Add \$1.50 Postage and Handling.
Canada add \$2.00. N.J. Residents add 5% Sales Tax.



New Tone Electronics
PO BOX 1738
Bloomfield, N.J. 07003

CIRCLE 44 ON FREE INFORMATION CARD

STAMP collectors. Fine sets of no-gum unused Canadian postage stamps. More than \$2 face value only \$1 US funds plus SASE. Quantities limited. G. STECKLER, 24 Straw La., Hicksville, NY 11801

BREATHE BETTER AIR WITH AMAZING NEGATIVE ION GENERATOR KITS AND ASSEMBLED UNITS

Scientists have long known that negative ions can be inhaled to make the human body feel better. They are potent, atmospheric particles abundant in nature. Now, through the design of scientists, you can duplicate the design of your environment in the privacy and convenience of your own home or office.

Room/Potable Units
on Tables
Accessories

DELIVERS
WARRANTY

GOLDEN ENTERPRISES
P.O. Box 328
Glendale, Arizona 95211

(Please send \$1.00 for free catalog details)

PLANS & KITS

LINEAR AMPLIFIER: Ham only 2-30 MHz, 100 watt, solid-state. **FREQUENCY COUNTER:** 300 MHz, miniportable/mobile, memory VOX—**COMPRESSOR:** Splitter-free modulation booster. Construction plans \$3.00 each. All \$7.50! Many others, catalog with order. **PANAXIS PRODUCTIONS**, Box 130-F12, Paradise, CA 95969

AMAZING ELECTRONIC PRODUCTS AND PRODUCTS: Lasers Super Powered, Burring, Cutting, Rifle, Pistol, Pocket. Set in Dark—Shotgun Directional Mikes—Uncramblers—Giant Tails—Stunwand—TV Cloner—Energy Producing, Surveillance, Detection, Electrifying, Ultrasonic, CB, Auto and Mech. Devices, Handcuffs More—All New Plus INFO UNIT TO PARTS SERVICE. Catalog \$1. Information Unlimited, Dept. RS Box 716 Amherst, N.H. 03031.

SCANNER users—build many useful accessories. Free kit catalog. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520

CONSTRUCTION plans; over 100. From TV to telephone, from broadcasting to computers. Catalog air mailed \$1.00; includes year's subscription to Electronic Newsletter. **DON BRITTON ENTERPRISES**, PO Box G, Walikiki, HI 96815

AUTOMATICALLY records phone calls onto cassette recorder. Plans \$5.00. **CASCO**, Box 947, Roswell, GA 30077



Digital Auto Security System 3-Way Protection For Your Entire Car or Van

- Proximity Triggered Theft Protection - for valuables, CB or Ham equipment.
- Voltage Triggered Entry Protection - for doors and trunk.
- Mechanically Triggered Entry Protection - for under-hood parts.
- Activated by Personal 4-Digit Code.
- Uses Your Auto Horn As An Alarm, Or Add A Siren.

Forget about anything you may have heard about other anti-theft systems. The OCULAR 2nd, total security system, adds a new dimension to automobile security — **Proximity Detection**. Even if the would-be thief could enter your car without triggering the voltage sensing circuit (not likely) — just approaching the protected area will sound your alarm instantly. **He does not have to touch anything!** Attention is the one thing the "rip-off" artist doesn't want.

And, there's more protection. Raising the hood sounds the alarm. Any change in voltage (door or trunk light on, starting the car) sounds the alarm. If the cable connecting the units in the passenger compartment is cut, the OCULAR 2 turns itself on and sounds the alarm.

Your personal 4-digit code activates and deactivates the whole system. Just enter your code through the attractive push-button "Code Lok" keyboard when you leave your car and the system is activated. When you return, there's enough time to enter your code to deactivate the system before the alarm sounds.

Installation is easy and requires only simple hand tools. Complete with all hardware, instructions and your personal code. For 12-volt, negative-ground electrical systems only.

Sorry, but at this price, we must limit each order to only two systems per customer.

Was \$49.95, now **Ocular 2 \$19.95**

Radio Shack: No. 1 Parts Place

Low Prices and New Items Everyday!

Top-quality devices, fully functional, carefully inspected. Guaranteed to meet all specifications, both electrically and mechanically. All are made by well-known American manufacturers, and all have to pass manufacturer's quality control procedures. These are not rejects, not fallouts, not seconds. In fact, there are none better on the market. Always count on Radio Shack for the finest quality electronic parts!

Linear ICs

By National Semiconductor and Motorola — first quality

Type	Cat. No.	ONLY
301CN	276-017	49¢
324N	276-171	1.49
338N	276-172	1.49
384CN	276-173	99¢
555CN	276-172	79¢
556CN	276-172	1.39
568CN	276-172	1.69
567CN	276-172	1.99
723CN	276-174	89¢
741CN	276-007	49¢
741H	276-010	59¢
3909N	276-173	99¢
3909N	276-105	79¢
4558CN	276-102	99¢
75491	276-171	99¢
75492	276-170	1.29
7605	276-170	1.29
7812	276-171	1.29
7815	276-172	1.29

Hand-Held 6-Digit Frequency Counter

Counts from 100 Hz to 45 MHz
kHz and MHz Decimals **9995**

A high quality "pocket" counter with accuracy of 3ppm at 25°C or less then 30 Hz at 10 MHz. Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Lead-zero blanking. Just 3x4 1/2" with mini-rod antenna, leads, case, instructions. Requires 9V alkaline battery. 22-351 99.95



Wire Wrapping Accessories



IC Socket Wire Wrapping Tool. Strips and wires 30-gauge wire. 276-1576
14-Pin Wire Wrapping Socket. 276-1893 2.59
10-Pin Wire Wrapping Socket. 276-1894 2.19
DIP Header, 18 pins. 276-1895 1.29
10 Red 30-g. Kynar Wire. 276-501 1.99
50 White 30-g. Kynar Wire. 276-502 1.99
50 Blue 30-g. Kynar Wire. 276-503 1.99

Computer Chip



8-Bit Data Bus, 16-Bit Address Bus
6805A Microprocessor. 100% prime CPU handles up to 65K bytes memory. 276-2515 12.95

RAM Memory IC



2102 1K Static RAM. Low power version. 16-pin DIP. Buy 3 and receive 276-2501 2.49 Ea. or \$14.95

TTL and CMOS Logic ICs



Full-Spec Devices
Direct from Motorola and National Semiconductor

Type	Cat. No.	ONLY
7400	276-1601	35¢
7402	276-1611	39¢
7404	276-1602	35¢
7406	276-1621	49¢
7410	276-1607	39¢
7413	276-1615	79¢
7420	276-1609	39¢
7427	276-1623	49¢
7432	276-1604	49¢
7441	276-1604	99¢
7447	276-1605	99¢
7448	276-1616	99¢
7451	276-1625	39¢
7473	276-1603	49¢
7474	276-1616	49¢
7475	276-1606	79¢
7478	276-1613	59¢
7485	276-1608	1.19
7488	276-1627	49¢
7490	276-1608	79¢
7492	276-1619	89¢
74123	276-1617	99¢
74145	276-1620	1.19
74150	276-1629	1.39
74154	276-1634	1.29
74192	276-1631	1.19
74193	276-1630	1.19
74194	276-1632	1.19
74196	276-1633	1.29
4001	276-2401	49¢
4011	276-2411	49¢
4013	276-2413	89¢
4017	276-2417	1.49
4020	276-2420	1.49
4027	276-2427	99¢
4028	276-2449	89¢
4050	276-2450	99¢
4511	276-2447	1.49
4515	276-2460	1.49

NEW IC Breadboard Sockets



Modular boards snap together and feature standard 0.3" center. Accepts 22 through 30-gauge solid hookup wire.

- 51 50 connections in 2 bus strips of 40 tie points each with 47 rows of 5 connected tie points. 2 1/2x3 1/2". 276-174 9.95
- 51 270 connections in 2 bus strips of 40 tie points each with 23 rows of 5 connected tie points. 2 1/2x3 1/2". 276-175 8.95
- 51 Mini-Socket. 22 rows of 5 tie points each, plus 2 bus strips with 10 connections each. 2 1/2x1 1/2". 276-176 3.95

Low-Cost Power Transformers

Primaries Designed to Operate from 120VAC, 60 Hz
Solder Lugs for Easy Wiring or PC Board Mounting

Volts	Current	Cat. No.	Each	Volts	Current	Cat. No.	Each
6.3	1.2A	273-050	2.49	6.3 CT	3A	273-1510	3.99
0.3	300 mA	273-1384	1.99	12.6 CT	3A	273-1511	4.69
12	300 mA	273-1385	2.49	25.2 CT	2A	273-1512	4.99
24	300 mA	273-1386	2.49	12	5A	273-1513	8.95
24	1.2A	273-1480	2.99	18 CT	4A	273-1514	6.95
12.6 CT	1.2A	273-1505	2.89	24	2A	273-1515	4.99

* Ideal for 5V (using CT) or 12V solid-state regulators

NEW 3-Amp 4PDT Relay



Switch up to four different circuits!
Contacts rated 3 amps at 125VAC, 12VDC coil, 160 ohms resistance. Solder terminals. Just 1 1/2x1 1/2x1 1/2". 275-214 4.99

Radio Shack Reference Books

Digital Integrated Circuits. Complete specs. AC test circuits, waveforms. 62-1370 3.95
Voltage Regulator Handbook. 62-1371 2.95
Linear Integrated Circuits. Covers op-amps, voltage regulators, more. 62-1372 3.95
Linear Applications. Fully indexed and cross-referenced. 62-1373 2.95
Linear Applications, Vol. 2. The latest data sheets, applications. 62-1374 Reg. 2.95 Sale 1.95

CMOS Integrated Circuits. Covers 74C series, CD4000 with date specs. 62-1375 Reg. 3.95 Sale 2.29
Memory Data Book. 62-1376 Reg. 3.95 Sale 2.29
Intel® 8080/8085 Programming Manual. Uses Intel's assembly language. 62-1377 3.95
Intel Memory Design Handbook. Companion to Data Catalog, below. 62-1378 3.95
Intel Data Catalog. 508 pages of complete specs on most Intel standard devices. 62-1379 4.95

Paddle Switches



NEW

Reted 6 Amps at 125VAC

Mounts in 1/2" round hole — no need to pre-drill opening.
SPST Switch. 275-541 1.99
SPDT Red. 275-542 1.99
DPDT Black. 275-543 2.19

Lighted DPDT Pushbutton Switch



NEW


Push-on/push-off switch rated 4A at 12VDC. Button glows red in "on" position. Mounts in 1/2" hole. U.L. listed.
275-575 4.59

8-Rocker DIP Switch



Standard .100x.300" DIP
Designed for easy change of preset logic states in circuit. Fits 16-pin IC socket or mounts on PC board.
275-1301 1.99

Epoxy-Glass Plug-In PC Boards

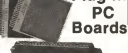

For 22-pin connectors. 4 1/2x4 1/2" grid. 3 styles available.
Standard. 276-155 4.49
Digital. 276-156 4.49
Op-Amp. 276-157 4.49
22-Pin Dual Connector. 276-1551 2.99

WHY WAIT FOR MAIL ORDER DELIVERY?
IN STOCK NOW AT OUR STORE NEAR YOU!

Prices may vary at individual stores and dealers

Radio Shack®
A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102
OVER 7000 LOCATIONS IN NINE COUNTRIES

DECEMBER 1978

CATCH-A-PULSE II LOGIC PROBE

10 Nsec SPEED AT 4 to 15V LEVELS

Compatible with TTL, TTL CMOS, MOS and Microprocessors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels; using LEDs to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, short jacket portable (protective tip cap and removable cord). Eliminates need for heavy test equipment. A definite savings in time and money for engineer and technician.

- 10 Nsec pulse response
- Open circuit detection
- Replaceable tip & cord
- High input impedance
- Pulse stretching
- Multi-family

SPECIAL PAK-II \$51.95

Includes a standard coiled cord, coiled cord with micro books, adaptor for using CATCH-A-PULSE on logic families whose power supply is 15V to 25V. Shipping add \$2.00 per probe.

AR ELECTRONICS
Box 19299, San Diego, CA 92119
(714) 447-1770

CIRCLE 6 ON FREE INFORMATION CARD

AMPLIFIER kits: Low TIM, Class A, BI-FET circuitry. Free 60-page manual. **MOONLIGHTER ELECTRONICS**, 117 Inverness, San Francisco, CA 94132

HOBBYST give your project the professional look. Printed circuit boards from your sketch or artwork. Affordable prices. Also fun kit projects. Rush free details. **DANOCINTHS**, Westland, MI 48185

3 DIGIT LED voltmeter kit \$19.60 complete. S.A.S.E. brings specifications, schematic. **ALPHA-SUPERKIT**, Box 21105-A, Woodhaven, NY 11421

EDUCATION & INSTRUCTION

GRANTHAM's FCC License Study Guide—377 pages, 1465 questions with answers/discussions—covering third, second, first radio telephone examinations. \$13.45 postpaid. **GSE PUBLICATIONS**, 2000 Stoner, Los Angeles, CA 90025

LOUDSPEAKER repair—complete how-to. 26 illustrations. \$2. **REPAIR**, 2860 Park St., Hono, HI 96817

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Mammory, study—Test-toppers for FCC and 2nd class Radio telephone licenses. Newly revised multiple choice questions and diagrams cover all areas tested in FCC exams, plus Self Study ability test. \$15.95 postpaid. **Wesley Book Company**

COMMAND PRODUCTIONS P.O. Box 26348 E
SUN FRANCISCO, CA 94126

TELEPHONE bugger? Don't be Watergated! Countermeasures brochure \$1.00. **NEVEGE LABORATORIES**, Box 547-RE, Pennsboro, WV 26415

UNIVERSITY degrees by mail Bachelors, Masters, Ph.D's . . . Free revealing details. **COUNSELING**, Box 317-RE12, Tustin, CA 92680

YOUR SCOPE OR COUNTER/TIMER CAN INSTANTLY MAKE PRECISE CAPACITANCE MEASUREMENTS WITH THE . . .

The C-PROBE is a precision test instrument using the latest CMOS IC technology to transform a capacitor's value into something your scope or counter/timer already understands . . . DIGITAL PULSES. The C-PROBE replaces the usual probe and causes a direct readout of a capacitor's value from 1 pF to over 10,000 Mfd. on the scope or C/T.


LEVER TERMINAL +
1" SPACED
TEST STRIP
FOR Cx
INPUT

BNC OUTPUT
TTL & CMOS COMPATIBLE
TEN TURN TRIMMERS
ASSURE EXACT pF & Mfd SETTINGS AND ZERO CONTROL FOR STRAY CAPACITANCE
ACTUAL COUNT/TIME IN SCOPE DISPLAYS W/IC PROBE

RANGES
1-10,000 pF
10-100,000 Mfd.
Resolution: 1 pF & 0.001 Mfd.
10 MHz or BETTER C/T
1 MHz or BETTER SCOPE

SHIPPED WITHIN 30 DAYS OF ORDER! FULLY CALIBRATED & WITH 100 HOUR, EASILY REPLACEABLE BATTERY
Box 3735
Thousand Oaks, CA 91320
805/496-7673
INTERNATIONAL INSTRUMENTATION, INC.
(order enclosure welcome)
C-PROBE @ \$40.00 SEACH
CALIBRATION CAPACITORS
pF RANGE \$1.14 Each
Mfd RANGE \$1.48 Each
SHIPPING & HANDLING
USA \$6.00 EUROPE \$4.50
C-4% SALES TAX

JUMBO LED READOUT ARRAY

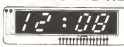

\$1.95 LIMITED STOCK

By Bowmar. .5 in. character common cathode. Designed for use with multiplexed clock chips 4 digits in 1 pack!

COMPUTER PARTS

Z-80	—	\$19.95
Z-80A	—	\$24.95
8080A	—	\$6.95
8212	—	\$2.25

16K DYNAMIC RAM CHIP

16K X 1 Bits 16 Pin Package. Same as Motek 4116-4 250 NS access 410 NS cycle time. Our best price yet for this state of the art RAM 32K and 64K RAM boards using this chip are readily available! These are new, fully guaranteed devices by a major mfg.

\$14.95 each

8 FOR \$89.95

NATIONAL SEMICONDUCTOR JUMBO CLOCK MODULE



ASSEMBLED NOT A KIT!

ZULU VERSION
We have a limited number of the 24 HR Real time version of this module in stock
#MA1008D — \$9.95

\$6.95

2 FOR \$13
(AC XFMR \$1.95)

PERFECT FOR USE WITH A TIMEBASE.

FEATURES:
• FOUR JUMBO 1" HIGH LED DISPLAYS
• 24 HR REAL TIME FORMAT
• 24 HR ALARM SIGNAL OUTPUT
• 20 OR 60 Hz OPERATION
• LED BRIGHTNESS CONTROL
• POWER FAILURE INDICATOR
• SLEEP & SNOOZE TIMERS
• DIRECT LED DRIVE (LOW RFI)
• COMES WITH FULL DATA
COMPARE AT UP TO TWICE OUR PRICE!
MANUFACTURER'S CLOSEOUT!

MA1008A BRAND NEW

EXPERIMENTER'S CRYSTAL



262 144KHz. This frequency is 2 to the 18th power. Easily divided down into any power of 2, and even to 1Hz. New by CTS-Knight. A \$5 value!

\$1.25 each

SALE!

1N4148 DIODES
High speed switching diodes. Silicon. Same as 1N914. Brand New. Full Leads. Prime!
100 For \$2 1000 For \$17.50

FAIRCHILD JUMBO READOUTS

.5 inch Char High Efficiency! FND-303-Common Cathode FND-310-Common Anode
YOUR CHOICE \$9.95 10 FOR \$5.75

DISC CAPACITORS

1 MFD 16V. P.C. leads. Most popular value! By Sprague.
20 for \$1.00

Full Wave Bridge

4 Amp 200 PIV
69¢ea. 10/5.75

COMPUTER CAPACITOR

By GE. 36 000 MFD 15WVDC
Small Size: 4 1/2 x 1 1/2 inches.
SUPER DEAL! \$2.95 Each
3 FOR \$8

MALLORY POWER SUPPLY CAPACITOR

1500 MFD 16 WVDC
3/\$1.00 10/\$2.95
FACTORY FRESH! SMALL SIZE

RECTIFIER SALE!

1N4006 Prime
New by ITT.
1 AMP. 800 PIV.
15 FOR \$1

FET SALE!

2N4304 Brand New N Channel Junction Fet BVGDD-303 IDSS=15 MA Typ. 1500 uMHOS TO-18 Plastic Case Mfg by Tele. Dyn.
6 FOR \$1

Motorola PNP Power

2N4905 TO-3 case 90W VCE=60. HFE=100 max at 2.5A Good mate for the 2N3055 PRIME!
75¢ ea. 4/\$2.50

ACA MICRO-POWER OP AMP.

ACA307ET. Metal Can. Most OPAMPs require +15V to operate. But the ACA307E is designed to operate from . . . 7.5 V to +60V perfect for battery use. Standby power as low as 100 nW. High Gain. 90 dB typical Open Loop Gain. Requires only one capacitor for compensation. See ACA Linear Data Book for more details. Similar to National LM12. Originally cost about \$2 each.
75¢ EACH 3 FOR \$2

Digital Research Corporation

(OF TEXAS)
P.O. BOX 401247B GARLAND, TEXAS 75040 • (214) 271-2461

CIRCLE 54 ON FREE INFORMATION CARD



LYTIC SPECTACULAR!

PRICES SLAMMED! THIS AD ONLY! Can type lYTics in all the popular sizes: 1/2", single, double, & triple section, up to 100 uS/mr. Fresh, small size, pop uS/mr.



5 or 10Mhz,
TTL, MOS,
or CMOS
compatible!

Specify frequency:

STOCK NO.	SECTION 1	SECTION 2	SECTION 3	E.A.
C-3236	600/360v	--PHOTOFASH--	--	.59
C-1760	2000/24v	--	--	.59
C-2175	2500/30v	--	--	.59
C-2260	6000/50v	COMPUTER GRADE	2.49	.59
C-1220	20/200v	20/200v	--	.25
C-2316	1500/70v	1500/70v	--	.89
C-2300	2500/70v	2000/25v	--	.79
C-2400	8/250v	8/250v	50/250v	.25
C-2305	1000/75v	1500/25v	1000/25v	.79
C-2333	2000/75v	2000/25v	1000/25v	.89
C-3700	2500/20v	2000/25v	2000/25v	.89

PRECISION OSCILLATOR

2.0002" ± 10 to +80°C
Precision hermetic steel
5 to 12V Operation
Choice of 5 or 10 Mhz
Frequency Isolator
Use with TTL, CMOS
\$1.95
OR WRITE FOR PRODUCTION QUOTES.
Add \$3 for assembled & tested unit

BUSINESS OPPORTUNITIES

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: BUSINESS-92-R, Brighton 11th, Brooklyn, NY 11235

HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! Postcard will do. Bara-RE-L, Box 248, Walnut Creek, CA 94597.

CABLE FM station. No experience required, excellent spare-time income, others operate for you. Details free. BROADCASTING, Box 130-F12, Paradise, CA 95969

MECHANICALLY INCLINED INDIVIDUALS—WANTED—

Assemble electronic devices in your home. Get started in spare time. Experience, Knowledge or Investment Not Necessary. Expect big profits: \$300 - \$600/WK. Possible. Write for free literature telling how.

ELECTRONIC DEVELOPMENT LAB
Box 1535R, Pinellas Park, FL 33565

GOVERNMENT SURPLUS

JEEPS—\$59.30!—Cars—\$33.50!—45,000 items! Government surplus—most comprehensive directory available tells how, where to buy—your area—\$2.00—moneyback guarantee—GOVERNMENT INFORMATION SERVICES, Department VA—12, Box 99249, San Francisco, CA 94109

SAVE!

AXIAL LYTICS at the lowest prices anywhere! Small size, long leads, fresh stock. Stock up while they last!

STOCK NO.	NFO	DOV	E.A.
C-1405	450	15	.25
C-1450	450	25	.27
C-1435	500	30	.29
C-1445	500	60	.39
C-1460	1000	15	.39
C-2314	1000	50	.59
C-1500	1500	30	.69
C-1040	1600	10	.39
C-2114	2000	20	.49
C-3200	3200	20	.59

RHYTHM GENERATOR ROM IC

\$1.95 PRE-PROGRAMMED MEMORY HAS HEAVY RHYTHM PATTERNS STORED THAT ARE "WALKED OUT" WITH A CLOCKER. CHANCE PATTERNS BY CHANGING ADDRESS. 24 PIN DIP SUPPLIED TO PLAY MATH. 6-4-30A

STOCK NO.	NFO	DOV	E.A.
C-1405	450	15	.25
C-1450	450	25	.27
C-1435	500	30	.29
C-1445	500	60	.39
C-1460	1000	15	.39
C-2314	1000	50	.59
C-1500	1500	30	.69
C-1040	1600	10	.39
C-2114	2000	20	.49
C-3200	3200	20	.59

TTL, CMOS, or MOS outputs.

Kit! K-4000

STOCK NO.	NFO	DOV	E.A.
C-1405	450	15	.25
C-1450	450	25	.27
C-1435	500	30	.29
C-1445	500	60	.39
C-1460	1000	15	.39
C-2314	1000	50	.59
C-1500	1500	30	.69
C-1040	1600	10	.39
C-2114	2000	20	.49
C-3200	3200	20	.59

Multi-Frequency Oscillator

2.0001" ± 10 to +30°C
8 independent outputs:
500KHz, 2MHz, 1MHz,
600KHz, 250KHz, etc.
Use any or all!
\$1.95 5 to 12v operation
Assembled - Add \$3

TRIACS & SCR's 6AMP 200V

YOUR CHOICE \$59.95/10/5

T0-220 "POWER TAB" CASE, HIGH GATE SENSITIVITY. FAMOS, FURS, LOSS IS YOUR GAIN
T-2006 6A 200V TRIAC .59
T-2006 6A 200V SCR .59

8038 SUPER-FUNCTION GENERATOR

\$3.95 32 PAGE DATA SHEET \$3.00

JFET INPUT 741

59¢ PIN-FOR-PIN WITH A 741 OP AMP, BUT WITH AN INPUT Z OF 5 x 10¹⁰ OHMS! TYPE LF 13743 BY NATIONAL.

DIAMONDBACK ELECTRONICS COMPANY

PO BOX 1184 SPRING VALLEY, IL 61356
FREE CATALOG... ALL REORDERABLES 100% GUARANTEED SHIPMENT OR REFUND. NO REORDERABLES AND NO BULK TAX PLEASE include sufficient postage
PHONE ORDERS 815/664-5151

CIRCLE 61 ON FREE INFORMATION CARD



NEW-TONE ELECTRONICS

INTERNATIONAL

Specializing in Japanese Semiconductors, with the LARGEST INVENTORY and LOWEST PRICES ANYWHERE

And YOU CAN ORDER TOLL FREE 800-631-1250

Check the prices in this partial list Dealers - send for our complete volume (discount price list)

INTEGRATED CIRCUITS				INTEGRATED CIRCUITS				TRANSISTORS				INTEGRATED CIRCUITS				INTEGRATED CIRCUITS				TRANSISTORS				TRANSISTORS			
AN115	2.25	MS1202	1.55	UCP374	1.20	2SC1429	4.49	IN7414	7.75	2SC1429	4.49	IN7414	7.75	2SC1006	6.40	25A175	38	2SC1006	6.40	25A175	38	2SC1006	6.40	25A175	38		
AN218	4.65	MS3216P	1.80	UCP383C	1.30	2SC1452	4.49	AN217	1.70	UCP1005	5.50	2SC1005	5.50	2SC1005	5.50	2SC1005	5.50	2SC1005	5.50	2SC1005	5.50	2SC1005	5.50	2SC1005	5.50		
AN272	7.90	MS3273P	1.60	UCP1028	1.60	2SC1474	9.65	AN239	6.50	UCP1006	6.40	2SC1006	6.40	2SC1006	6.40	2SC1006	6.40	2SC1006	6.40	2SC1006	6.40	2SC1006	6.40	2SC1006	6.40		
AN313	4.65	MS4873P	2.90	UCP1031H	2.98	2SC1548	7.99	AN241	2.10	UCP255	3.30	2SC1025	3.30	2SC1025	3.30	2SC1025	3.30	2SC1025	3.30	2SC1025	3.30	2SC1025	3.30	2SC1025	3.30		
AN321	2.25	MS3710	7.95	UCP1032H	1.35	2SC1583	6.60	AN247	4.10	UCP558H	1.80	2SC485	1.80	2SC485	1.80	2SC485	1.80	2SC485	1.80	2SC485	1.80	2SC485	1.80	2SC485	1.80		
AN376	3.30	MS8710	7.70			2SC1622	4.49	AN251	2.80	UCP568H	3.65	2SC490	3.65	2SC490	3.65	2SC490	3.65	2SC490	3.65	2SC490	3.65	2SC490	3.65	2SC490	3.65		
AN382	2.70	MS1005	1.60			2SC1681	3.90	BA211	2.75	UCP5752C	2.25	2SC495	2.25	2SC495	2.25	2SC495	2.25	2SC495	2.25	2SC495	2.25	2SC495	2.25	2SC495	2.25		
AN386	4.50	MS1007	1.60			2SC1682	3.90	CI1016	6.20	UCP5812C	1.60	2SC502	1.60	2SC502	1.60	2SC502	1.60	2SC502	1.60	2SC502	1.60	2SC502	1.60	2SC502	1.60		
AN388	4.50	MS1017	14.95			2SC1742	3.90	HA1306H	3.75	UCP1012H	3.40	2SC502	3.40	2SC502	3.40	2SC502	3.40	2SC502	3.40	2SC502	3.40	2SC502	3.40	2SC502	3.40		
BA401	1.50	SG256A	4.50			2SC1761	1.58	HA1335A	3.50	UCP1008C	5.75	2SC1008C	5.75	2SC1008C	5.75	2SC1008C	5.75	2SC1008C	5.75	2SC1008C	5.75	2SC1008C	5.75	2SC1008C	5.75		
BA402	1.50	SG269	3.40			2SC1775	5.45	LA1386	3.60	UCP1030H	3.30	2SC1030H	3.30	2SC1030H	3.30	2SC1030H	3.30	2SC1030H	3.30	2SC1030H	3.30	2SC1030H	3.30	2SC1030H	3.30		
BA405	6.30	SG269-3	3.40			2SC1778	4.45	LA1386	3.60	UCP1030H	3.30	2SC1030H	3.30	2SC1030H	3.30	2SC1030H	3.30	2SC1030H	3.30	2SC1030H	3.30	2SC1030H	3.30	2SC1030H	3.30		
BA412	2.40	SG253	17.50			2SC1779	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA131Q	2.34	SI0110	6.90	25A772	89	2SC1811	1.29	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA132	2.10	SI0120	13.85	25A786	39	2SC1844	54	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA137B	4.45	SI0120	18.00	25A788	1.54	2SC1845	7.95	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA138W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85	2SC1055H	2.85		
BA139W	3.30	SI0150	27.00	25A788	1.05	2SC1906	4.45	LA405P	2.70	UCP1055H</																	

COMPUTER INTERFACES & PERIPHERALS

For free catalog including parts lists and schematics, send a self-addressed stamped envelope.

APPLE II SERIAL I/O
INTERFACE *

Part no. 2
Baud rate is continuously adjustable from 0 to 30,000 • Plugs into any peripheral connector • Low current drain. RS-232 input and output • On board switch selectable 5 to 8 data bits, 1 or 2 stop bits, and parity or no parity either odd or even • Jumper selectable address • SOFTWARE • Input and Output routine from monitor or BASIC to teletype or other serial printer.
• Program for using an Apple II for a video or an intelligent terminal. Also can output in correspondence code to interface with some selectrics. Board only — \$15.00; with parts — \$42.00; assembled and tested — \$62.00




T.V. TYPEWRITER

Part no. 106
• Stand alone TVT
• 32 char/line, 16 lines, modifications for 64 char/line included • Parallel ASCII (TTL) input
• Video output • 1K on board memory • Output for computer controlled cursor • Auto scroll • Non-destructive cursor • Cursor inputs: up, down, left, right, home, EOL, EOS • Scroll up, down • Requires +5 volts at 1.5 amps, and -12 volts at 30 mA • All 7400, TTL chips • Cris. gen. 2513 • Upper case only • Board only \$39.00; with parts \$145.00

8K STATIC
RAM

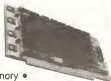Part no. 300
• 8K Altair bus memory • Uses 2102 Static memory chips • Memory protect • Gold contacts • Wait states • On board regulator • S-100 bus compatible • Vector input option • TRI state buffered • Board only \$22.50; with parts \$160.00



RF MODULATOR *

Part no. 107
• Converts video to AM modulated RF. Channels 2 or 3. So powerful almost no tuning is required. On board regulated power supply makes this extremely stable. Rated very highly in Doctor Dobbs' Journal. Recommended by Apple. • Power required is 12 volts AC C.T., or +5 volt DC • Board \$76.00; with parts \$135.00




MODEM *

Part no. 109
• Type 103 • Full or half duplex • Works up to 300 baud • Originate or Answer • No coils, only low cost components • TTL input and output-serial • Connect 8 ohm speaker and crystal vnc. directly to board • Uses XF, FSK demodulator • Requires +5 volts • Board \$7.60; with parts \$27.50



TIDMA *

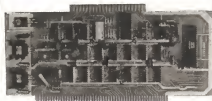

Part no. 112
• Tape Interface Direct Memory Access • Record and play programs without bootstrap loader (no prom) has FSK encoder/decoder for direct connections to low cost recorder at 1200 baud rate, and direct connections for inputs and outputs to a digital recorder at any baud rate. • S-100 bus compatible • Board only \$35.00, with parts \$110.00

DC POWER SUPPLY *

Part no. 6085
• Board supplies a regulated +5 volts at 3 amps, -12, -12, and -5 volts at 1 amp • Power required is 8 volts AC at 3 amps, and 24 volts AC C.T. at 1.5 amps • Board only \$12.50; with parts excluding transformers \$42.50



RS 232/TTY *

Part no. 600
• Converts RS-232 to 20mA current loop, and 20mA current loop to RS-232 • Two separate circuits • Requires +12 and -12 volts • Board only \$4.50, with parts \$7.00



TAPE INTERFACE *

Part no. 111
• Play and record Kansas City Standard tapes • Converts a low cost tape recorder to a digital recorder • Works up to 1200 baud • Digital in and out are TTL-serial • Output of board connects to mic. in of recorder • Earphone of recorder connects to input on board • No coils • Requires +5 volts, low power drain • Board \$7.60; with parts \$27.50

UART & BAUD RATE
GENERATOR *

Part no. 101
• Converts serial to parallel and parallel to serial • Low cost on board baud rate generator • Baud rates: 110, 150, 300, 600, 1200, and 2400 • Low power drain +5 volts and -12 volts required • TTL compatible • All characters contain a start bit, 5 to 8 data bits, 1 or 2 stop bits, and either odd or even parity • All connections go to a 44 pin gold plated edge connector • Board only \$12.00; with parts \$35.00 with connector add \$3.00



RS 232/TTL *

Part no. 232
• Converts RS-232, and converts RS-232 to TTL • Two separate circuits • Requires -12 and +12 volts • All connections go to a 10 pin gold plated edge connector • Board only \$4.50; with parts \$7.00 with connector add \$2.00



ELECTRONIC SYSTEMS

Dept. RE-9 P.O. Box 21638, San Jose, CA. USA 95151

To Order:

Mention part number and description. For parts kits add "A" to part number. In USA, shipping paid for orders accompanied by check, money order, or Master Charge, BankAmericard, or VISA number, expiration date and signature. Shipping charges added to C.O.D. orders. California residents add 6.5% for tax. Outside USA add 10% for air mail postage, no C.O.D.'s. Checks and money orders must be payable in US dollars. Parts kits include sockets for all J/Cs, components, and circuit board. Documentation is included with all products. All items are in stock, and will be shipped the day order is received via first class mail. Prices are in US dollars. No open accounts. To eliminate tam in Canada boxes are marked "Computer Parts". Dealer inquiries invited. 24 Hour Order Line: (408) 226-4064



* Circuits designed by John Bell

FIRST QUALITY CARBON RESISTOR KITS 1/4W

Each kit contains all the EIA designated 10% values from 2.2 ohms to 8.2 megohms. Your cost: Only \$5.02 per resistor.



KIT A
1,000 Pcs. 19⁹⁵ ppd.
Includes FREE
9-drawer box
(\$5.00 value)



KIT B
500 Pcs. 9⁹⁵ ppd.
Includes FREE
compartmentalized
box (\$2.00 value)



KIT C
250 Pcs. 4⁹⁵ ppd.
In Poly Bag

MANY OTHER KITS

Aluminum Electrolytic,
Tantalum and Ceramic
Capacitor Kits. Semicon-
ductor Kits, too. Lamps also.

We have **over 2,000**
quality Receiving Tubes.
Many hard-to-get types.
All at 75% off list.

ORIGINAL JAPANESE SEMICONDUCTORS

Full range available to
fill just about any
requirement.

Call (516) 752-0060
or send for
complete
catalog

TO ORDER:

Send check or Money Order—
N.Y. residents add appropriate tax.

STEVEN PRODUCTS

P.O. BOX 698, MELVILLE, N.Y. 11746

MULTI-TESTER

IT TESTS
TRANSISTORS AND LED's
AS WELL!!

YX-360TR

TRANSISTOR TESTER
320 OHMS/VOLT

SPECIFICATIONS

DCV 0.0 1.0 5.0 10 50 250 1000 (20uV)
V_I 1.2V, 25uV (w/10V probe)
DCA 0.50uA 0.2 2.0ma 0.0 25A 100mV
A 250mV ±2%
ACV 0.10 10 250 1000 (RM/V) ±4%
F₁ 20Hz to 20KHz
F₂ 20Hz to 20KHz
F₃ 10 Hz to 100 Hz (max 20Hz)
Batt 1.5V ±2 & 9V ±1
dB -10 to +62
IC80 0 150uA 0 15 150mA ±5%
HFE 0-1000 ±2% (w/connector)
150-150-57 420g



\$28.50

THE MOST POPULAR MM5314 CLOCK KIT

Features:

- * 12/24 Hours Display
- * 50/60 Hz Input
- * 6 Digits Bright Orange Readouts

Kit includes plastic case, MM 5314 I.C. One set transistor drivers, P.C. Board, gas discharge displays, all other electronic parts and transformer. Catalog no. DC-8SP

**SPECIAL PRICE,
\$16.95 PER KIT**



9 STEPS LED LEVEL INDICATOR KIT



for most stereo amplifiers

This new project works as a pair of VU meter to indicate the output level of your amplifier from -20dB to +3dB. Kit includes all LED, transistors, electronic components, P.C. Board and Instructions.

Easy to build and fun to see.

ONLY \$12.50 EA.

60W + 60W

STEREO




AMPLIFIER

COMPLETED UNIT—NOT A KIT!

OCL pre amp, & power stereo amp, with bass, middle, treble 3-way tone control. Fully assembled and tested, ready to work. Total harmonic distortion less than 0.5% at full power. Output maximum is 60 watts per channel at 8Ω. Power supply is 24 - 36V AC or DC. Complete unit

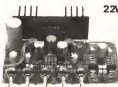only **\$49.50 ea.**
Power transformer **\$8.50 ea.**



POWER TRANSFORMER \$8.50 EACH

22W + 22W STEREO HYBRID AMPLIFIER KIT

It Works in 12V D.C. As Well! Kit includes 1 PC SANYO STK-024 stereo power amp. IC LM1458 as pre amp, all other electronic parts, PC Board, all control pots and special heat sink for hybrid. Power transformer not included. It produces ultra hi-fi output up to 44 watts (22 watts per channel) yet gives out less than 0.1% total harmonic distortion between 100Mhz and 10KHz.

\$32.50 PER KIT

SANYO HYBRID

Audio power amplifiers I.C.
Max. hi-fi output power, minimum ext. components needed.



15 Watts	STK-28	\$ 9.50
23 Watts	STK-064	\$13.50
30 Watts	STK-066	\$17.50
50 Watts	STK-050	\$26.50
10W + 10W (stereo)	STK-040	\$14.50
15W + 15W (stereo)	STK-041	\$25.50
20W + 20W (stereo)	STK-043	\$31.50

*data sheet comes with purchase

COMPUTER GRADE CAPACITORS



All capacitors are Brand New
U.S. made in standard size

9000MFD	50V	\$3.25 EA.
11000MFD	35V	\$3.20 EA.
14500MFD	40V	\$3.40 EA.
23000MFD	20V	\$3.00 EA.
58000MFD	20V	\$3.20 EA.
100,000MFD	6V	\$2.50 EA.

ULTRA-SONIC REMOTE CONTROL SWITCH KIT



Kit includes the transmitter, the receiver, ultra sonic transducers, P.L.L. I.C., all other electronic parts and P.C. Boards, ideal for control TV, light, fan or garage door. Case not included.

\$18.50 PER KIT

DIP SWITCHES



(On-Off Contacts)	
4 positions	\$1.50
5 positions	\$1.60
6 positions	\$1.70
7 positions	\$1.70
8 positions	\$1.80
10 positions	\$2.00

ELECTRONIC WHEEL OF FORTUNE KIT
With 10 numbers split into black and white on dial. The LED turns when you hit the play switch, then it slows down and stops on one number. It sounds like a motor inside, but there is none. Lots of fun and easy to build. Kit comes with nice looking case, all electronic parts, P.C. Board and LEDs. Battery not included.



\$12.50

TRS-80 MEMORY EXPANSION: \$159!

Our Conversion Kit contains all parts (and detailed instructions) necessary to upgrade a TRS-80 memory from 4K to 16K, or populate the Memory Expansion Module. Also works with APPLes. Only \$159 (kit \$450)... and we back up our parts with a 1 year warranty.

MA1003 CLOCK MODULE: \$16.50



Add 3 time-setting switches, 12V DC, and you're up and running. Crystal-controlled timebase makes this unit ideal for car, van, boat, other mobile applications. Large (0.3") blue-green fluorescent readouts are visible under conditions where LEDs would wash out. Includes special options for car applications (for example, turning on headlights dims display slightly for night viewing). Whether you need a clock for yourself or want to present someone with a fine gift, this is an excellent choice. With applications data. 31548.

12V 8A POWER SUPPLY \$44.50



Handles 12A with 50% duty cycle. Ideal for powering mobile equipment (CB rigs, portable TVs, transceivers, etc.) in the home, can also power punches of floppy disc drives. Crowbar overvoltage protection, foldback current limiting, adjustable output 11-14V, custom heavy-duty transformer, RF suppression, and easy assembly (all parts except xfrm'r/liter caps/diodes mount on circuit board). Does not include case. With full assembly instructions.

play with wire? request our flyer!

Our flyer is full of parts, music kits, computer kits, enclosures, specialty tools, capacitors, resistors... 40 pages of bargains in all. It's free: send us your name and address, we'll take care of the rest.

TERMS: Cal res add tax. Allow 5% shipping, (more for power supply), excess refunded. COD OK with street address for UPS delivery. VISA/Mastercharge® call 24 hr. order desk at (416) 562-0636. Thank you for your business.

GODBOUT
BILL GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

CIRCLE 49 ON FREE INFORMATION CARD



GREAT IDEAS FROM WEST SIDE ELECTRONICS

17 Digit, 10 Function Digital Clock Kit
The Ultimate Electronic Timepiece. 17 digits continuously read out the time, date, alarm setting, and timer. 12/24 HR, AC/DC, crystal timebase, 3 mode timer, status LEDs, and more. Now with DIGISST™ thumbwheel preset option (see below). Featured in Radio-Electronics (Aug/Sep 1977).
MTT-C kit, less case **\$129.95**

Pink Noise Generator Kit **\$13.95**
NOW IMPROVED!! With 5% tolerance components. Allows proper set-up of graphic equalizer in a stereo system to achieve acoustically flat response. Uses latest MOS IC. See Jan '78 Radio Electronics.
PNC-2C Partial kit **\$13.95**
PNC-2K Complete kit with case **\$19.95**
PNC-2W Assembled and tested **\$27.95**

WRITE FOR DETAILS
DIGISST™ Thumbwheel preset for MT1. Simply dial in alarm setting, timer, etc. and DIGISST™ does the rest. Also adds second ALARM feature. Will work with other 7001 based clocks.
APPLE II OWNERS: Real Time Clock plugs directly into any I/O slot. Crystal oscillator and AC supply (with battery backup) keeps clock running at all times.

SPECIAL
16K MEMORY EXPANSION KIT **\$130.00**
Includes 8 16Kx116 RAMs and instructions for Apple and TRS-80. Upgrade NOW at this LOW PRICE.

WEST SIDE ELECTRONICS
P.O. Box 636, Chatsworth, CA 91311
We pay all shipping in Continental U.S.A.
Others add 10%, California residents add 6% tax.

CIRCLE 89 ON FREE INFORMATION CARD

Everything you ever want to know about Personal Computers . . .

\$100

Postage Paid in U.S.



Here it is—everything you need to know about the state of the art, just as it appeared in the big, colorful special section of the June, 1978 RADIO-ELECTRONICS—"Your Own Computer."

This complete, colorful, 32-page reprint of that first-in-the-field special feature tells you everything you want to know, including: An Introduction to Personal Computers—what they can do and how to select your own; What Makes a Computer System—peripheral devices and accessories; The Different Ways You Can Talk to Your Computer—programming languages and how to use them; a special edition of Computer Corner, and, A Roundup of the Equipment, the most complete Who-Makes-It Computer Manufacturer Listing you can find!

We've reprinted this giant special section of RADIO-ELECTRONICS for your convenience. Every serious experimenter and technician will want this vital information at home and in the office, lab or workshop, where you can refer to it when you need it. At this very special low, low price of just \$1.00, you can afford to have your own copy of "Your Own Computer" everywhere you go—and give some to friends, too.

Don't delay. We're ordering a big reprint of this very popular feature section, but we're expecting a big demand, too. For your convenience, use the coupon below to order your own reprints of the single most authoritative, most colorful, most comprehensive report on today's Personal Computers.

Please send me _____ copies @ \$1.00. Total \$_____

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

17 Slate Lane, Central Islip, New York 11722

Ms. Nancy Extrada

Send me 32 copies of the special section of RADIO-ELECTRONICS "Your Own Computer" report. My check or money order is enclosed. New York State residents must include State Sales Tax. CANADA—Add 50¢ postage. ALL OTHER COUNTRIES—Add \$1.00 postage.

9704 NLS
1c SALE

LM3A 3 dig 1% DC \$134.00
LM3A 3 dig 1% DC \$158.50
LM3A 4 dig 1% DC \$209.00
LM4A 4 dig .03% DC \$250.00

- Rechargeable batteries and charger included
- Measures DC Volts, AC Volts, Ohms and Current
- Automatic polarity, decimal and overload indication
- Rechargeable batteries and charger
- Measures DC Volts, AC Volts, Ohms and Current
- Automatic polarity, decimal and overload indication
- No zero adjustment and no full-scale ohms adjust
- Battery-operated — NiCAD batteries; also AC line operation
- Large LCD display for easy reading without interpolation
- Size 1.9" x 2.7" x 4" D
- Parts & labor guaranteed 1 year
- This brand option \$3.50
- Leather case \$20.00

Purchase any of the LM series Meters and buy the LEATHER CASE for 1c

NLS MS-15 MINISCOPES with Rechargeable Batteries & Charger Unit

\$318.

MS-15 MINISCOPES

- 5" magnifying bandwidth
- External automatic line trigger
- Time base 1" microsec. to 0.5 Sec/div - 21 settings - 1.3%
- Battery back line operation
- Automatic & line sync modes
- Power consumption 100 watts
- Vertical gain - 50 to 100 Volts - 12 settings x 1.3
- Horizontal gain 1" to 3"
- Line sync 1.7 MHz to 1.5 MHz, 300 pps
- 100 pps to 100 kHz
- 100 pps to 100 kHz
- 100 pps to 100 kHz

MS-215 Dual Trace Version of MS-15 \$435.

SALE S-100 BUS EDGE CONNECTORS

Other Popular Edge Connectors

ATTN: OEM'S & Distributors, many other connectors available at our quotation

3 LEVEL GOLD WIRE WRAP SOCKETS

Sockets purchased in multiples of 50 per type may be combined for best price

	1-24	25-49	50-99	100-249	250-999	1K-5K
8 pin**	41	38	35	31	27	23
14 pin**	39	36	33	29	25	21
16 pin**	42	39	35	32	28	23
18 pin	63	58	54	47	42	36
20 pin	80	75	70	63	58	53
22 pin**	90	85	80	70	61	57
24 pin	90	84	78	68	63	58
28 pin	110	104	98	84	76	71
40 pin	150	140	130	120	104	89

All sockets are Gold 3 level closed entry **End and side, available 2 level. Solder Test Low Profile Tin Sockets and Dip Plugs available CALL FOR QUOTATION

LIQUID CRYSTAL DIGITAL CLOCK-CALENDAR

• For Auto. Home Office

• Clock in size (2 1/2" x 1 1/2")

• Push button for seconds release for date

• Check month anywhere with other 3M source

• Set date of WEEKEND (included)

• 2 MODELS AVAILABLE

• LCD-101, portable model runs on self-contained batteries for better than a year

• LCD-102, bench model 12 Volt system and 10 back

• LCD-103 on LCD-102

• Your choice

\$34.95

• Clear base stand for

\$2.00

8803 VECTOR BOARD

1500 BUS MICRO COMPUTERS

Price: \$29.50

8800V VECTOR

Plugboards

8801-1

Same as 8800V except plain, less power buses & heat sink

3577 9.6" x 4.5"

\$10.90

3577-2 6.5" x 4.5"

\$9.74

3577-3 6.5" x 4.5"

\$7.65

3577-4 6.5" x 4.5"

\$11.45

3577-5 6.5" x 4.5"

\$11.45

3577-6 6.5" x 4.5"

\$11.45

3577-237 6.5" x 4.5"

\$11.45

3577

Rockwell AIM 65

The Head-Start in Computers

AIM 65 Technical Overview

THERMAL PRINTER

Most desired feature on low-cost microcomputer systems . . .
Wide 20-column printout
Variable 5 x 7 dot matrix format
Complete 64-character ASCII alphanumeric format
Fast 120 lines per minute
Quiet thermal operation
Proven reliability

FULL-SIZE ALPHANUMERIC KEYBOARD

Provides compatibility with system terminals . . .
Standard 54 key, terminal-style layout
26 alphabetic characters
10 numeric characters
22 special characters
9 control functions
3 user-defined functions

TRUE ALPHANUMERIC DISPLAY

Provides legible and lengthy display . . .
20 characters wide
16-segment characters
High contrast monolithic characters
Complete 64-character ASCII alphanumeric format

PROVEN R6500 MICROCOMPUTER SYSTEM DEVICES

Reliable, high performance NMOS technology . . .
R6502 Central Processing Unit (CPU), operating at 1 MHz.
Has 65K address capability, 13 addressing modes and true index capability. Simple, but powerful 56 instructions.
Read/Write Memory using R2114 Static RAM devices. Available in 1K byte and 4K byte versions.

6K Monitor Program Memory, using R2332 Static ROM devices. Has sockets to accept additional 2332 ROM or 2532 PROM devices, to expand on-board Program Memory up to 20K bytes.
R6532 ROM-Input/Output-Timer (RIOT) combination device. Multipurpose circuit for almost 65 Monitor functions.
Two R6522 Versatile Interface Adapter (VIA) devices, which support AIM 65 and user functions. Each VIA has two parallel and one serial 8-bit, bidirectional I/O ports, two 2-bit peripheral handshake control lines and two fully-programmable 16-bit interval timer/event counters.

BUILT-IN EXPANSION CAPABILITY

44-Pin Application Connector for peripheral add-ons
44-Pin Expansion Connector has full system bus
Both connectors are KIM-1 compatible
TTY and AUDIO CASSETTE INTERFACES
Standard interface to low-cost peripherals
20 mA current loop TTY interface
Interface for two audio cassette recorders
Two audio cassette formatters: ASCII KIM-1 compatible and binary blocked file assembler compatible

ROM-RESIDENT ADVANCED INTERACTIVE MONITOR

Advanced features found only on larger systems
Monitor-generated prompts
Single keystroke commands
Address independent data entry
Debug aids
Error messages
Option and user interface linkage

MONEY BACK GUARANTEE

If you are not convinced that the AIM 65 is the best of its kind on the market, we will refund your money immediately.

TRINICO INTERNATIONAL

2795-L West Lincoln Ave.
Anaheim, CA 92801
(714) 821-0234

Store Hours 10 - 7, Mon. - Sat.

VISA

MASTERCARD

ADVANCED INTERACTIVE MONITOR COMMANDS

Major Function Entry
(RESET) Button—Enter and initialize Monitor
ESC—Re-enter Monitor
E—Enter and initialize Text Editor
T—Re-enter Text Editor
N—Enter Assembler
5—Enter and initialize BASIC Interpreter
6—Re-enter BASIC Interpreter

Instruction Entry and Disassembly

I—Enter mnemonic instruction entry mode
K—Disassemble memory

Display/Alter Registers and Memory

A—Alter Program Counter to (address)
A—Alter Accumulator to (byte)
X—Alter X Register to (byte)
Y—Alter Y Register to (byte)
P—Alter Processor Status to (byte)
S—Alter Stack Pointer to (byte)
R—Display all registers
M—Displays four memory locations, starting (I) address

(SPACE)—Display next four memory locations

—Alter current memory location

Manipulate Breakpoints

#—Clear all breakpoints
4—Toggle breakpoint enable on/off
5—Set one to four breakpoint addresses
7—Display breakpoint addresses

Control Instruction/Trace

—Execute user's program
Z—Toggle instruction trace mode on/off
V—Toggle register trace mode on/off
H—Trace Program Counter history

Control Peripheral Devices

L—Load object code into memory from peripheral I/O device
D—Dump object code to peripheral I/O device

1—Toggle Tape 1 control on/off
2—Toggle Tape 2 control on/off
3—Toggle checkmark

CTRL PRINT—Toggle Printer on/off
L—Line Feed

Monitor Prompt Display contents

Call User-Defined Functions

F1—Call User Function 1
F2—Call User Function 2
F3—Call User Function 3

Text Editor Commands

R—Read lines into text buffer from peripheral I/O device
I—Insert line into text buffer from Keyboard
K—Delete current line of text
(SPACE)—Display current line of text
L—List lines of text to peripheral I/O device
M—Move up one line
D—Move down one line
G—Go to top line of text
B—Go to bottom line of text
F—Find character string
C—Change character string
O—Quit Text Editor, return to Monitor

LOW COST PLUG-IN ROM OPTIONS

4K ASSEMBLER—jymbic, two-pass
6K BASIC Interpreter

POWER SUPPLY SPECIFICATIONS

5 VDC ± 1% regulated @ 2.0 amps (max)
5 VDC ± 1% unregulated @ 2.5 amps (peak)
0.5 amps (average)

AIM 65 (1K) \$375.00 ("\$15.00)

AIM 65 (4K) \$450.00 ("\$15.00)

Assembler ROM—Add \$95.00

BASIC Interpreter—Add \$100.00

Power Supply—Add \$45.00

Shipping and handling charge

Cash, residents 8% sales tax



Rockwell's AIM 65 Advanced Interactive Microcomputer can get you into the exciting world of microcomputers a lot easier and at a lower cost than you may have thought possible. And you'll be working with the 6500 family, the advanced state-of-the-art NMOS system that's an everincreasing favorite for new commercial and hobbyist applications.

As a learning aid, AIM 65 gives you an assembled, versatile microcomputer system with a fullsize keyboard, 20-character display end, uniquely, a thermal printer. An on-board Advanced Interactive Monitor program provides extensive control and program development functions. And our AIM 65 User's Manual will help you along each step of the way.

You'll master fundamentals rapidly. Then you'll appreciate the fact that unlike the computer "toys" on the market, AIM 65 offers flexibility and expandability you would expect to find in a sophisticated microcomputer development system.

THERMAL PRINTER GIVES YOU HARD COPY — FAST AND QUIET.
AIM 65's 20-column Thermal Printer prints on low-cost, thermal roll paper at a fast 120 lines per minute. It produces all of the standard 64 ASCII characters with a crisp-printing five-by-seven dot matrix. AIM 65's on-board printer is a unique feature for a low-cost computer.

EXTENDED ALPHANUMERIC DISPLAY IS BUILT FOR UNDERSTANDING, NOT DECIPHERING.
AIM 65's terminal-style keyboard frees you from the hassles of fumbling around with a tiny calculator-type keypad. And its 54 keys provide 70 different alphabetic, numeric, control and special functions.

FULL-SIZE KEYBOARD IS DESIGNED FOR HUMANS, NOT ELVES.
AIM 65's terminal-style keyboard frees you from the hassles of fumbling around with a tiny calculator-type keypad. And its 54 keys provide 70 different alphabetic, numeric, control and special functions.

ON-BOARD ADVANCED INTERACTIVE MONITOR GETS YOUR PROGRAMS UP AND RUNNING.
The ROM-resident AIM 65 Advanced Interactive Monitor Program provides a comprehensive set of easy-to-use, single-keystroke commands for debugging your programs, and offers features normally available only in larger, expensive microcomputer development systems. And with the AIM 65 Monitor, there's no guesswork involved; the Monitor gives a self-explanatory prompt when it needs information and it will generate a meaningful error message if an error has occurred.

The AIM 65 Monitor includes commands to:
• Enter and edit programs directly — no "opcode" memorization
• List programs on Printer or TTY
• Display/register registers and memory
• Set breakpoints, trace and debug program execution
• Control the Thermal Printer
• Transfer information to/from attached Cassette Recorders or TTY
• Execute programs on on-board or external ROM, ROM or PROM memory
• Interface the optional AIM 65 Assembler and BASIC Interpreter

AIM 65'S ADVANCED R6500 NMOS ARCHITECTURE.
The R6502 Central Processing Unit is the heart of the AIM 65. It provides demonstrated speed and simplicity, plus 65K addressability and the power of a 56-command, microcomputer-like instruction set.

The R6532 ROM-Input/Output-Timer (RIOT) combination device is used by the AIM 65 Monitor for scratchpad memory and keyboard operations.

Two R6522 Versatile Interface Adapter (VIA) devices are provided. One device supports AIM 65's Thermal Printer and the TTY. The other supports two user-designated 6-line I/O ports, plus an 8-bit serial I/O port and access to two 16-bit interval timer/event counters, on the module's Application Connector.

AIM 65's memory has two R2332 4K Read Only Memory (ROM) devices installed. These hold the Advanced Interactive Monitor program. Spare sockets allow you to expand on-board ROM up to 20K bytes. These sockets will accept user programs on R2332 ROMs or compatible PROMs, or can be used to install the optional AIM 65 Assembler and BASIC Interpreter ROM devices.

On-Board Read/Write RAM memory is available in 1K-byte and 4K-byte configurations.

AIM 65 HAS EXPANSION BUILT IN.
And to allow AIM 65 to grow the way you want it, we've provided an Application Connector and Expansion Connector. Both the Application Connector and Expansion Connector permit you to add a TTY (20 mA current loop) and one or two standard audio cassette recorders. It also has the pinouts for the VIA's General-Purpose I/O ports. The Expansion Connector extends AIM 65's system bus — address, data and control — out to additional memory, or anything else you might attach.

And, BASIC high-level language programming is a built-in option.

KITS • KITS • KITS

Perforated Boards **NOT INCLUDED** w/100 Series



- 103 MINI-WINK NEON FLASHER.** Random flash pattern. Interesting displays. 6 neon lamps. AC operated.
- | | | |
|-----------------------|-------|--------|
| 103 | | \$3.00 |
| 103A (103 w/PCB) | | 4.65 |
| 103B (103 w/PCB,CASE) | | 6.90 |



- 110 ELECTRONIC WHOOPER SIREN.** Powerful wailing sound. Dual oscillator circuit. Use with any alarm circuit. Battery not included.
- | | | |
|-----------------------|-------|--------|
| 110 | | \$4.95 |
| 110A (110 w/PCB) | | 6.50 |
| 110B (110 w/PCB,CASE) | | 9.60 |



- 117 TUNABLE ELECTRONIC ORGAN.** Tunable 7-note scale. Play sing-a-long favorites. Battery not included.
- | | | |
|-----------------------|-------|--------|
| 117 | | \$7.55 |
| 117A (117 w/PCB) | | 9.50 |
| 117B (117 w/PCB,CASE) | | 12.60 |



- 120 SIREN/CODE OSCILLATOR.** Loud, piercing alarm. Practice Morse code. Battery not included.
- | | | |
|-----------------------|-------|--------|
| 120 | | \$4.20 |
| 120A (120 w/PCB) | | 5.55 |
| 120B (120 w/PCB,CASE) | | 8.65 |



- 104 VARIABLE STROBE LIGHT.** Great for parties and photography. Variable flash rate. AC operated.
- | | | |
|-----------------------|-------|---------|
| 104 | | \$10.60 |
| 104A (104 w/PCB) | | 14.85 |
| 104B (104 w/PCB,CASE) | | 20.35 |



- 126 PROGRAMMABLE OODORBELL.** Adjustable rate and pitch for 15 musical notes. Play favorite tunes. 6 IC's. Uses existing transformer and switch.
- | | | |
|-----------------------|-------|---------|
| 126 | | \$16.95 |
| 126A (126 w/PCB) | | 23.70 |
| 126B (126 w/PCB,CASE) | | 29.20 |

502 POWER SUPPLY. Switch from 6 to 9V DC. 100mA output. Filtered. Manual. Stepdown transformer. Insulated test clips.



\$6.95 Complete

540 BINARY CLOCK. Handcraft tomorrow's timepiece today. Watch constantly changing patterns of LED's as they display Binary Time. This unique clock project enhances the learning of Digital Logic and the Binary Coding System, as well as offering a beautifully styled conversation piece.

10 TTL INTEGRATED CIRCUITS • VOLTAGE REGULATOR • MANUAL TEACHES BINARY SYSTEM • FAST, SLOW AND HOLD CONTROLS • 115VAC 50 or 60Hz.



\$39.95 Complete

523 STROBE LITE. Create flashing light effects. Ideal for creating kaleidoscope effects for photography. Long life flash tube. PCB. Manual. Variable flash control. On-off switch. Silicon diodes. 117VAC 50-60 Hz.



\$22.95 Complete

536 8-TRANSISTOR AM RADIO. Experience jewel-like clarity in sound. The best superheterodyne kit circuit available. SEPARATE LOCAL OSCILLATOR for high sensitivity and excellent selectivity. Unique IF Transformer mounting system. Manual. 9V battery required (not included).



\$16.45 Complete

504 TRANSISTOR AMPLIFIER. 4 Transistors. Push-Pull output. Variable volume control. Requires one 9V battery (not included). PCB. Manual. 3 transformer stages for maximum gain. Power output 360mW. Can be operated with any 3.2 - 8 ohm speaker.



\$6.95 Complete

510 FIVE TUBE RADIO. Rediscover TUBES. This fun antique circuit offers high selectivity and sensitivity. 2 IF Transformers. HI-Q Ferrite antenna. Manual. Superheterodyne circuit. Large PM speaker. For 110-120 VAC or DC.



\$34.95 Complete

401 TACHOMETER. Know exactly when to shift. This fabulous Tach, with a range from 0-8 grand, will mount anywhere - dash, steering column, boat, motorcycle frame, etc. 250° wide sweep scale. Reading accuracy within 2% of full scale. PCB. Manual. Illuminated dial. For all cylinder engines.



\$27.95 Complete

Perforated Boards **NOT INCLUDED** w/100 Series



124 WARBLER SIREN. Two-tone oscillating siren. Loud and penetrating, 2 IC's. For automobile or other 12 volt systems.

- | | | |
|-----------------------|-------|--------|
| 124 | | \$5.65 |
| 124A (124 w/PCB) | | 7.10 |
| 124B (124 w/PCB,CASE) | | 10.20 |



105 FISH CALLER. Clicking sound imitates distressed fish. Adjustable speed. Battery not included.

- | | | |
|-----------------------|-------|--------|
| 105 | | \$3.15 |
| 105A (105 w/PCB) | | 4.30 |
| 105B (105 w/PCB,CASE) | | 5.80 |



107 COLOR ORGAN CONTROL - 3 CHANNEL. Over 200W per channel. Separate sensitivity control. HI-mid-lo frequency response. AC operated.

- | | | |
|-----------------------|-------|--------|
| 107 | | \$9.20 |
| 107A (107 w/PCB) | | 11.85 |
| 107B (107 w/PCB,CASE) | | 14.95 |



118 TV SCRAMBLER. Tunable to all VHF stations. 30 foot range. Battery not included.

- | | | |
|-----------------------|-------|--------|
| 118 | | \$1.95 |
| 118A (118 w/PCB) | | 2.90 |
| 118B (118 w/PCB,CASE) | | 4.40 |



122 COMPUTER SOUND EFFECTS GENERATOR. Produces weird, spacey sounds. 4 IC's. Control tone, rate and blip or glide. Battery not included.

- | | | |
|-----------------------|-------|---------|
| 122 | | \$14.95 |
| 122A (122 w/PCB) | | 19.40 |
| 122B (122 w/PCB,CASE) | | 22.75 |

We accept:
VISA,



MASTER CHARGE CALL NOW TOLL FREE
BANKAMERICARD 800-824-5136

IN CALIFORNIA CALL 800-852-7631
ASK FOR OPERATOR 318

DO NOT SEND CASH • NO COD • ORDER BY PHONE OR MAIL

MINIMUM ORDER \$10.00. CALIF. RESIDENTS
ADD 6% SALES TAX.

WE PAY POSTAGE AND HANDLING
IN U.S.A. OVERSEAS COUNTRIES:
ADD 15% OF TOTAL FOR POSTAGE.

SEND CHECK OR
MONEY ORDER TO:

Graymark International, Inc.
1751 McGaw Avenue Dept. 12 Irvine, CA 92714 (714) 540-5480

STUDENTS & TEACHERS

WITH YOUR ORDER, SEND PROOF OF YOUR STATUS AND RECEIVE 5% OF YOUR PRESENT ORDER AS A CREDIT CERTIFICATE YOU CAN USE ON YOUR NEXT ORDER.

CHRISTMAS SPECIAL OF 5% OFF EFFECTIVE ON ALL ORDERS MAILED BEFORE DECEMBER 25, 1978.

THE FIRST MEMORY SPECIAL YOU WON'T FORGET

2102-2	650ms	8/89 ¹	32/379 ¹	64/710 ¹	128/1350 ¹
2102-4	450ms	8/10 ¹	32/419 ¹	64/780 ¹	128/1450 ¹
21140	450ms	8/79 ¹	16/149 ¹	32/274 ¹	64/499 ¹

PRESALER - 250 MHZ

complete \$23⁹⁵

PRESALER - 650 MHZ

complete \$49⁹⁵

11C90 - PRESALER CHIP

650 mc \$19⁹⁵

SOLID STATE RELAY

• 400 V at 3 AMPS • TTL COMPATIBLE

• MICRO REED ACTUATED TO MINIMIZE

CHANCES OF AC POWER SPILLOVER INTO

LOGIC CIRCUITS \$3⁹⁵

CHEAPER BY THE 100

LEDS - (HP AXIAL RED)	100/8 ⁹⁵
LEDS - (MINI RED)	100/9 ⁹⁵
LEDS - (CUMBO RED)	100/13 ⁹⁵
LEDS - (DUAL COLOR)	100/59 ⁰⁰
1N4001 (50V 1 AMP)	100/4 ⁹⁵
1N4148 (SWITCHING DIODE)	100/3 ⁹⁵
2N4303 (NPN FET)	100/21 ⁹⁵
2N4392 (PNP-NPN LOW NOISE)	100/3 ⁹⁵

SINGLE

TDA2020-20 Watt	\$9 ⁹⁵
TL1020H-20 Watt	\$10 ⁵⁰
TL1130H-30 Watt	\$12 ⁵⁰
STR-50 -50 Watt	\$18 ⁹⁵

INSTALLATION, PARTS AND LABOR \$49⁹⁵

FREE SOCKETS WITH PURCHASE OF ANY OF THESE I.C.'s.

8080A SYSTEM	8008	895
8213	375	
8214	895	
8220	480	
8226	475	
8228	725	
8229	825	
8231	945	
8251	2150	
8252	1075	
8257	2050	
8259	2050	

Z-80 SYSTEM	3580	2750
3801	125	
3802	1250	
3803	4900	
3842	7300	

OPTO ISOLATORS

1. MC12	\$7 ⁹⁵
2. MC1000	\$8 ⁹⁵
3. 4N26	\$5 ⁹⁵
4. CL1422	

CLAIREX PHOTO MODULE (USE AS VOLTAGE VARIABLE RESISTOR - 40 MEG OHM 10 40 OHM - MILLION TO ONE RATIO - OR USE AS VERY HIGH VOLTAGE OPTO ISOLATOR) \$14⁹⁵

REFLECTIVE PHOTO COUPLERS

TL139 LED INTO PHOTO TRANSISTOR \$2⁹⁵

ROC100 INCANDESCENT INTO COS CELL -

20 MEG OHM OFF

RESISTANCE \$1⁹⁵

1801 SYSTEM

1827 2625

1828 1335

1852 1335

1856 1175

1857 1175

1861 2000

2650 1995

2651 1995

SC/NP 1495

CPU's cont.

8008 895

8035 1995

RAM

14024 480

3101 395

8225 295

1801 295

2101 325

2101A 325

2102 150

2102A 195

82510 495

82511 495

51011 3195

2107 150

1000 SYSTEM

6800 1695

6801 720

6802 795

6811 850

6850 895

6852 2195

6860 995

6862 1375

6800 SYSTEM

6502 1495

6520 1275

6527 1250

6530 1750

9900 SYSTEM

9900 6600

9901 5400

9902 1950

9903 5400

9981 5400

1801 SYSTEM

1827 2625

1828 1335

1852 1335

1856 1175

1857 1175

1861 2000

2650 1995

2651 1995

SC/NP 1495

3341 795

1502E 1095

PROC. LOGIC ARRAYS

823100 1195

823101 1195

STUFF RESISTERS

14024 480

MM1403AH 295

MM1506AH 295

MM1506AH 295

MM1506AH 295

MM1506AH 295

1500 MOTHER BOARD - 8 Slot Kit

69 00

1000 32K STATIC MEMORY BOARD

850ms 599 00

AND TESTED 450ms 735 00

extra low connectors 200ms 875 00

1500 FLOPPY CADD CONNECTIONS 3 50

MAIL KEYBOARD - 53 Keys 19 95

MAIL KEYBOARD - 14 Keys 33 95

KEYPAD - 16 Keys x mirrored 1 95

KEYPAD - 20 Keys x mirrored 2 95

WIRE WRAP TOYS 4 level 100/495

2 level 100/95

WIRE WRAP SOCKET PIN 100/95

TAPE READER - 12 level - includes both 29 00

IP SOURCE AND SINKS 29 00

MAKE YOUR OWN PAPER TAPE READER 10/9 50

1101 SPACED PHOTO TRANSISTORS 1 89

REED RELAY - TTL compatible 3 95

SOLID STATE RELAY - micro reed actuated for full isolation 3 95

CAPACITORS - 455 Kc miniature single section 1 95

PRECISION THERMISTORS 2 95

Y51 BEAD - 1% 5000 OHM 2 95

GLASS BEAD - 1% 15000 OHM 2 95

Y51 BEAD - 1% 200 OHM 2 95

POWER THERMISTOR - positive temperature coefficient 20-250 OHM 2 95

DATA CONVERTER - NES008 (8 bit) 7 95

DATA CONVERTER - DAC-01 (54 bit) 4 95

PHOTO DIODE - super fast 0.5ms 3 95

IR DETECTOR - super sensitive 4 95

READ OUTS - MULTI OIG

LED 3-1/2 dig 4" 95

LED 17-3 dig 1.25 - 6 dig 3.95 - 8 dig 4 95

PHOTO DEVICES - DIODES, STRs, BARRELINGS

2N5737 - 1.75 FT/100 79 MCI 1 95

3N38 3.25 MRO-250 195 LASCR 1 95

HIGH VOLTAGE TRANSISTORS

2N2511 100V 1400V 5A TO-3 7 95

2N2511 100V 1400V 5A TO-3 5 95

3601 100V 500V 5A Plastic 4 95

W62 20W 500V 1A Plastic 2 25

338-7 20W 350V 1A Plastic 1 50

HIGH VOLTAGE DIODES

UNMARKED 1500V at 1 AMP 10/99

EG 250 2500V at 35 AMP 1 95

W62L 6000V at 25 ma 1 95

SUBSTRATE 100,000V at 100 ma 2 95

CARBIDE DRILL BITS AND ROUTER BITS

for P.C. board use - MIXED SIZES

OUR MIX - DRILLS 10/12 95 100/95 00


OUR MIX - ROUTERS 10/15 95 100/125 00

INCLUDED FOR ONLY \$425⁰⁰

WE INSTALL YOUR LEVEL 2 SO YOU KEEP

FREQUENCY COUNTER KIT

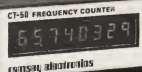Outstanding Performance
Incredible Price **\$89.95**
CT-50



The CT-50 is a versatile and precision frequency counter which will measure frequencies to 60 mHz and up to 600 mHz with the CT-600 option. Large Scale Integration, CMOS circuitry and solid state display technology have enabled this counter to match performance found in units selling for over three times as much. Low power consumption (typically 300-400 mW) makes the CT-50 ideal for portable battery operation. Features of the CT-50 include: large 8 digit LED display, RF shielded all metal case, easy pushbutton operation, automatic decimal point, fully socketed IC chips and input protection to 50 volts to insure against accidental burnout or overload. And, the best feature of all is the easy assembly. Clear, step by step instructions guide you to a finished unit you can rely on.

Order your today!

CT-50, 60 mHz counter kit	\$89.95	CB-1, Color TV calibrator-stabilizer	\$14.95
CT-50W, 50 mHz counter, wired and tested	159.95	DP-1, Diode probe, general purpose probe	12.95
CT-600, 600 mHz scaler option, add	29.95	HP-1, High impedance probe, non-loader	15.95

SPECIFICATIONS:

Frequency range: 8 Hz to 65 mHz, 600 mHz with CT-600
Resolution: 10 Hz @ 0.1 sec gate, 1 Hz @ 1 sec gate
Readout: 8 digit, 0.4" high LED, direct readout in mHz
Accuracy: adjustable to 0.5 ppm
Stability: 2.0 ppm over 10° to 40° C, temperature compensated
Input: 100 mV, 1 megohm/20 pF direct, 50 ohm with CT-600
Overload: 50VAC maximum, all modes
Sensitivity: less than 25 mV to 65 mHz, 50-150 mV to 600 mHz
Power: 110 VAC 5 Watts, 12 VDC @ 400 mA
Size: 6" x 4" x 2", high quality aluminum case, 2 lbs
ICs: 13 units, all socketed

CAR CLOCK



The UN-KIT, only
5 solder connections

Here's a super looking rugged and accurate auto clock which is a snap to build and install. Clock movement is completely assembled—you only solder 3 wires and 2 switches (takes about 15 minutes). Display is bright green with automatic brightness control photo-cell—assures you of a highly readable display day or night. Comes in a satin finish anodized aluminum case which can be attached 5 different ways using 2 sided tape. Choice of silver, black or gold case (specify).
DC-3 kit, 12 hour timer **\$22.95**
DC-3 kit, 24 hour timer **\$29.95**
DC-3 wired and tested **\$29.95**
110V AC adapter **\$5.95**

Under dash car clock



12-24 hour car clock in a beautiful plastic case features 8 jumbo LEDS high accuracy (1 min. mo.) easy 3 wire hookup display blanks with ignition and super instructions. Optional dimmer automatically adjusts display to ambient light level.
DC-11 clock with mfg bracket **\$27.95**
DM-1 dimmer adapter **2.50**

PRESCALER



Extend the range of your counter to 600 mHz. Works with any counter. Includes 2 transistor pre-amp to give pulse pens, typically 20 mV at 150 mHz. Specify: -10 or -100 ratio.
PS-1B, 600 mHz prescaler **\$59.95**
PS-1BK, 600 mHz oscillator kit **49.95**

FM WIRELESS MIKE KIT

Transmits up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V type FM-2 has additional sensitive mic preamp stage.
FM-1 kit **\$2.95** FM-2 kit **\$4.95**

COLOR ORGAN/MUSIC LIGHTS

See music come alive! 3 different lights flicker with music. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable and drives up to 300W. Great for parties, band music, night clubs and more.
Complete kit, ML-1 **\$7.95**

LED BLINKY KIT

A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volts.
Complete kit, BL-1 **\$2.95**

OP-AMP SPECIAL

741 mini dip	12/\$2.00
81-FET mini dip, 741 type	12/\$2.00

VIDEO TERMINAL

A completely self-contained, stand alone video terminal. Requires only an ASCII keyboard and TV set to become a complete terminal unit. Two units available, common features are: single 5V supply, XTAL controlled sync and baud rate (to 3600), complete computer and keyboard control of cursor. Parity error control and display. Accepts and generates serial ASCII plus parallel keyboard input. The 3216 is 32 char, by 16 lines, 2 pages with memory dump feature. The 6416 is 64 char by 16 lines, with scrolling, upper and lower case (optional) and has RS-232 and 20ma loop interfaces on board. Kits include sockets and complete documentation.
RE 3216, terminal card **\$149.95**
RE 6416, terminal card **199.95**
Lower Case option, 6416 only **13.95**
Power Supply Kit **14.95**
Video/RF Modulator, VD-1 **6.95**
Assembled, tested units, add **60.00**

CALENDAR ALARM CLOCK

The clock that's got it all! 6 1/2" LEDS, 12-24 hour, snooze, 24 hour alarm, 4 year calendar, battery backup, and lots more. The super 7001 chip is used. Size 5x4x2 inches.
Complete kit, less case (not available) **\$34.95**
DC-9

30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain 1 W in for 8 out, 2 in for 15 out, 4 W in for 30 out. Max output of 35 W, incredible value, complete with all parts, less case and T-R relay.
PA-1, 30 W pwr amp kit **\$22.95**
TR-1, RF sensed T-R relay kit **6.95**

Ramsey's famous MINI-KITS

VIDEO MODULATOR KIT

Converts any TV to video monitor. Super stable, tunable over 4-6 Runs on 5-15V, accepts std video signal. Best unit on the market.
Complete kit, VM-1 **\$5.95**

TONE DECODER

A complete tone decoder on a single PC board. Features: 400-5000 Hz adjustable range via 20 turn pot, voltage regulation 56T IC. Useful for touch tone decoding, tone burst detector, FSK, etc. Can also be used as a stable tone in coder. Runs on 5-16 12 volts.
Complete kit, TD-1 **\$5.95**

WHISPER LIGHT KIT

An interesting kit small mike picks up sounds and converts them to light. The louder the sound, the brighter the light. Completely self contained, includes mic, runs on 110VAC, controls up to 300 watts.
Complete kit, WL-1 **\$6.95**

SUPER SLEUTH

A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2 W rms output, runs on 6 to 15 volts. Uses 5-45 ohm speaker.
Complete kit, SN-9 **\$5.95**

POWER SUPPLY KIT

Complete triple regulated power supply provides variable 6 to 18 volts at 200 mA and +3V at 1 A. Amp. Excellent load regulation, good filtering and small size. Less transformers, requires 6 3V @ 1 A and 24 VCT.
Complete kit, PS-3LT **\$6.95**

SIREN KIT

Produces upward and downward wail characteristic of a police siren. 3 W peak audio output runs on 3-15 volts, uses 3-45 ohm speaker.
Complete kit, SM-3 **\$2.95**

FM MINI MIKE KIT



A super high performance FM wireless mike kit. Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mic. Kit includes case, mfg on/off switch, antenna, battery and super instructions. This is the finest unit available.

FM-3 kit

FM-3 wired and tested

\$12.95

16.95

CLOCK KITS

our Best Seller
your Best Deal

Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six 4" LED digits provide a highly readable display. This is a complete kit, no extra tools or it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, bronze black (specify).
Clock with 12-24 hour timer **\$22.95**
Clock with 10 min ID timer 12-24 hour **27.95**
DC-10 **27.95**
Alarm clock, 12 hour only, DC-8 **24.95**
12V DC car clock, DC-7 **27.95**
For wired and tested clocks add \$10.00 to kit price

Hard to find PARTS

LINEAR ICs		REGULATORS	
301	\$ 35	78GL	\$1.25
324	1.50	723	.50
380	1.25	309K	.85
380-A	.75	7805	2.35
555	.45	78L05	1.25
556	.65	7905	.25
556	.75	7812	.85
567	1.25	7912	1.95
1458	.50	7815	.85
3900	1.75	TLA	
		74500	
CMOS ICs		TTL ICs	
4011	20	7474	35
2N3906 type	10/1.00	4511	2.00
2N3908 type	10/1.00	551A	2.85
NPN 30W Pwr	3/1.00	5375AB	2.35
PNP 30W Pwr	3/1.00	7001	6.00
2N2055	6.00	4059-N	9.50
ULN 2805A type	3/2.00	7208	17.95
FET MPF102 type	3/2.00	LEDs	
UMF 12517B type	3/2.00	Jumbo red	8/1.00
MW-238 RF	11.95	Jumbo green	8/1.00
SOCKETS		Jumbo yellow	8/1.00
8 pin	10/2.00	Mini red	8/1.00
14 pin	10/2.00	Micro red	8/1.00
16 pin	10/2.00	Bi-color	75
24 pin	4/2.00	FERRITE BEADS	
28 pin	4/2.00	With info, specs	15/1.00
40 pin	3/2.00	6 hole bobbin	5/1.00

TERMS: Satisfaction guaranteed or money refunded. COD, add \$1.50. Minimum order \$5.00. Orders under \$10.00, add \$1.75. Add 5% for postage, insurance, handling. Overseas, add 15% V.W. results, add 7% tax.

ramsey electronics

BOX 4072, ROCHESTER, N.Y. 14610

PHONE ORDERS CALL

(716) 271-6487

CIRCLE 45 ON FREE INFORMATION CARD



Solar cell panels, used, OK condition

20 cell panel, 2" cells 6 volt 1/2 amp.....\$ 75.00

36 cell panel, 12 volt 1/2 amp.....100.00

24 cell panel, 8 volt .45 amp.....85.00

10 half cell panel, 5 volt 1/2 amp.....50.00

5 cell panel, 2.5 volt 1/2 amp.....40.00

Single 3.5 inch cell, 1 amp, .45 volt.....8.50

Solar power kit, 3.5 inch cell, motor, propeller. \$ 10.25

ULTRASONIC room alarm, intrusion detection with full data for hookup.....40.00



SEE IN THE DARK

IR viewer complete ready to operate. Guaranteed by the manufacturer.

Portable, runs on lantern battery. New, see in total darkness.

No shipments to Calif. Comes complete with built in IR source and adjustable focus lens.

SPL-21 \$199.00

All items FOB Lynn, Mass. Send for free 64 page catalog jam packed with goodies.

Meshna Inc., PO Box 62, E. Lynn, Mass. 01904

CIRCLE 39 ON FREE INFORMATION CARD

UNIVERSAL 4Kx8 MEMORY BOARD KIT \$69.95 32-21023 1 fully buffered, 16 address lines, on board decoupling for any 4 of 64 pages, standard 44 pin bus, may be used with P.B. & K.		PRINTED CIRCUIT BOARD 4 x 4 in. SINGLE SILENT POWER BOARD 16 "A" 160.00 7 WATT D-6 LASER DIODE IR \$99.95 2N 3820 P 1 FT 5.45 2N 2827 P 1 FT 5.45 2N2646 V 1 FT 4.45 1R 902 TANGENT DIODES 4 \$1.00 7R 902S PROBE UNIT 5 \$1.00	
EXPANDABLE F8 CPU BOARD KIT \$99.00 featuring Fairbug PSU 1K of static rms, RS 232 interface, documentation, 64 BYTE input		MINIATURE MULTI-TURN TRIM POT 10K, 1K, 2K, 4K, 10K, 20K, 50K, 100K, 200K, 500K, 1Meg, 2Meg, 5.75 each 3/12/00 CHARGED COUPLED DEVICES CCD 302 100x100 Image Sensor \$95.00 CCD 300 100x100 Image Sensor \$145.00 VERIPAC PC BOARD.....\$4.00 This board is a 1/8" single sided power board, 40x40" DRILLED and ETCHED which will hold up to 21 single 16 pin IC's or 18 or 16 LSI DIP IC's with built in power supply connector	
C/MOS (DIODE CLAMPED) 4001 18 4019 37 4040 35 36 723 85 4002 18 4010 36 4080 38 36 724 86 4003 18 4021 36 4033 31 60 7403 113 4007 18 4022 36 4051 35 74 7406 40 4009 37 4023 18 4052 70 7405 30 4010 37 4024 75 4037 18 74 7401 145 4011 18 4025 18 4074 97 74 7406 113 4012 18 4027 37 4030 70 74 7401 145 4014 37 4028 36 7402 22 74 7401 145 4015 37 4030 33 7402 22 74 7401 145 4016 37 4031 33 7402 22 74 7401 145 4017 37 4032 33 7402 22 74 7401 145 4018 37 4033 33 7402 22 74 7401 145		LARGE LED's 2".....\$5.00 RED, YELLOW, GREEN & AMBER TLT-118 OPTO ISOLATOR.....\$ 7.75 MOLLEX PINS.....\$100.00 1 WATT ZENER'S 3.3, 4.7, 6.6, 9.1, 12, 15, 18, 22V 6.51/00 MCM68 MODERN CHIP.....\$9.95 MCM 6571A 7 x 8 character gen \$10.75	
CRYSTALS \$3.45 ea. 4000MHz 1.00 5.000MHz 1.00 6.000MHz 1.00 7.000MHz 1.00 8.000MHz 1.00 9.000MHz 1.00 10.000MHz 1.00		Silicon Power Rectifiers 1N4001 1A 50V 100 1.25 1N4002 1A 50V 100 1.25 1N4003 1A 50V 100 1.25 1N4099 1A 50V 100 1.25 1N4100 1A 50V 100 1.25	

WIRE WRAP

— PRECUT WIRE —

Why buy wire on rolls?

PRECUT & STRIPPED WIRE IS:

- Fast - No more cutting & stripping by hand
- Reliable - Good, clean, uniform strip
- Economical - Cheaper than using bulk wire

PRECUT WIRE		BULK WIRE	
100' spool 3" 45 31.40	50' roll at \$1.99	40' 100' spool 6" 11.18	100' roll at \$2.35
Wax Kit 1 at \$2.95	2.95/ea		

30 Kilar strip 3" on each end Lengths are overall Colors: Red-Blue-Green-Yellow-Black-Orange Wire packaged in plastic bags And 25' length for tubes

	100	500	1000
2 m	78	240	420K
3 m	82	260	471K
3 m	96	280	471K
4 m	90	300	552K
4 m	94	321	552K
5 m	98	342	634K
5 m	102	363	675K
5 m	106	385	716K
5 m	110	405	757K
7 m	120	425	788K
7 m	140	525	1035K
8 m	109	465	880K
8 m	132	485	921K
9 m	136	505	942K
1 m	140	525	1035K
1 m	145	551	1044K
1 m	150	571	1084K
1 m	155	591	1124K
1 m	160	611	1164K
1 m	165	631	1204K
1 m	170	651	1244K
1 m	175	671	1284K
1 m	180	691	1324K
1 m	185	711	1364K
1 m	190	731	1404K
1 m	195	751	1444K
1 m	200	771	1484K
1 m	205	791	1524K
1 m	210	811	1564K
1 m	215	831	1604K
1 m	220	851	1644K
1 m	225	871	1684K
1 m	230	891	1724K
1 m	235	911	1764K
1 m	240	931	1804K
1 m	245	951	1844K
1 m	250	971	1884K
1 m	255	991	1924K
1 m	260	1011	1964K
1 m	265	1031	2004K
1 m	270	1051	2044K
1 m	275	1071	2084K
1 m	280	1091	2124K
1 m	285	1111	2164K
1 m	290	1131	2204K
1 m	295	1151	2244K
1 m	300	1171	2284K
1 m	305	1191	2324K
1 m	310	1211	2364K
1 m	315	1231	2404K
1 m	320	1251	2444K
1 m	325	1271	2484K
1 m	330	1291	2524K
1 m	335	1311	2564K
1 m	340	1331	2604K
1 m	345	1351	2644K
1 m	350	1371	2684K
1 m	355	1391	2724K
1 m	360	1411	2764K
1 m	365	1431	2804K
1 m	370	1451	2844K
1 m	375	1471	2884K
1 m	380	1491	2924K
1 m	385	1511	2964K
1 m	390	1531	3004K
1 m	395	1551	3044K
1 m	400	1571	3084K
1 m	405	1591	3124K
1 m	410	1611	3164K
1 m	415	1631	3204K
1 m	420	1651	3244K
1 m	425	1671	3284K
1 m	430	1691	3324K
1 m	435	1711	3364K
1 m	440	1731	3404K
1 m	445	1751	3444K
1 m	450	1771	3484K
1 m	455	1791	3524K
1 m	460	1811	3564K
1 m	465	1831	3604K
1 m	470	1851	3644K
1 m	475	1871	3684K
1 m	480	1891	3724K
1 m	485	1911	3764K
1 m	490	1931	3804K
1 m	495	1951	3844K
1 m	500	1971	3884K
1 m	505	1991	3924K
1 m	510	2011	3964K
1 m	515	2031	4004K
1 m	520	2051	4044K
1 m	525	2071	4084K
1 m	530	2091	4124K
1 m	535	2111	4164K
1 m	540	2131	4204K
1 m	545	2151	4244K
1 m	550	2171	4284K
1 m	555	2191	4324K
1 m	560	2211	4364K
1 m	565	2231	4404K
1 m	570	2251	4444K
1 m	575	2271	4484K
1 m	580	2291	4524K
1 m	585	2311	4564K
1 m	590	2331	4604K
1 m	595	2351	4644K
1 m	600	2371	4684K
1 m	605	2391	4724K
1 m	610	2411	4764K
1 m	615	2431	4804K
1 m	620	2451	4844K
1 m	625	2471	4884K
1 m	630	2491	4924K
1 m	635	2511	4964K
1 m	640	2531	5004K
1 m	645	2551	5044K
1 m	650	2571	5084K
1 m	655	2591	5124K
1 m	660	2611	5164K
1 m	665	2631	5204K
1 m	670	2651	5244K
1 m	675	2671	5284K
1 m	680	2691	5324K
1 m	685	2711	5364K
1 m	690	2731	5404K
1 m	695	2751	5444K
1 m	700	2771	5484K
1 m	705	2791	5524K
1 m	710	2811	5564K
1 m	715	2831	5604K
1 m	720	2851	5644K
1 m	725	2871	5684K
1 m	730	2891	5724K
1 m	735	2911	5764K
1 m	740	2931	5804K
1 m	745	2951	5844K
1 m	750	2971	5884K
1 m	755	2991	5924K
1 m	760	3011	5964K
1 m	765	3031	6004K
1 m	770	3051	6044K
1 m	775	3071	6084K
1 m	780	3091	6124K
1 m	785	3111	6164K
1 m	790	3131	6204K
1 m	795	3151	6244K
1 m	800	3171	6284K
1 m	805	3191	6324K
1 m	810	3211	6364K
1 m	815	3231	6404K
1 m	820	3251	6444K
1 m	825	3271	6484K
1 m	830	3291	6524K
1 m	835	3311	6564K
1 m	840	3331	6604K
1 m	845	3351	6644K
1 m	850	3371	6684K

Active Electronic Sales Corp.

1978 IC MASTER

Complete integrated circuit data selector. New 1978 edition (2200 pages) is twice as big as last year. Master guide to the latest IC's including microprocessors and consumer circuits.

Free quarterly updates

\$24.95 \$19.95

Tremendous Opportunity. Subject to Prior Sale. Lowest Price Ever Offered Anywhere.



TTL LOW POWER SCHOTTKY PLASTIC DUAL-IN-LINE I.C.

Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price
74LS00	15	74LS47	89	74LS123	79	74LS170	125	74LS258	75	74LS368	55
74LS01	15	74LS48	89	74LS124	99	74LS173	99	74LS259	145	74LS373	175
74LS02	15	74LS49	89	74LS125	59	74LS174	69	74LS260	29	74LS374	175
74LS03	15	74LS50	19	74LS126	59	74LS175	69	74LS261	185	74LS375	175
74LS04	19	74LS54	19	74LS127	79	74LS181	250	74LS266	39	74LS377	150
74LS05	19	74LS55	19	74LS130	29	74LS183	350	74LS273	165	74LS378	125
74LS06	19	74LS63	150	74LS136	39	74LS190	89	74LS275	450	74LS379	135
74LS09	19	74LS73	29	74LS138	64	74LS191	89	74LS279	59	74LS386	49
74LS10	15	74LS74	35	74LS139	64	74LS192	95	74LS280	175	74LS390	150
74LS11	19	74LS75	49	74LS145	99	74LS193	95	74LS283	85	74LS393	125
74LS12	19	74LS76	39	74LS147	195	74LS194	75	74LS290	85	74LS395	150
74LS13	35	74LS78	39	74LS148	99	74LS195	66	74LS293	110	74LS396	170
74LS14	59	74LS83	99	74LS151	59	74LS196	109	74LS295	125	74LS398	265
74LS15	19	74LS85	99	74LS153	59	74LS197	109	74LS298	125	74LS399	150
74LS20	15	74LS86	35	74LS155	99	74LS221	125	74LS299	295	74LS424	450
74LS21	19	74LS90	59	74LS156	80	74LS240	135	74LS324	125	74LS445	125
74LS22	19	74LS91	99	74LS157	59	74LS241	195	74LS325	255	74LS447	125
74LS26	25	74LS92	59	74LS158	69	74LS242	195	74LS326	255	74LS480	195
74LS27	21	74LS93	49	74LS160	84	74LS243	195	74LS327	255	74LS668	90
74LS28	21	74LS95	70	74LS161	84	74LS244	195	74LS347	125	74LS669	90
74LS30	15	74LS96	99	74LS162	84	74LS245	195	74LS348	175	74LS670	200
74LS32	25	74LS107	39	74LS163	84	74LS247	125	74LS352	135		
74LS33	27	74LS109	32	74LS164	89	74LS248	125	74LS353	135		
74LS37	23	74LS112	32	74LS165	125	74LS249	125	74LS362	700		
74LS38	23	74LS113	39	74LS166	145	74LS251	85	74LS365	55		
74LS40	19	74LS114	59	74LS168	150	74LS253	85	74LS366	55		
74LS42	34	74LS122	50	74LS169	130	74LS257	80	74LS367	55		

Dual In-line

Sockets

Finest Quality Sockets Available Anywhere

Stock level	Contacts	Price
14000	8 PIN	.11
345000	14 PIN	.13
156000	16 PIN	.15
33000	18 PIN	.19
18000	22 PIN	.27
84000	24 PIN	.28
25000	28 PIN	.36
46000	40 PIN	.48

- PLUGGABLE SOCKET FOR IC PACKAGES WITH LEADS
- HIGH RELIABILITY GAS TIGHT JOINT
- FULLY QUALIFIED TO MIL-STD-883C
- COMPACT LOW PROFILE DESIGN
- NO WICKING WHEN SOLDERED TO PCB BOARD
- FLAMMABILITY RATING UL 94V0

All new major manufacturer production material offered. Largest variety of device types available anywhere.

LINEAR I.C.'S

LM324N	.49	Quad Op Amp
LM339N	.49	Quad Comparator
LM555N	.8	Timer
LM556N	.14	Dual Timer
LM723CN	.34	Voltage Regulator
LM723CN	.39	Voltage Regulator
LM741CN	.37	Op Amp
LM741CN	.24	Op Amp
LM1458N	.39	Dual Op Amp

MOS Static RAM'S

Stock level	Part No.	Price
41400	2114	7.50
	4K (1K x 4) 450NS	
59500	2102LFPC	1.19
	1K 350NS (Low Power)	

MOS Dynamic RAM'S

Stock level	Part No.	Price
21110	4K 4060 300NS	3.95
27550	16K 416-3 200NS	11.95
18650	16K 416-5 300MS	8.95
<hr/>		
UART's		
Stock level	Part No.	Price
29000	AY5-1013A	4.95
9200	AY3-1015	5.95

1K CMOS RAM

Stock level	Part No.	Price
4400	5101	4.95
	450NS (Low Power)	


MICROPROCESSOR CHIPS

Stock level	Part No.	Price
21600	8080A	3.95 5.50
2700	6800	3.95 7.95

INTERFACE SUPPORT CIRCUITS

Stock level	Part No.	Price
1250	8212	1.98
1800	8214	3.95 3.95
11200	8216	1.98
1700	8224	2.75
2800	8226	1.98
1500	8228	4.75
1000	8238	4.75
4900	8251	3.95 4.95
500	8253	14.95
5200	8255	5.95
1100	8257	9.95
300	8259	14.95
1500	6810	3.95 3.50
1700	6820	4.95 3.95
1400	6821	3.95 3.95
2800	6850	5.95 4.95
700	6852	3.95 4.95

SWITCHING DIODES

		1N4148	(100V 4N5)	027
<hr/>				
 Zilog	Z80-CPU	14.95	Z80-SIO/0	59.00
	Z80A-CPU	24.95	Z80A-SIO/0	68.00
	Z80-PIO	7.95	(common TX & RX clock	
	Z80A-PIO	11.95	with DTRB)	
	Z80-CTC	7.95	Z80-SIO/1	59.00
	Z80A-CTC	11.95	Z80A-SIO/1	68.00
	Z80-DMA	46.00	(separate TX & RX clock	

Active Electronic Sales Corp.

P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701

Over the counter sales.
12 Mercer Rd., Woburn, Mass. 01790
Behind Zaynes on Rte. 9
Telephone Orders & Enquiries (617) 879-0077

IN CANADA 3 LOCATIONS

5651 FERRIER ST.
MONTREAL, QUEBEC
H4P 2G2
Tel: (514) 735-8425

4600 DUFFERIN ST.
DOWNSVIEW, ONTARIO
M3H 5S6
Tel: (416) 661-1115

BAXTER CENTRE
1050 BAXTER ROAD
OTTAWA, ONTARIO
K2C 3P2
Tel: (613) 593-9471



RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

42	Active Electronics.....	129
	Advance Electronics.....	22,79,86,87
3	Advanced Computer Products.....	109
—	A M C Sales.....	104
2	American Antenna.....	Cov. 4
70	A P Products, Inc.....	17
5	A V R Electronics.....	108
6	Audio-Technica.....	25
	Karel Barta.....	110
60	B & K Precision Dynascan Co.....	34
—	Bullett Electronics.....	104
—	Burdex Security Co.....	103
80	Byte.....	99
64	C F R Associates.....	120
—	Chaney.....	130

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

ATTACH
LABEL
HERE

Your old address and zip code

Your new address and zip code

name (please print)

address

city state zip code

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80322

RADIO-ELECTRONICS

Spend less. Test more.

Faster, easier and more economical digital testing. That's what CSC's Logic Probes are all about. And that's what engineers, technicians and hobbyists need, to deal with the increased use and complexity of digital circuits.

Unlike oscilloscopes, meters and other conventional test equipment, CSC probes are *logic-state oriented*. Just touch the probe to a circuit node and *instantly* read logic state, detect level transitions, check duty cycles. And store high-speed, low-rep-rate events that even fast scopes miss.

By accurately detecting the state of individual logic elements without removing ICs or cutting copper paths, CSC's circuit-powered,

without pulse memory capability. Handling a minimum pulse width of 300 nanoseconds, this 300 K ohm probe is the economical way to test



circuits up to 1.5 MHz. It detects pulse trains or single-shot events in TTL, DTL, HTL and CMOS circuits, replacing separate pulse detectors, pulse stretchers and node state analyzers.

LP-3 LOGIC PROBE. \$69.95*

Our LP-3 has all the features of the LP-1 plus extra high speed. It captures pulses as narrow as 10 nanoseconds, and monitors pulse trains to over 50 MHz. Giving you the essential capabilities of a high-quality memory scope at about 1/100th the cost. LP-3 captures

one-shot or low-rep-rate events all-but-impossible to detect any other way. All without the weight, bulk, inconvenience and power consumption of conventional methods.



Use CSC's highly versatile logic probes for testing, debugging or servicing any type of digital circuit. They give you a lot of information about IC circuit conditions... and help you do more in less time. For less money.

NEED MORE INFORMATION? CALL

203-624-3103 to order, or for the name of your local distributor. Prices slightly higher outside U.S.A.



multi-family Logic Probes locate over 95% of circuit problems in minutes instead of hours. And they're easy to use. Simply connect two clip leads across the power supply, touch the probe tip to a node and watch the LEDs.

LP-1 LOGIC PROBE. \$44.95*

LP-1 has a minimum detectable pulse width of 50 nanoseconds and maximum input frequency of 10 MHz. This 100 K ohm probe is an inexpensive workhorse for any shop, lab or field service tool kit. It detects high-speed pulse trains or one-shot events and stores pulse or level transitions, replacing separate level detectors, pulse detectors, pulse stretchers and pulse memory devices. All, for less than the price of a DVM.

LP-2 LOGIC PROBE. \$24.95*

LP-2 performs the same basic functions as the LP-1, but for slower-speed circuits and

© 1978, Continental Specialties Corporation. Prices, specifications, subject to change without notice.

*Manufacturer's suggested retail.

Corporate Headquarters:

Continental Specialties Corporation

70 Fulton Terr. Box 1942, New Haven, CT 06509

351 California St. San Francisco, CA 94104

(415) 421-8872, TWX 910-372-7992

CONTINENTAL SPECIALTIES CORPORATION



Europe, Africa, Mid-East: CSC UK LTD.

Shire Hill Industrial Estate, Units 1 and 2

Saffron Walden, Essex CB 11 3AQ

Telephone Number SAFFRON WALDEN 21682

TLX 817477

CIRCLE 7 ON FREE INFORMATION CARD

New, K40 Magnamount: Grips like a grapple, actually improves transmission.



We double guarantee it.*

Exclusive Octopole Construction.



That's eight magnets set in eight different directions to give you a magnetic seal so complete and powerful, your antenna would stay up there if you could squeeze between two semis passing each other at 180 miles an hour. That's magnetic octopower.

* GUARANTEE I

Placed on the roof of a vehicle; properly tuned, the K40 Magnamount is guaranteed to transmit a further distance than a standard K40 without the Magnamount or you will receive a prompt and full refund from your K40 dealer who installed and tuned the Magnamount K40 for you.

* GUARANTEE II

Materials and workmanship are guaranteed for a full 12 months. Any part that fails to perform satisfactorily will be replaced absolutely free.

Exclusive K40 Flux Harmonics for Greater Transmission.

The magnetic radiation pattern was designed to match the K40 antenna radiation for greater distance than the standard K40. See our guarantee.

The facts: Physics and Physical.

1. Magnamount is a bigger, stronger magnet—in fact it's 8 bigger, stronger, magnets.
2. It doesn't just hold the K40 antenna, it helps it transmit further.
3. Remember the law of reciprocity. The antenna that transmits better, receives better.
4. It provides a flatter, lower SWR because the Magnamount is capacitance grounded.
5. It puts your $\frac{3}{8}$ wave K40 antenna securely in place in the most advantageous place to work against a ground plane—high and free from obstruction. That's square in the middle, right up on top.

\$15.95 buys it.

(SUGGESTED RETAIL)

K40 Magnamount.

American Antenna 1945 South Street Elgin, Illinois 60120

This professional CB equipment available only through Registered K40 Dealers!

CIRCLE 2 ON FREE INFORMATION CARD